

ID:

Name:

**Brac University**

Semester: Fall 2023

Course Code: CSE250

Circuits And Electronics

Section: 18

Set

A

Assessment: *Class Assignment 1*

Duration: 1 hour 20 minutes

Date: September 28, 2023

Full Marks: 10

- ✓ No washroom breaks. Phones must be turned off. Using/carrying any notes during the exam is not allowed.
- ✓ All **4 questions** are compulsory. Marks allotted for each question are mentioned beside each question.
- ✓ Write your answers inside the indicated boxes (where applicable). If you run out of room, continue on the back page.
- ✓ Symbols have their usual meanings.

Student ID

1	<input type="radio"/>	<input type="radio"/>	<input type="radio"/>	<input type="radio"/>	<input type="radio"/>	<input type="radio"/>	<input type="radio"/>
2	<input type="radio"/>	<input type="radio"/>	<input type="radio"/>	<input type="radio"/>	<input type="radio"/>	<input type="radio"/>	<input type="radio"/>
3	<input type="radio"/>	<input type="radio"/>	<input type="radio"/>	<input type="radio"/>	<input type="radio"/>	<input type="radio"/>	<input type="radio"/>
4	<input type="radio"/>	<input type="radio"/>	<input type="radio"/>	<input type="radio"/>	<input type="radio"/>	<input type="radio"/>	<input type="radio"/>
5	<input type="radio"/>	<input type="radio"/>	<input type="radio"/>	<input type="radio"/>	<input type="radio"/>	<input type="radio"/>	<input type="radio"/>
6	<input type="radio"/>	<input type="radio"/>	<input type="radio"/>	<input type="radio"/>	<input type="radio"/>	<input type="radio"/>	<input type="radio"/>
7	<input type="radio"/>	<input type="radio"/>	<input type="radio"/>	<input type="radio"/>	<input type="radio"/>	<input type="radio"/>	<input type="radio"/>
8	<input type="radio"/>	<input type="radio"/>	<input type="radio"/>	<input type="radio"/>	<input type="radio"/>	<input type="radio"/>	<input type="radio"/>
9	<input type="radio"/>	<input type="radio"/>	<input type="radio"/>	<input type="radio"/>	<input type="radio"/>	<input type="radio"/>	<input type="radio"/>
0	<input type="radio"/>	<input type="radio"/>	<input type="radio"/>	<input type="radio"/>	<input type="radio"/>	<input type="radio"/>	<input type="radio"/>

Set Identifier

§ ☒ ☒ ☒ ☒ ☒ ☒ ☒ ☐

Answers (1-10)

	A	B	C	D	E
1	<input type="radio"/>	<input type="radio"/>	<input type="radio"/>	<input type="radio"/>	<input type="radio"/>
2	<input type="radio"/>	<input type="radio"/>	<input type="radio"/>	<input type="radio"/>	<input type="radio"/>
3	<input type="radio"/>	<input type="radio"/>	<input type="radio"/>	<input type="radio"/>	<input type="radio"/>
4	<input type="radio"/>	<input type="radio"/>	<input type="radio"/>	<input type="radio"/>	<input type="radio"/>
5	<input type="radio"/>	<input type="radio"/>	<input type="radio"/>	<input type="radio"/>	<input type="radio"/>

	A	B	C	D	E
6	<input type="radio"/>	<input type="radio"/>	<input type="radio"/>	<input type="radio"/>	<input type="radio"/>
7	<input type="radio"/>	<input type="radio"/>	<input type="radio"/>	<input type="radio"/>	<input type="radio"/>
8	<input type="radio"/>	<input type="radio"/>	<input type="radio"/>	<input type="radio"/>	<input type="radio"/>
9	<input type="radio"/>	<input type="radio"/>	<input type="radio"/>	<input type="radio"/>	<input type="radio"/>
10	<input type="radio"/>	<input type="radio"/>	<input type="radio"/>	<input type="radio"/>	<input type="radio"/>

Answers (11-20)

	A	B	C	D	E
11	<input type="radio"/>	<input type="radio"/>	<input type="radio"/>	<input type="radio"/>	<input type="radio"/>
12	<input type="radio"/>	<input type="radio"/>	<input type="radio"/>	<input type="radio"/>	<input type="radio"/>
13	<input type="radio"/>	<input type="radio"/>	<input type="radio"/>	<input type="radio"/>	<input type="radio"/>
14	<input type="radio"/>	<input type="radio"/>	<input type="radio"/>	<input type="radio"/>	<input type="radio"/>
15	<input type="radio"/>	<input type="radio"/>	<input type="radio"/>	<input type="radio"/>	<input type="radio"/>

	A	B	C	D	E
16	<input type="radio"/>	<input type="radio"/>	<input type="radio"/>	<input type="radio"/>	<input type="radio"/>
17	<input type="radio"/>	<input type="radio"/>	<input type="radio"/>	<input type="radio"/>	<input type="radio"/>
18	<input type="radio"/>	<input type="radio"/>	<input type="radio"/>	<input type="radio"/>	<input type="radio"/>
19	<input type="radio"/>	<input type="radio"/>	<input type="radio"/>	<input type="radio"/>	<input type="radio"/>
20	<input type="radio"/>	<input type="radio"/>	<input type="radio"/>	<input type="radio"/>	<input type="radio"/>


Answers (21-30)

	A	B	C	D	E
21	<input type="radio"/>	<input type="radio"/>	<input type="radio"/>	<input type="radio"/>	<input type="radio"/>
22	<input type="radio"/>	<input type="radio"/>	<input type="radio"/>	<input type="radio"/>	<input type="radio"/>
23	<input type="radio"/>	<input type="radio"/>	<input type="radio"/>	<input type="radio"/>	<input type="radio"/>
24	<input type="radio"/>	<input type="radio"/>	<input type="radio"/>	<input type="radio"/>	<input type="radio"/>
25	<input type="radio"/>	<input type="radio"/>	<input type="radio"/>	<input type="radio"/>	<input type="radio"/>


	A	B	C	D	E
26	<input type="radio"/>	<input type="radio"/>	<input type="radio"/>	<input type="radio"/>	<input type="radio"/>
27	<input type="radio"/>	<input type="radio"/>	<input type="radio"/>	<input type="radio"/>	<input type="radio"/>
28	<input type="radio"/>	<input type="radio"/>	<input type="radio"/>	<input type="radio"/>	<input type="radio"/>
29	<input type="radio"/>	<input type="radio"/>	<input type="radio"/>	<input type="radio"/>	<input type="radio"/>
30	<input type="radio"/>	<input type="radio"/>	<input type="radio"/>	<input type="radio"/>	<input type="radio"/>

## ◇ Question 1 of 4 [CO1] [2 marks]


Which of the following circuits is/are impossible (violates Kirchhoff's laws)?

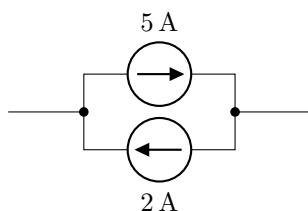

Circuit 1

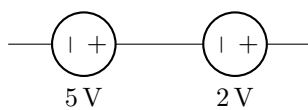


Circuit 2

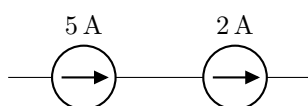

Circuit 3


- ☐ Circuit 3   
 ☐ Circuit 1 & 3   
 ☐ Circuit 2  
☒ **Circuit 1**   
 ☐ None of the above

## ◇ Question 2 of 4 [CO3] [2 marks]

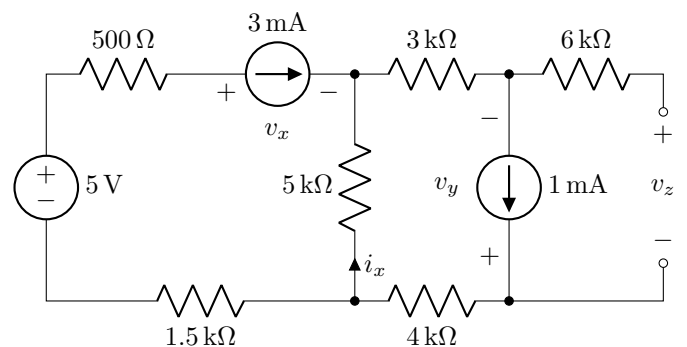

- ☐ c  
☒ **a**  
☐ b


◇ Question 3 of 4 [CO3] [5 marks]

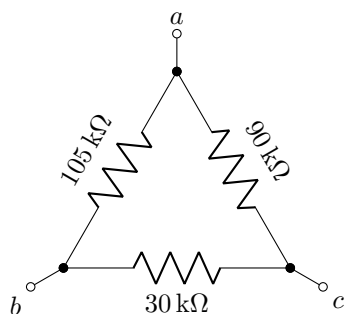

Which of the following statements is true?

- (A)  $R_{ab} = 56 \text{ k}\Omega$ ,  $R_{bc} = 26 \text{ k}\Omega$ ,  $R_{ca} = 54 \text{ k}\Omega$
- (B)  $R_{ab} = 105 \text{ k}\Omega$ ,  $R_{bc} = 30 \text{ k}\Omega$ ,  $R_{ca} = 90 \text{ k}\Omega$
- (C)  $R_{ab} = 56 \text{ }\Omega$ ,  $R_{bc} = 26 \text{ }\Omega$ ,  $R_{ca} = 54 \text{ }\Omega$
- (D)  $R_{ab} = R_{bc} = R_{ca} = 18.529 \text{ k}\Omega$
- (E) None of the above

◇ Question 4 of 4 [CO1] [1 mark]

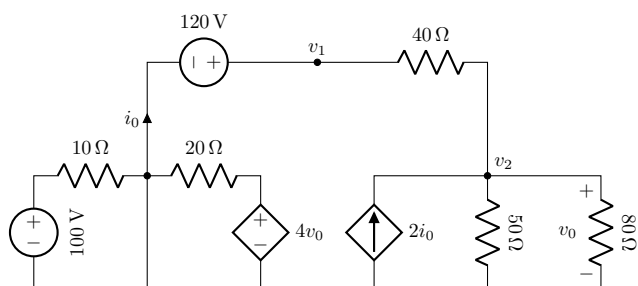

How many nodes are in this circuit?

- (A) 7 (B) 3 (C) 5 (D) 6 (E) 4

ID:

Name:

**Brac University**

Semester: Fall 2023

Course Code: CSE250

Circuits And Electronics

Section: 18

Set

B

Assessment: *Class Assignment 1*

Duration: 1 hour 20 minutes

Date: September 28, 2023

Full Marks: 10

- ✓ No washroom breaks. Phones must be turned off. Using/carrying any notes during the exam is not allowed.
- ✓ All **4 questions** are compulsory. Marks allotted for each question are mentioned beside each question.
- ✓ Write your answers inside the indicated boxes (where applicable). If you run out of room, continue on the back page.
- ✓ Symbols have their usual meanings.

Student ID

1	<input type="radio"/>	<input type="radio"/>	<input type="radio"/>	<input type="radio"/>	<input type="radio"/>	<input type="radio"/>	<input type="radio"/>
2	<input type="radio"/>	<input type="radio"/>	<input type="radio"/>	<input type="radio"/>	<input type="radio"/>	<input type="radio"/>	<input type="radio"/>
3	<input type="radio"/>	<input type="radio"/>	<input type="radio"/>	<input type="radio"/>	<input type="radio"/>	<input type="radio"/>	<input type="radio"/>
4	<input type="radio"/>	<input type="radio"/>	<input type="radio"/>	<input type="radio"/>	<input type="radio"/>	<input type="radio"/>	<input type="radio"/>
5	<input type="radio"/>	<input type="radio"/>	<input type="radio"/>	<input type="radio"/>	<input type="radio"/>	<input type="radio"/>	<input type="radio"/>
6	<input type="radio"/>	<input type="radio"/>	<input type="radio"/>	<input type="radio"/>	<input type="radio"/>	<input type="radio"/>	<input type="radio"/>
7	<input type="radio"/>	<input type="radio"/>	<input type="radio"/>	<input type="radio"/>	<input type="radio"/>	<input type="radio"/>	<input type="radio"/>
8	<input type="radio"/>	<input type="radio"/>	<input type="radio"/>	<input type="radio"/>	<input type="radio"/>	<input type="radio"/>	<input type="radio"/>
9	<input type="radio"/>	<input type="radio"/>	<input type="radio"/>	<input type="radio"/>	<input type="radio"/>	<input type="radio"/>	<input type="radio"/>
0	<input type="radio"/>	<input type="radio"/>	<input type="radio"/>	<input type="radio"/>	<input type="radio"/>	<input type="radio"/>	<input type="radio"/>

Set Identifier

§ ☒ ☒ ☒ ☒ ☒ ☒ ☐ ☒

Answers (1-10)

	A	B	C	D	E
1	<input type="radio"/>	<input type="radio"/>	<input type="radio"/>	<input type="radio"/>	<input type="radio"/>
2	<input type="radio"/>	<input type="radio"/>	<input type="radio"/>	<input type="radio"/>	<input type="radio"/>
3	<input type="radio"/>	<input type="radio"/>	<input type="radio"/>	<input type="radio"/>	<input type="radio"/>
4	<input type="radio"/>	<input type="radio"/>	<input type="radio"/>	<input type="radio"/>	<input type="radio"/>
5	<input type="radio"/>	<input type="radio"/>	<input type="radio"/>	<input type="radio"/>	<input type="radio"/>

	A	B	C	D	E
6	<input type="radio"/>	<input type="radio"/>	<input type="radio"/>	<input type="radio"/>	<input type="radio"/>
7	<input type="radio"/>	<input type="radio"/>	<input type="radio"/>	<input type="radio"/>	<input type="radio"/>
8	<input type="radio"/>	<input type="radio"/>	<input type="radio"/>	<input type="radio"/>	<input type="radio"/>
9	<input type="radio"/>	<input type="radio"/>	<input type="radio"/>	<input type="radio"/>	<input type="radio"/>
10	<input type="radio"/>	<input type="radio"/>	<input type="radio"/>	<input type="radio"/>	<input type="radio"/>

Answers (11-20)

	A	B	C	D	E
11	<input type="radio"/>	<input type="radio"/>	<input type="radio"/>	<input type="radio"/>	<input type="radio"/>
12	<input type="radio"/>	<input type="radio"/>	<input type="radio"/>	<input type="radio"/>	<input type="radio"/>
13	<input type="radio"/>	<input type="radio"/>	<input type="radio"/>	<input type="radio"/>	<input type="radio"/>
14	<input type="radio"/>	<input type="radio"/>	<input type="radio"/>	<input type="radio"/>	<input type="radio"/>
15	<input type="radio"/>	<input type="radio"/>	<input type="radio"/>	<input type="radio"/>	<input type="radio"/>


	A	B	C	D	E
16	<input type="radio"/>	<input type="radio"/>	<input type="radio"/>	<input type="radio"/>	<input type="radio"/>
17	<input type="radio"/>	<input type="radio"/>	<input type="radio"/>	<input type="radio"/>	<input type="radio"/>
18	<input type="radio"/>	<input type="radio"/>	<input type="radio"/>	<input type="radio"/>	<input type="radio"/>
19	<input type="radio"/>	<input type="radio"/>	<input type="radio"/>	<input type="radio"/>	<input type="radio"/>
20	<input type="radio"/>	<input type="radio"/>	<input type="radio"/>	<input type="radio"/>	<input type="radio"/>

Answers (21-30)

	A	B	C	D	E
21	<input type="radio"/>	<input type="radio"/>	<input type="radio"/>	<input type="radio"/>	<input type="radio"/>
22	<input type="radio"/>	<input type="radio"/>	<input type="radio"/>	<input type="radio"/>	<input type="radio"/>
23	<input type="radio"/>	<input type="radio"/>	<input type="radio"/>	<input type="radio"/>	<input type="radio"/>
24	<input type="radio"/>	<input type="radio"/>	<input type="radio"/>	<input type="radio"/>	<input type="radio"/>
25	<input type="radio"/>	<input type="radio"/>	<input type="radio"/>	<input type="radio"/>	<input type="radio"/>

	A	B	C	D	E
26	<input type="radio"/>	<input type="radio"/>	<input type="radio"/>	<input type="radio"/>	<input type="radio"/>
27	<input type="radio"/>	<input type="radio"/>	<input type="radio"/>	<input type="radio"/>	<input type="radio"/>
28	<input type="radio"/>	<input type="radio"/>	<input type="radio"/>	<input type="radio"/>	<input type="radio"/>
29	<input type="radio"/>	<input type="radio"/>	<input type="radio"/>	<input type="radio"/>	<input type="radio"/>
30	<input type="radio"/>	<input type="radio"/>	<input type="radio"/>	<input type="radio"/>	<input type="radio"/>


## ◇ Question 1 of 4 [CO1] [1 mark]

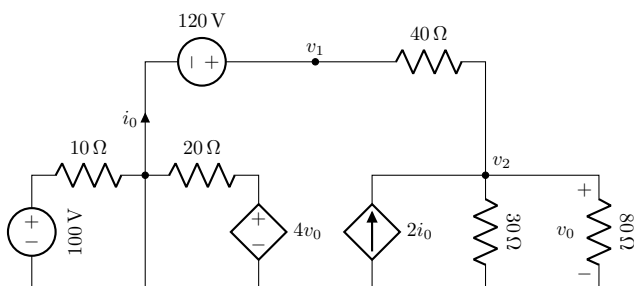

How many nodes are in this circuit?

- (A) 4 (B) 7 (C) 5 (D) 6 (E) 3


## ◇ Question 2 of 4 [CO3] [5 marks]

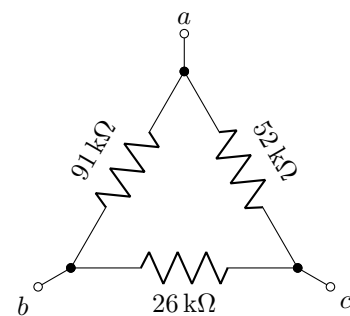

Which of the following statements is true?

- (A)  $R_{ab} = 91 \text{ k}\Omega$ ,  $R_{bc} = 26 \text{ k}\Omega$ ,  $R_{ca} = 52 \text{ k}\Omega$   
 (B)  $R_{ab} = 42 \text{ }\Omega$ ,  $R_{bc} = 22 \text{ }\Omega$ ,  $R_{ca} = 36 \text{ }\Omega$   
 (C)  $R_{ab} = 42 \text{ k}\Omega$ ,  $R_{bc} = 22 \text{ k}\Omega$ ,  $R_{ca} = 36 \text{ k}\Omega$   
 (D)  $R_{ab} = R_{bc} = R_{ca} = 14.56 \text{ k}\Omega$   
 (E) None of the above


◇ Question 3 of 4 [CO3] [2 marks]

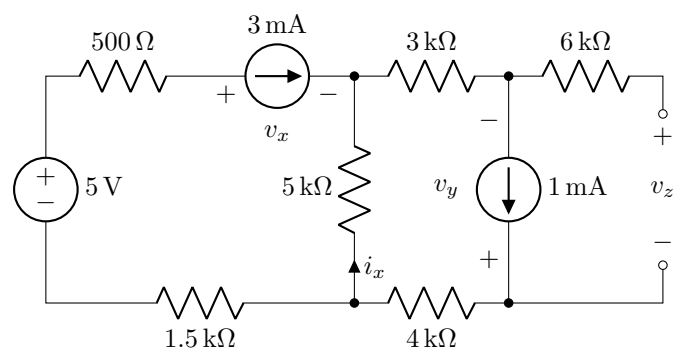

- ☒ A a
- ☐ B c
- ☐ C b

◇ Question 4 of 4 [CO1] [2 marks]

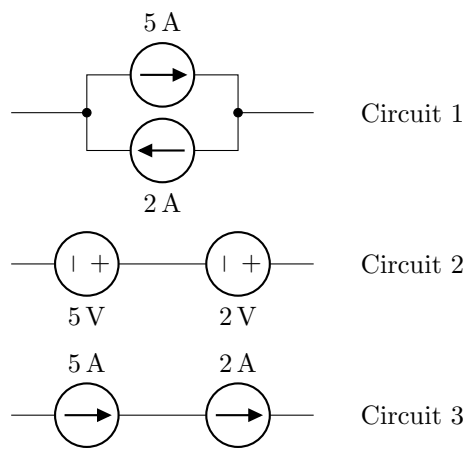Which of the following circuits is/are impossible (violates Kirchhoff's laws)?



- ☒ A Circuit 1
- ☐ B Circuit 1 & 3
- ☐ C Circuit 3
- ☐ D Circuit 2
- ☐ E None of the above

ID:

Name:

**Brac University**

Semester: Fall 2023

Course Code: CSE250

Circuits And Electronics

Section: 18

Set

C

Assessment: *Class Assignment 1*

Duration: 1 hour 20 minutes

Date: September 28, 2023

Full Marks: 10

- ✓ No washroom breaks. Phones must be turned off. Using/carrying any notes during the exam is not allowed.
- ✓ All **4 questions** are compulsory. Marks allotted for each question are mentioned beside each question.
- ✓ Write your answers inside the indicated boxes (where applicable). If you run out of room, continue on the back page.
- ✓ Symbols have their usual meanings.

Student ID

1	<input type="radio"/>	<input type="radio"/>	<input type="radio"/>	<input type="radio"/>	<input type="radio"/>	<input type="radio"/>	<input type="radio"/>
2	<input type="radio"/>	<input type="radio"/>	<input type="radio"/>	<input type="radio"/>	<input type="radio"/>	<input type="radio"/>	<input type="radio"/>
3	<input type="radio"/>	<input type="radio"/>	<input type="radio"/>	<input type="radio"/>	<input type="radio"/>	<input type="radio"/>	<input type="radio"/>
4	<input type="radio"/>	<input type="radio"/>	<input type="radio"/>	<input type="radio"/>	<input type="radio"/>	<input type="radio"/>	<input type="radio"/>
5	<input type="radio"/>	<input type="radio"/>	<input type="radio"/>	<input type="radio"/>	<input type="radio"/>	<input type="radio"/>	<input type="radio"/>
6	<input type="radio"/>	<input type="radio"/>	<input type="radio"/>	<input type="radio"/>	<input type="radio"/>	<input type="radio"/>	<input type="radio"/>
7	<input type="radio"/>	<input type="radio"/>	<input type="radio"/>	<input type="radio"/>	<input type="radio"/>	<input type="radio"/>	<input type="radio"/>
8	<input type="radio"/>	<input type="radio"/>	<input type="radio"/>	<input type="radio"/>	<input type="radio"/>	<input type="radio"/>	<input type="radio"/>
9	<input type="radio"/>	<input type="radio"/>	<input type="radio"/>	<input type="radio"/>	<input type="radio"/>	<input type="radio"/>	<input type="radio"/>
0	<input type="radio"/>	<input type="radio"/>	<input type="radio"/>	<input type="radio"/>	<input type="radio"/>	<input type="radio"/>	<input type="radio"/>

Set Identifier

§ ☒ ☒ ☒ ☒ ☒ ☒ ☐ ☐

Answers (1-10)

	A	B	C	D	E
1	<input type="radio"/>	<input type="radio"/>	<input type="radio"/>	<input type="radio"/>	<input type="radio"/>
2	<input type="radio"/>	<input type="radio"/>	<input type="radio"/>	<input type="radio"/>	<input type="radio"/>
3	<input type="radio"/>	<input type="radio"/>	<input type="radio"/>	<input type="radio"/>	<input type="radio"/>
4	<input type="radio"/>	<input type="radio"/>	<input type="radio"/>	<input type="radio"/>	<input type="radio"/>
5	<input type="radio"/>	<input type="radio"/>	<input type="radio"/>	<input type="radio"/>	<input type="radio"/>

	A	B	C	D	E
6	<input type="radio"/>	<input type="radio"/>	<input type="radio"/>	<input type="radio"/>	<input type="radio"/>
7	<input type="radio"/>	<input type="radio"/>	<input type="radio"/>	<input type="radio"/>	<input type="radio"/>
8	<input type="radio"/>	<input type="radio"/>	<input type="radio"/>	<input type="radio"/>	<input type="radio"/>
9	<input type="radio"/>	<input type="radio"/>	<input type="radio"/>	<input type="radio"/>	<input type="radio"/>
10	<input type="radio"/>	<input type="radio"/>	<input type="radio"/>	<input type="radio"/>	<input type="radio"/>

Answers (11-20)

	A	B	C	D	E
11	<input type="radio"/>	<input type="radio"/>	<input type="radio"/>	<input type="radio"/>	<input type="radio"/>
12	<input type="radio"/>	<input type="radio"/>	<input type="radio"/>	<input type="radio"/>	<input type="radio"/>
13	<input type="radio"/>	<input type="radio"/>	<input type="radio"/>	<input type="radio"/>	<input type="radio"/>
14	<input type="radio"/>	<input type="radio"/>	<input type="radio"/>	<input type="radio"/>	<input type="radio"/>
15	<input type="radio"/>	<input type="radio"/>	<input type="radio"/>	<input type="radio"/>	<input type="radio"/>


	A	B	C	D	E
16	<input type="radio"/>	<input type="radio"/>	<input type="radio"/>	<input type="radio"/>	<input type="radio"/>
17	<input type="radio"/>	<input type="radio"/>	<input type="radio"/>	<input type="radio"/>	<input type="radio"/>
18	<input type="radio"/>	<input type="radio"/>	<input type="radio"/>	<input type="radio"/>	<input type="radio"/>
19	<input type="radio"/>	<input type="radio"/>	<input type="radio"/>	<input type="radio"/>	<input type="radio"/>
20	<input type="radio"/>	<input type="radio"/>	<input type="radio"/>	<input type="radio"/>	<input type="radio"/>

Answers (21-30)

	A	B	C	D	E
21	<input type="radio"/>	<input type="radio"/>	<input type="radio"/>	<input type="radio"/>	<input type="radio"/>
22	<input type="radio"/>	<input type="radio"/>	<input type="radio"/>	<input type="radio"/>	<input type="radio"/>
23	<input type="radio"/>	<input type="radio"/>	<input type="radio"/>	<input type="radio"/>	<input type="radio"/>
24	<input type="radio"/>	<input type="radio"/>	<input type="radio"/>	<input type="radio"/>	<input type="radio"/>
25	<input type="radio"/>	<input type="radio"/>	<input type="radio"/>	<input type="radio"/>	<input type="radio"/>

	A	B	C	D	E
26	<input type="radio"/>	<input type="radio"/>	<input type="radio"/>	<input type="radio"/>	<input type="radio"/>
27	<input type="radio"/>	<input type="radio"/>	<input type="radio"/>	<input type="radio"/>	<input type="radio"/>
28	<input type="radio"/>	<input type="radio"/>	<input type="radio"/>	<input type="radio"/>	<input type="radio"/>
29	<input type="radio"/>	<input type="radio"/>	<input type="radio"/>	<input type="radio"/>	<input type="radio"/>
30	<input type="radio"/>	<input type="radio"/>	<input type="radio"/>	<input type="radio"/>	<input type="radio"/>

## ◇ Question 1 of 4 [CO3] [5 marks]

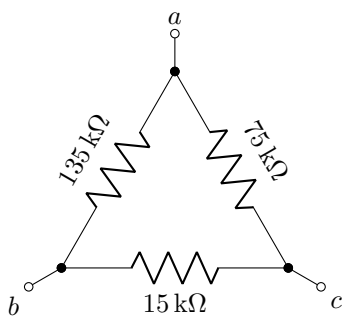


Which of the following statements is true?


- (A)  $R_{ab} = 54 \Omega$ ,  $R_{bc} = 14 \Omega$ ,  $R_{ca} = 50 \Omega$
- (B)  $R_{ab} = R_{bc} = R_{ca} = 11.441 \text{ k}\Omega$
- (C)  $R_{ab} = 54 \text{ k}\Omega$ ,  $R_{bc} = 14 \text{ k}\Omega$ ,  $R_{ca} = 50 \text{ k}\Omega$**
- (D)  $R_{ab} = 135 \text{ k}\Omega$ ,  $R_{bc} = 15 \text{ k}\Omega$ ,  $R_{ca} = 75 \text{ k}\Omega$
- (E) None of the above

## ◇ Question 2 of 4 [CO1] [2 marks]


Which of the following circuits is/are impossible (violates Kirchhoff's laws)?

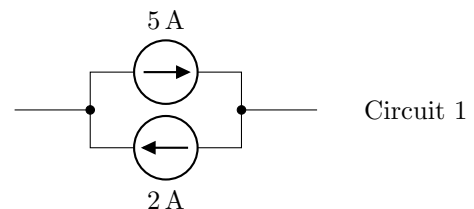

Circuit 1

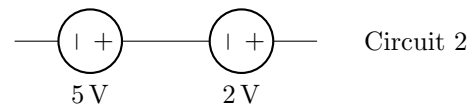


Circuit 2

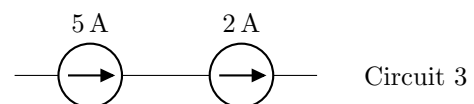

Circuit 3

- (A) Circuit 3      (B) Circuit 1 & 3      (C) Circuit 2
- (D) Circuit 1**      (E) None of the above


◇ Question 3 of 4 [CO3] [2 marks]

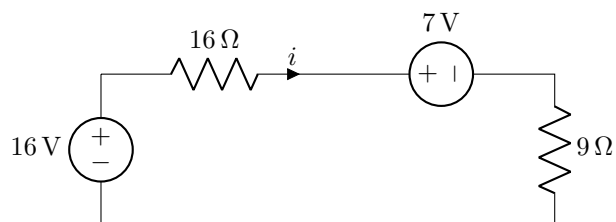

What's the relation between  $v_1$ ,  $v_2$  and  $i$ ?

- ☐ (A)  $-16 + 16i - 7 + 9i = 0$   
☐ (B)  $-16 - 16i - 7 + 9i = 0$   
☒ (C)  $-16 + 16i + 7 + 9i = 0$   
☐ (D)  $-16 - 16i + 7 + 9i = 0$   
☐ (E) None of the above

◇ Question 4 of 4 [CO1] [1 mark]

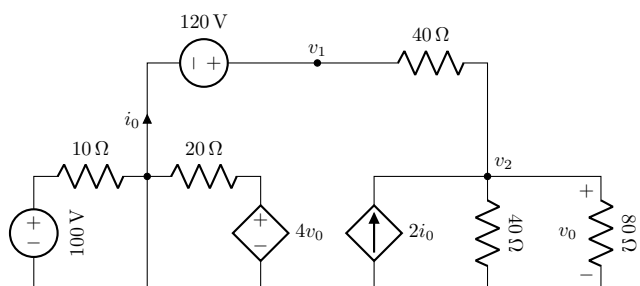

How many nodes are in this circuit?

- ☐ (A) 3   ☐ (B) 7   ☐ (C) 4   ☐ (D) 6   ☒ (E) 5

ID:

Name:

**Brac University**

Semester: Fall 2023

Course Code: CSE250

Circuits And Electronics

Section: 18

Set

D

Assessment: *Class Assignment 1*

Duration: 1 hour 20 minutes

Date: September 28, 2023

Full Marks: 10

- ✓ No washroom breaks. Phones must be turned off. Using/carrying any notes during the exam is not allowed.
- ✓ All **4 questions** are compulsory. Marks allotted for each question are mentioned beside each question.
- ✓ Write your answers inside the indicated boxes (where applicable). If you run out of room, continue on the back page.
- ✓ Symbols have their usual meanings.

Student ID

1	<input type="radio"/>	<input type="radio"/>	<input type="radio"/>	<input type="radio"/>	<input type="radio"/>	<input type="radio"/>	<input type="radio"/>
2	<input type="radio"/>	<input type="radio"/>	<input type="radio"/>	<input type="radio"/>	<input type="radio"/>	<input type="radio"/>	<input type="radio"/>
3	<input type="radio"/>	<input type="radio"/>	<input type="radio"/>	<input type="radio"/>	<input type="radio"/>	<input type="radio"/>	<input type="radio"/>
4	<input type="radio"/>	<input type="radio"/>	<input type="radio"/>	<input type="radio"/>	<input type="radio"/>	<input type="radio"/>	<input type="radio"/>
5	<input type="radio"/>	<input type="radio"/>	<input type="radio"/>	<input type="radio"/>	<input type="radio"/>	<input type="radio"/>	<input type="radio"/>
6	<input type="radio"/>	<input type="radio"/>	<input type="radio"/>	<input type="radio"/>	<input type="radio"/>	<input type="radio"/>	<input type="radio"/>
7	<input type="radio"/>	<input type="radio"/>	<input type="radio"/>	<input type="radio"/>	<input type="radio"/>	<input type="radio"/>	<input type="radio"/>
8	<input type="radio"/>	<input type="radio"/>	<input type="radio"/>	<input type="radio"/>	<input type="radio"/>	<input type="radio"/>	<input type="radio"/>
9	<input type="radio"/>	<input type="radio"/>	<input type="radio"/>	<input type="radio"/>	<input type="radio"/>	<input type="radio"/>	<input type="radio"/>
0	<input type="radio"/>	<input type="radio"/>	<input type="radio"/>	<input type="radio"/>	<input type="radio"/>	<input type="radio"/>	<input type="radio"/>

Set Identifier

§ ☒ ☒ ☒ ☒ ☒ ☐ ☒ ☒

Answers (1-10)

	A	B	C	D	E
1	<input type="radio"/>	<input type="radio"/>	<input type="radio"/>	<input type="radio"/>	<input type="radio"/>
2	<input type="radio"/>	<input type="radio"/>	<input type="radio"/>	<input type="radio"/>	<input type="radio"/>
3	<input type="radio"/>	<input type="radio"/>	<input type="radio"/>	<input type="radio"/>	<input type="radio"/>
4	<input type="radio"/>	<input type="radio"/>	<input type="radio"/>	<input type="radio"/>	<input type="radio"/>
5	<input type="radio"/>	<input type="radio"/>	<input type="radio"/>	<input type="radio"/>	<input type="radio"/>

	A	B	C	D	E
6	<input type="radio"/>	<input type="radio"/>	<input type="radio"/>	<input type="radio"/>	<input type="radio"/>
7	<input type="radio"/>	<input type="radio"/>	<input type="radio"/>	<input type="radio"/>	<input type="radio"/>
8	<input type="radio"/>	<input type="radio"/>	<input type="radio"/>	<input type="radio"/>	<input type="radio"/>
9	<input type="radio"/>	<input type="radio"/>	<input type="radio"/>	<input type="radio"/>	<input type="radio"/>
10	<input type="radio"/>	<input type="radio"/>	<input type="radio"/>	<input type="radio"/>	<input type="radio"/>

Answers (11-20)

	A	B	C	D	E
11	<input type="radio"/>	<input type="radio"/>	<input type="radio"/>	<input type="radio"/>	<input type="radio"/>
12	<input type="radio"/>	<input type="radio"/>	<input type="radio"/>	<input type="radio"/>	<input type="radio"/>
13	<input type="radio"/>	<input type="radio"/>	<input type="radio"/>	<input type="radio"/>	<input type="radio"/>
14	<input type="radio"/>	<input type="radio"/>	<input type="radio"/>	<input type="radio"/>	<input type="radio"/>
15	<input type="radio"/>	<input type="radio"/>	<input type="radio"/>	<input type="radio"/>	<input type="radio"/>


	A	B	C	D	E
16	<input type="radio"/>	<input type="radio"/>	<input type="radio"/>	<input type="radio"/>	<input type="radio"/>
17	<input type="radio"/>	<input type="radio"/>	<input type="radio"/>	<input type="radio"/>	<input type="radio"/>
18	<input type="radio"/>	<input type="radio"/>	<input type="radio"/>	<input type="radio"/>	<input type="radio"/>
19	<input type="radio"/>	<input type="radio"/>	<input type="radio"/>	<input type="radio"/>	<input type="radio"/>
20	<input type="radio"/>	<input type="radio"/>	<input type="radio"/>	<input type="radio"/>	<input type="radio"/>

Answers (21-30)

	A	B	C	D	E
21	<input type="radio"/>	<input type="radio"/>	<input type="radio"/>	<input type="radio"/>	<input type="radio"/>
22	<input type="radio"/>	<input type="radio"/>	<input type="radio"/>	<input type="radio"/>	<input type="radio"/>
23	<input type="radio"/>	<input type="radio"/>	<input type="radio"/>	<input type="radio"/>	<input type="radio"/>
24	<input type="radio"/>	<input type="radio"/>	<input type="radio"/>	<input type="radio"/>	<input type="radio"/>
25	<input type="radio"/>	<input type="radio"/>	<input type="radio"/>	<input type="radio"/>	<input type="radio"/>

	A	B	C	D	E
26	<input type="radio"/>	<input type="radio"/>	<input type="radio"/>	<input type="radio"/>	<input type="radio"/>
27	<input type="radio"/>	<input type="radio"/>	<input type="radio"/>	<input type="radio"/>	<input type="radio"/>
28	<input type="radio"/>	<input type="radio"/>	<input type="radio"/>	<input type="radio"/>	<input type="radio"/>
29	<input type="radio"/>	<input type="radio"/>	<input type="radio"/>	<input type="radio"/>	<input type="radio"/>
30	<input type="radio"/>	<input type="radio"/>	<input type="radio"/>	<input type="radio"/>	<input type="radio"/>


## ◇ Question 1 of 4 [CO1] [1 mark]

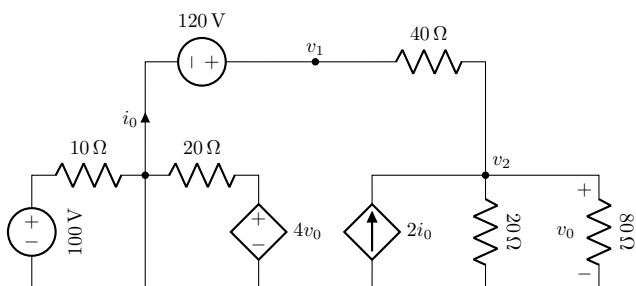

How many nodes are in this circuit?

- (A) 7 (B) 3 (C) 4 (D) 6 (E) 5




## ◇ Question 2 of 4 [CO3] [2 marks]

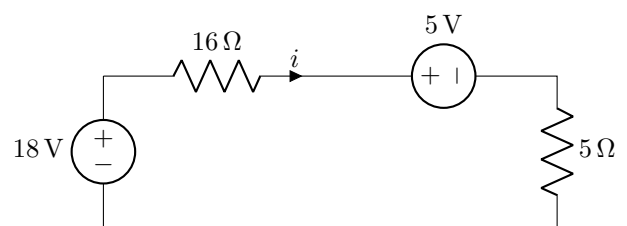What's the relation between  $v_1$ ,  $v_2$  and  $i$ ?

- (A)  $-18 + 16i - 5 + 5i = 0$   
 (B)  $-18 + 16i + 5 + 5i = 0$   
 (C)  $-18 - 16i + 5 + 5i = 0$   
 (D)  $-18 - 16i - 5 + 5i = 0$   
 (E) None of the above

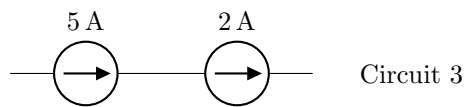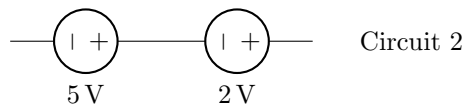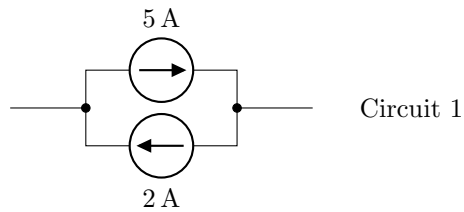
### ◇ Question 3 of 4 [CO1] [2 marks]

Which of the following circuits is/are impossible (violates Kirchhoff's laws)?



- ☒ **A** Circuit 1   
 ☐ B Circuit 1 & 3   
 ☐ C Circuit 3  
☐ D Circuit 2   
 ☐ E None of the above

### ◇ Question 4 of 4 [CO3] [5 marks]

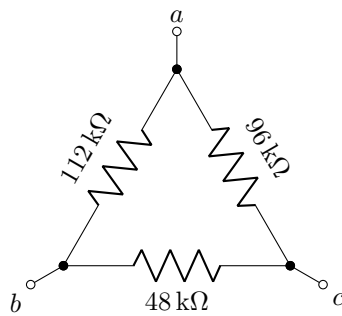

Which of the following statements is true?

- ☐ A  $R_{ab} = 63 \Omega, R_{bc} = 39 \Omega, R_{ca} = 60 \Omega$   
☐ B  $R_{ab} = 112 \text{ k}\Omega, R_{bc} = 48 \text{ k}\Omega, R_{ca} = 96 \text{ k}\Omega$   
☒ **C**  $R_{ab} = 63 \text{ k}\Omega, R_{bc} = 39 \text{ k}\Omega, R_{ca} = 60 \text{ k}\Omega$   
☐ D  $R_{ab} = R_{bc} = R_{ca} = 24.889 \text{ k}\Omega$   
☐ E None of the above



ID:

Name:

**Brac University**

Semester: Fall 2023

Course Code: CSE250

Circuits And Electronics

Section: 18

Set

E

Assessment: *Class Assignment 1*

Duration: 1 hour 20 minutes

Date: September 28, 2023

Full Marks: 10

- ✓ No washroom breaks. Phones must be turned off. Using/carrying any notes during the exam is not allowed.
- ✓ All **4 questions** are compulsory. Marks allotted for each question are mentioned beside each question.
- ✓ Write your answers inside the indicated boxes (where applicable). If you run out of room, continue on the back page.
- ✓ Symbols have their usual meanings.

Student ID

       
1 ☐ ☐ ☐ ☐ ☐ ☐ ☐ ☐2 ☐ ☐ ☐ ☐ ☐ ☐ ☐ ☐3 ☐ ☐ ☐ ☐ ☐ ☐ ☐ ☐4 ☐ ☐ ☐ ☐ ☐ ☐ ☐ ☐5 ☐ ☐ ☐ ☐ ☐ ☐ ☐ ☐6 ☐ ☐ ☐ ☐ ☐ ☐ ☐ ☐7 ☐ ☐ ☐ ☐ ☐ ☐ ☐ ☐8 ☐ ☐ ☐ ☐ ☐ ☐ ☐ ☐9 ☐ ☐ ☐ ☐ ☐ ☐ ☐ ☐0 ☐ ☐ ☐ ☐ ☐ ☐ ☐ ☐

Set Identifier

§ ☒ ☒ ☒ ☒ ☒ ☐ ☒ ☐

Answers (1-10)

A B C D E

1 ☐ ☐ ☐ ☐ ☐2 ☐ ☐ ☐ ☐ ☐3 ☐ ☐ ☐ ☐ ☐4 ☐ ☐ ☐ ☐ ☐5 ☐ ☐ ☐ ☐ ☐

A B C D E

6 ☐ ☐ ☐ ☐ ☐7 ☐ ☐ ☐ ☐ ☐8 ☐ ☐ ☐ ☐ ☐9 ☐ ☐ ☐ ☐ ☐10 ☐ ☐ ☐ ☐ ☐

Answers (11-20)

A B C D E

11 ☐ ☐ ☐ ☐ ☐12 ☐ ☐ ☐ ☐ ☐13 ☐ ☐ ☐ ☐ ☐14 ☐ ☐ ☐ ☐ ☐15 ☐ ☐ ☐ ☐ ☐

A B C D E

16 ☐ ☐ ☐ ☐ ☐17 ☐ ☐ ☐ ☐ ☐18 ☐ ☐ ☐ ☐ ☐19 ☐ ☐ ☐ ☐ ☐20 ☐ ☐ ☐ ☐ ☐

Answers (21-30)


A B C D E

21 ☐ ☐ ☐ ☐ ☐22 ☐ ☐ ☐ ☐ ☐23 ☐ ☐ ☐ ☐ ☐24 ☐ ☐ ☐ ☐ ☐25 ☐ ☐ ☐ ☐ ☐

A B C D E

26 ☐ ☐ ☐ ☐ ☐27 ☐ ☐ ☐ ☐ ☐28 ☐ ☐ ☐ ☐ ☐29 ☐ ☐ ☐ ☐ ☐30 ☐ ☐ ☐ ☐ ☐


## ◇ Question 1 of 4 [CO3] [2 marks]

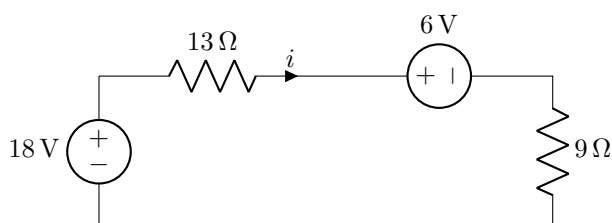What's the relation between  $v_1$ ,  $v_2$  and  $i$ ?


- (A)  $-18 + 13i - 6 + 9i = 0$
- (B)  $-18 - 13i - 6 + 9i = 0$
- (C)  $-18 + 13i + 6 + 9i = 0$
- (D)  $-18 - 13i + 6 + 9i = 0$
- (E) None of the above

## ◇ Question 2 of 4 [CO1] [2 marks]


Which of the following circuits is/are impossible (violates Kirchhoff's laws)?

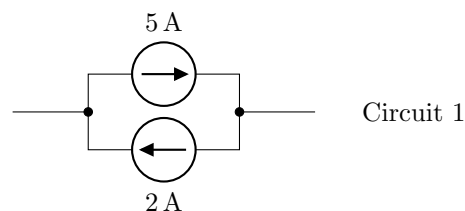

Circuit 1

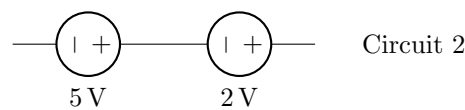


Circuit 2

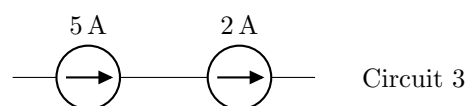

Circuit 3

- (A) Circuit 3      (B) Circuit 2      (C) Circuit 1 & 3
- (D) **Circuit 1**      (E) None of the above


◇ Question 3 of 4 [CO3] [5 marks]

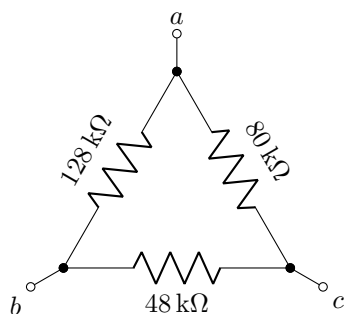

Which of the following statements is true?

- (A)  $R_{ab} = 64 \text{ k}\Omega$ ,  $R_{bc} = 39 \text{ k}\Omega$ ,  $R_{ca} = 55 \text{ k}\Omega$
- (B)  $R_{ab} = R_{bc} = R_{ca} = 24.304 \text{ k}\Omega$
- (C)  $R_{ab} = 128 \text{ k}\Omega$ ,  $R_{bc} = 48 \text{ k}\Omega$ ,  $R_{ca} = 80 \text{ k}\Omega$
- (D)  $R_{ab} = 64 \text{ }\Omega$ ,  $R_{bc} = 39 \text{ }\Omega$ ,  $R_{ca} = 55 \text{ }\Omega$
- (E) None of the above

◇ Question 4 of 4 [CO1] [1 mark]

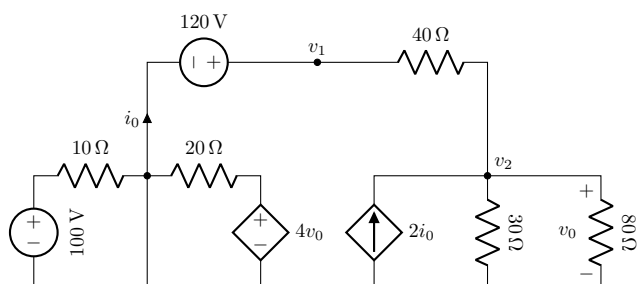

How many nodes are in this circuit?

- (A) 3 (B) 7 (C) 5 (D) 6 (E) 4

ID:

Name:

**Brac University**

Semester: Fall 2023

Course Code: CSE250

Circuits And Electronics

Section: 18

Set

F

Assessment: *Class Assignment 1*

Duration: 1 hour 20 minutes

Date: September 28, 2023




Full Marks: 10

- ✓ No washroom breaks. Phones must be turned off. Using/carrying any notes during the exam is not allowed.
- ✓ All **4 questions** are compulsory. Marks allotted for each question are mentioned beside each question.
- ✓ Write your answers inside the indicated boxes (where applicable). If you run out of room, continue on the back page.
- ✓ Symbols have their usual meanings.

<div style="border: 1px solid black; padding: 5px; margin-bottom: 10px;">             Student ID  <div style="display: flex; justify-content: space-around; height: 20px;"> <div style="width: 20px; height: 20px; border: 1px solid black;"></div> <div style="width: 20px; height: 20px; border: 1px solid black;"></div> <div style="width: 20px; height: 20px; border: 1px solid black;"></div> <div style="width: 20px; height: 20px; border: 1px solid black;"></div> <div style="width: 20px; height: 20px; border: 1px solid black;"></div> <div style="width: 20px; height: 20px; border: 1px solid black;"></div> <div style="width: 20px; height: 20px; border: 1px solid black;"></div> </div> </div> <div style="display: flex; flex-direction: column;"> <div style="margin-bottom: 10px;">             1 <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> </div> <div style="margin-bottom: 10px;">             2 <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> </div> <div style="margin-bottom: 10px;">             3 <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> </div> <div style="margin-bottom: 10px;">             4 <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> </div> <div style="margin-bottom: 10px;">             5 <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> </div> <div style="margin-bottom: 10px;">             6 <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> </div> <div style="margin-bottom: 10px;">             7 <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> </div> <div style="margin-bottom: 10px;">             8 <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> </div> <div style="margin-bottom: 10px;">             9 <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> </div> <div style="margin-bottom: 10px;">             0 <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> </div> </div> <div style="margin-top: 10px;">             Set Identifier              § <input checked="" type="radio"/> <input checked="" type="radio"/> <input checked="" type="radio"/> <input checked="" type="radio"/> <input checked="" type="radio"/> <input type="radio"/> <input type="radio"/> <input checked="" type="radio"/> </div>	<div style="border: 1px solid black; padding: 5px; margin-bottom: 10px;">             Answers (1-10)         </div> <div style="display: flex; flex-direction: column;"> <div style="margin-bottom: 10px;">             A B C D E              1 <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> </div> <div style="margin-bottom: 10px;">             2 <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> </div> <div style="margin-bottom: 10px;">             3 <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> </div> <div style="margin-bottom: 10px;">             4 <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> </div> <div style="margin-bottom: 10px;">             5 <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> </div> </div> <div style="margin-top: 10px;">             A B C D E              6 <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> </div> <div style="margin-bottom: 10px;">             7 <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> </div> <div style="margin-bottom: 10px;">             8 <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> </div> <div style="margin-bottom: 10px;">             9 <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> </div> <div style="margin-bottom: 10px;">             10 <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> </div>	<div style="border: 1px solid black; padding: 5px; margin-bottom: 10px;">             Answers (11-20)         </div> <div style="display: flex; flex-direction: column;"> <div style="margin-bottom: 10px;">             A B C D E              11 <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> </div> <div style="margin-bottom: 10px;">             12 <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> </div> <div style="margin-bottom: 10px;">             13 <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> </div> <div style="margin-bottom: 10px;">             14 <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> </div> <div style="margin-bottom: 10px;">             15 <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> </div> </div> <div style="margin-top: 10px;">             A B C D E              16 <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> </div> <div style="margin-bottom: 10px;">             17 <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> </div> <div style="margin-bottom: 10px;">             18 <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> </div> <div style="margin-bottom: 10px;">             19 <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> </div> <div style="margin-bottom: 10px;">             20 <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> </div>	<div style="border: 1px solid black; padding: 5px; margin-bottom: 10px;">             Answers (21-30)         </div> <div style="display: flex; flex-direction: column;"> <div style="margin-bottom: 10px;">             A B C D E              21 <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> </div> <div style="margin-bottom: 10px;">             22 <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> </div> <div style="margin-bottom: 10px;">             23 <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> </div> <div style="margin-bottom: 10px;">             24 <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> </div> <div style="margin-bottom: 10px;">             25 <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> </div> </div> <div style="margin-top: 10px;">             A B C D E              26 <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> </div> <div style="margin-bottom: 10px;">             27 <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> </div> <div style="margin-bottom: 10px;">             28 <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> </div> <div style="margin-bottom: 10px;">             29 <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> </div> <div style="margin-bottom: 10px;">             30 <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> </div>
--	---	---	---

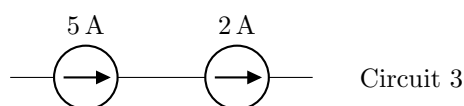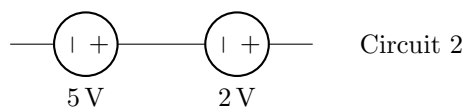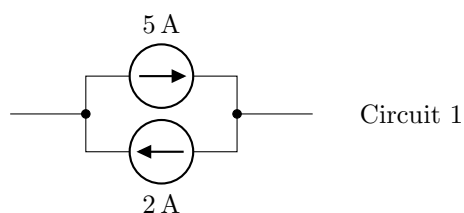
### ◇ Question 1 of 4 [CO1] [2 marks]

Which of the following circuits is/are impossible (violates Kirchhoff's laws)?



- ☐ (A) Circuit 2    
 ☒ (B) **Circuit 1**    
 ☐ (C) Circuit 3  
☐ (D) Circuit 1 & 3    
☐ (E) None of the above


### ◇ Question 2 of 4 [CO3] [2 marks]

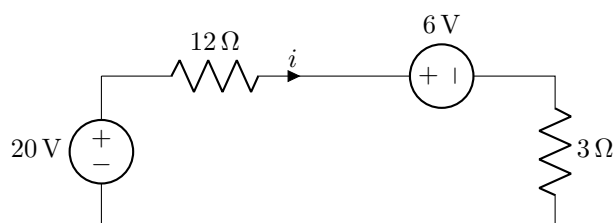

What's the relation between  $v_1$ ,  $v_2$  and  $i$ ?

- ☐ (A)  $-20 - 12i - 6 + 3i = 0$   
☐ (B)  $-20 + 12i - 6 + 3i = 0$   
☒ (C)  $-20 + 12i + 6 + 3i = 0$   
☐ (D)  $-20 - 12i + 6 + 3i = 0$   
☐ (E) None of the above


◇ Question 3 of 4 [CO1] [1 mark]

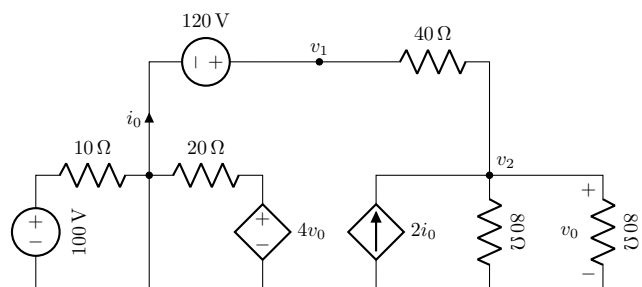

How many nodes are in this circuit?

- (A) 7 (B) 5 (C) 4 (D) 6 (E) 3

◇ Question 4 of 4 [CO3] [5 marks]

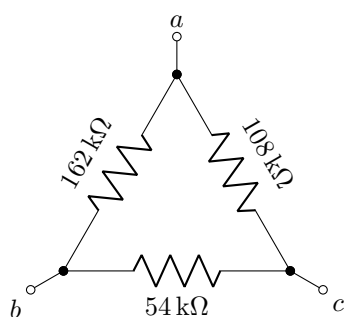

Which of the following statements is true?

- (A)  $R_{ab} = 162 \text{ k}\Omega$ ,  $R_{bc} = 54 \text{ k}\Omega$ ,  $R_{ca} = 108 \text{ k}\Omega$   
 (B)  $R_{ab} = 81 \text{ k}\Omega$ ,  $R_{bc} = 45 \text{ k}\Omega$ ,  $R_{ca} = 72 \text{ k}\Omega$   
 (C)  $R_{ab} = 81 \text{ }\Omega$ ,  $R_{bc} = 45 \text{ }\Omega$ ,  $R_{ca} = 72 \text{ }\Omega$   
 (D)  $R_{ab} = R_{bc} = R_{ca} = 29.455 \text{ k}\Omega$   
 (E) None of the above

ID:

Name:

**Brac University**

Semester: Fall 2023

Course Code: CSE250

Circuits And Electronics

Section: 18

Set

G

Assessment: *Class Assignment 1*

Duration: 1 hour 20 minutes

Date: September 28, 2023

Full Marks: 10

- ✓ No washroom breaks. Phones must be turned off. Using/carrying any notes during the exam is not allowed.
- ✓ All **4 questions** are compulsory. Marks allotted for each question are mentioned beside each question.
- ✓ Write your answers inside the indicated boxes (where applicable). If you run out of room, continue on the back page.
- ✓ Symbols have their usual meanings.

Student ID

1	<input type="radio"/>	<input type="radio"/>	<input type="radio"/>	<input type="radio"/>	<input type="radio"/>	<input type="radio"/>	<input type="radio"/>
2	<input type="radio"/>	<input type="radio"/>	<input type="radio"/>	<input type="radio"/>	<input type="radio"/>	<input type="radio"/>	<input type="radio"/>
3	<input type="radio"/>	<input type="radio"/>	<input type="radio"/>	<input type="radio"/>	<input type="radio"/>	<input type="radio"/>	<input type="radio"/>
4	<input type="radio"/>	<input type="radio"/>	<input type="radio"/>	<input type="radio"/>	<input type="radio"/>	<input type="radio"/>	<input type="radio"/>
5	<input type="radio"/>	<input type="radio"/>	<input type="radio"/>	<input type="radio"/>	<input type="radio"/>	<input type="radio"/>	<input type="radio"/>
6	<input type="radio"/>	<input type="radio"/>	<input type="radio"/>	<input type="radio"/>	<input type="radio"/>	<input type="radio"/>	<input type="radio"/>
7	<input type="radio"/>	<input type="radio"/>	<input type="radio"/>	<input type="radio"/>	<input type="radio"/>	<input type="radio"/>	<input type="radio"/>
8	<input type="radio"/>	<input type="radio"/>	<input type="radio"/>	<input type="radio"/>	<input type="radio"/>	<input type="radio"/>	<input type="radio"/>
9	<input type="radio"/>	<input type="radio"/>	<input type="radio"/>	<input type="radio"/>	<input type="radio"/>	<input type="radio"/>	<input type="radio"/>
0	<input type="radio"/>	<input type="radio"/>	<input type="radio"/>	<input type="radio"/>	<input type="radio"/>	<input type="radio"/>	<input type="radio"/>

Set Identifier

§ ☒ ☒ ☒ ☒ ☒ ☐ ☐ ☐

Answers (1-10)

	A	B	C	D	E
1	<input type="radio"/>	<input type="radio"/>	<input type="radio"/>	<input type="radio"/>	<input type="radio"/>
2	<input type="radio"/>	<input type="radio"/>	<input type="radio"/>	<input type="radio"/>	<input type="radio"/>
3	<input type="radio"/>	<input type="radio"/>	<input type="radio"/>	<input type="radio"/>	<input type="radio"/>
4	<input type="radio"/>	<input type="radio"/>	<input type="radio"/>	<input type="radio"/>	<input type="radio"/>
5	<input type="radio"/>	<input type="radio"/>	<input type="radio"/>	<input type="radio"/>	<input type="radio"/>

	A	B	C	D	E
6	<input type="radio"/>	<input type="radio"/>	<input type="radio"/>	<input type="radio"/>	<input type="radio"/>
7	<input type="radio"/>	<input type="radio"/>	<input type="radio"/>	<input type="radio"/>	<input type="radio"/>
8	<input type="radio"/>	<input type="radio"/>	<input type="radio"/>	<input type="radio"/>	<input type="radio"/>
9	<input type="radio"/>	<input type="radio"/>	<input type="radio"/>	<input type="radio"/>	<input type="radio"/>
10	<input type="radio"/>	<input type="radio"/>	<input type="radio"/>	<input type="radio"/>	<input type="radio"/>

Answers (11-20)

	A	B	C	D	E
11	<input type="radio"/>	<input type="radio"/>	<input type="radio"/>	<input type="radio"/>	<input type="radio"/>
12	<input type="radio"/>	<input type="radio"/>	<input type="radio"/>	<input type="radio"/>	<input type="radio"/>
13	<input type="radio"/>	<input type="radio"/>	<input type="radio"/>	<input type="radio"/>	<input type="radio"/>
14	<input type="radio"/>	<input type="radio"/>	<input type="radio"/>	<input type="radio"/>	<input type="radio"/>
15	<input type="radio"/>	<input type="radio"/>	<input type="radio"/>	<input type="radio"/>	<input type="radio"/>


	A	B	C	D	E
16	<input type="radio"/>	<input type="radio"/>	<input type="radio"/>	<input type="radio"/>	<input type="radio"/>
17	<input type="radio"/>	<input type="radio"/>	<input type="radio"/>	<input type="radio"/>	<input type="radio"/>
18	<input type="radio"/>	<input type="radio"/>	<input type="radio"/>	<input type="radio"/>	<input type="radio"/>
19	<input type="radio"/>	<input type="radio"/>	<input type="radio"/>	<input type="radio"/>	<input type="radio"/>
20	<input type="radio"/>	<input type="radio"/>	<input type="radio"/>	<input type="radio"/>	<input type="radio"/>

Answers (21-30)

	A	B	C	D	E
21	<input type="radio"/>	<input type="radio"/>	<input type="radio"/>	<input type="radio"/>	<input type="radio"/>
22	<input type="radio"/>	<input type="radio"/>	<input type="radio"/>	<input type="radio"/>	<input type="radio"/>
23	<input type="radio"/>	<input type="radio"/>	<input type="radio"/>	<input type="radio"/>	<input type="radio"/>
24	<input type="radio"/>	<input type="radio"/>	<input type="radio"/>	<input type="radio"/>	<input type="radio"/>
25	<input type="radio"/>	<input type="radio"/>	<input type="radio"/>	<input type="radio"/>	<input type="radio"/>

	A	B	C	D	E
26	<input type="radio"/>	<input type="radio"/>	<input type="radio"/>	<input type="radio"/>	<input type="radio"/>
27	<input type="radio"/>	<input type="radio"/>	<input type="radio"/>	<input type="radio"/>	<input type="radio"/>
28	<input type="radio"/>	<input type="radio"/>	<input type="radio"/>	<input type="radio"/>	<input type="radio"/>
29	<input type="radio"/>	<input type="radio"/>	<input type="radio"/>	<input type="radio"/>	<input type="radio"/>
30	<input type="radio"/>	<input type="radio"/>	<input type="radio"/>	<input type="radio"/>	<input type="radio"/>

## ◇ Question 1 of 4 [CO1] [1 mark]

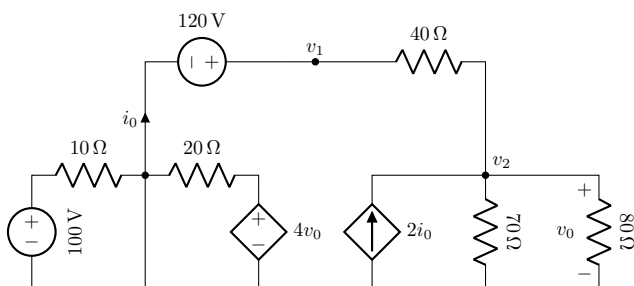


How many nodes are in this circuit?


- (A) 4 (B) 7 (C) 5 (D) 6 (E) 3

## ◇ Question 2 of 4 [CO1] [2 marks]


Which of the following circuits is/are impossible (violates Kirchhoff's laws)?

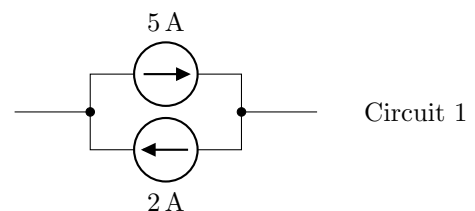

Circuit 1

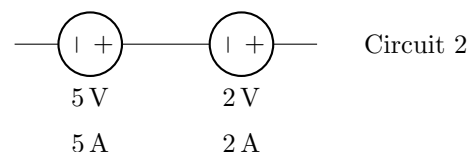


Circuit 2

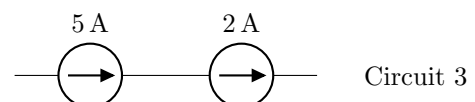

Circuit 3

- (A) Circuit 3 (B) Circuit 1 (C) Circuit 1 & 3  
(D) Circuit 2 (E) None of the above


◇ Question 3 of 4 [CO3] [5 marks]

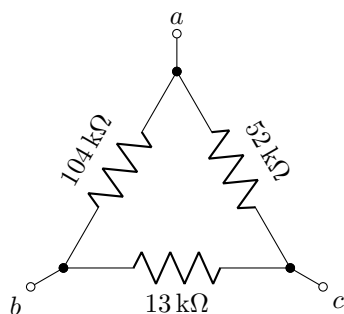

Which of the following statements is true?

- (A)  $R_{ab} = 40 \Omega$ ,  $R_{bc} = 12 \Omega$ ,  $R_{ca} = 36 \Omega$
- (B)  $R_{ab} = 40 \text{ k}\Omega$ ,  $R_{bc} = 12 \text{ k}\Omega$ ,  $R_{ca} = 36 \text{ k}\Omega$
- (C)  $R_{ab} = 104 \text{ k}\Omega$ ,  $R_{bc} = 13 \text{ k}\Omega$ ,  $R_{ca} = 52 \text{ k}\Omega$
- (D)  $R_{ab} = R_{bc} = R_{ca} = 9.455 \text{ k}\Omega$
- (E) None of the above

◇ Question 4 of 4 [CO3] [2 marks]

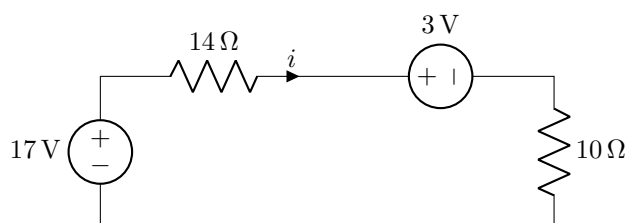

What's the relation between  $v_1$ ,  $v_2$  and  $i$ ?

- (A)  $-17 - 14i - 3 + 10i = 0$
- (B)  $-17 + 14i + 3 + 10i = 0$
- (C)  $-17 - 14i + 3 + 10i = 0$
- (D)  $-17 + 14i - 3 + 10i = 0$
- (E) None of the above

ID:

Name:

**Brac University**

Semester: Fall 2023

Course Code: CSE250

Circuits And Electronics

Section: 18

Set

H

Assessment: *Class Assignment 1*

Duration: 1 hour 20 minutes

Date: September 28, 2023

Full Marks: 10

- ✓ No washroom breaks. Phones must be turned off. Using/carrying any notes during the exam is not allowed.
- ✓ All **4 questions** are compulsory. Marks allotted for each question are mentioned beside each question.
- ✓ Write your answers inside the indicated boxes (where applicable). If you run out of room, continue on the back page.
- ✓ Symbols have their usual meanings.

Student ID

1	<input type="radio"/>	<input type="radio"/>	<input type="radio"/>	<input type="radio"/>	<input type="radio"/>	<input type="radio"/>	<input type="radio"/>
2	<input type="radio"/>	<input type="radio"/>	<input type="radio"/>	<input type="radio"/>	<input type="radio"/>	<input type="radio"/>	<input type="radio"/>
3	<input type="radio"/>	<input type="radio"/>	<input type="radio"/>	<input type="radio"/>	<input type="radio"/>	<input type="radio"/>	<input type="radio"/>
4	<input type="radio"/>	<input type="radio"/>	<input type="radio"/>	<input type="radio"/>	<input type="radio"/>	<input type="radio"/>	<input type="radio"/>
5	<input type="radio"/>	<input type="radio"/>	<input type="radio"/>	<input type="radio"/>	<input type="radio"/>	<input type="radio"/>	<input type="radio"/>
6	<input type="radio"/>	<input type="radio"/>	<input type="radio"/>	<input type="radio"/>	<input type="radio"/>	<input type="radio"/>	<input type="radio"/>
7	<input type="radio"/>	<input type="radio"/>	<input type="radio"/>	<input type="radio"/>	<input type="radio"/>	<input type="radio"/>	<input type="radio"/>
8	<input type="radio"/>	<input type="radio"/>	<input type="radio"/>	<input type="radio"/>	<input type="radio"/>	<input type="radio"/>	<input type="radio"/>
9	<input type="radio"/>	<input type="radio"/>	<input type="radio"/>	<input type="radio"/>	<input type="radio"/>	<input type="radio"/>	<input type="radio"/>
0	<input type="radio"/>	<input type="radio"/>	<input type="radio"/>	<input type="radio"/>	<input type="radio"/>	<input type="radio"/>	<input type="radio"/>

Set Identifier

§ ☒ ☒ ☒ ☒ ☐ ☒ ☒ ☒

Answers (1-10)

	A	B	C	D	E
1	<input type="radio"/>	<input type="radio"/>	<input type="radio"/>	<input type="radio"/>	<input type="radio"/>
2	<input type="radio"/>	<input type="radio"/>	<input type="radio"/>	<input type="radio"/>	<input type="radio"/>
3	<input type="radio"/>	<input type="radio"/>	<input type="radio"/>	<input type="radio"/>	<input type="radio"/>
4	<input type="radio"/>	<input type="radio"/>	<input type="radio"/>	<input type="radio"/>	<input type="radio"/>
5	<input type="radio"/>	<input type="radio"/>	<input type="radio"/>	<input type="radio"/>	<input type="radio"/>

	A	B	C	D	E
6	<input type="radio"/>	<input type="radio"/>	<input type="radio"/>	<input type="radio"/>	<input type="radio"/>
7	<input type="radio"/>	<input type="radio"/>	<input type="radio"/>	<input type="radio"/>	<input type="radio"/>
8	<input type="radio"/>	<input type="radio"/>	<input type="radio"/>	<input type="radio"/>	<input type="radio"/>
9	<input type="radio"/>	<input type="radio"/>	<input type="radio"/>	<input type="radio"/>	<input type="radio"/>
10	<input type="radio"/>	<input type="radio"/>	<input type="radio"/>	<input type="radio"/>	<input type="radio"/>

Answers (11-20)

	A	B	C	D	E
11	<input type="radio"/>	<input type="radio"/>	<input type="radio"/>	<input type="radio"/>	<input type="radio"/>
12	<input type="radio"/>	<input type="radio"/>	<input type="radio"/>	<input type="radio"/>	<input type="radio"/>
13	<input type="radio"/>	<input type="radio"/>	<input type="radio"/>	<input type="radio"/>	<input type="radio"/>
14	<input type="radio"/>	<input type="radio"/>	<input type="radio"/>	<input type="radio"/>	<input type="radio"/>
15	<input type="radio"/>	<input type="radio"/>	<input type="radio"/>	<input type="radio"/>	<input type="radio"/>

	A	B	C	D	E
16	<input type="radio"/>	<input type="radio"/>	<input type="radio"/>	<input type="radio"/>	<input type="radio"/>
17	<input type="radio"/>	<input type="radio"/>	<input type="radio"/>	<input type="radio"/>	<input type="radio"/>
18	<input type="radio"/>	<input type="radio"/>	<input type="radio"/>	<input type="radio"/>	<input type="radio"/>
19	<input type="radio"/>	<input type="radio"/>	<input type="radio"/>	<input type="radio"/>	<input type="radio"/>
20	<input type="radio"/>	<input type="radio"/>	<input type="radio"/>	<input type="radio"/>	<input type="radio"/>


Answers (21-30)

	A	B	C	D	E
21	<input type="radio"/>	<input type="radio"/>	<input type="radio"/>	<input type="radio"/>	<input type="radio"/>
22	<input type="radio"/>	<input type="radio"/>	<input type="radio"/>	<input type="radio"/>	<input type="radio"/>
23	<input type="radio"/>	<input type="radio"/>	<input type="radio"/>	<input type="radio"/>	<input type="radio"/>
24	<input type="radio"/>	<input type="radio"/>	<input type="radio"/>	<input type="radio"/>	<input type="radio"/>
25	<input type="radio"/>	<input type="radio"/>	<input type="radio"/>	<input type="radio"/>	<input type="radio"/>


	A	B	C	D	E
26	<input type="radio"/>	<input type="radio"/>	<input type="radio"/>	<input type="radio"/>	<input type="radio"/>
27	<input type="radio"/>	<input type="radio"/>	<input type="radio"/>	<input type="radio"/>	<input type="radio"/>
28	<input type="radio"/>	<input type="radio"/>	<input type="radio"/>	<input type="radio"/>	<input type="radio"/>
29	<input type="radio"/>	<input type="radio"/>	<input type="radio"/>	<input type="radio"/>	<input type="radio"/>
30	<input type="radio"/>	<input type="radio"/>	<input type="radio"/>	<input type="radio"/>	<input type="radio"/>

## ◇ Question 1 of 4 [CO1] [2 marks]


Which of the following circuits is/are impossible (violates Kirchhoff's laws)?

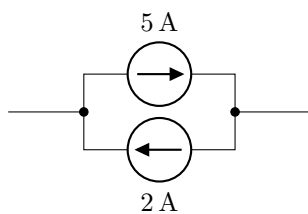

Circuit 1

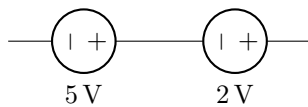


Circuit 2

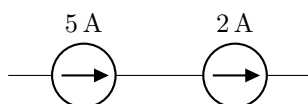

Circuit 3

- ☐ (A) Circuit 1 & 3   
 ☐ (B) Circuit 3   
 ☒ (C) **Circuit 1**   
 ☐ (D) Circuit 2   
 ☐ (E) None of the above


## ◇ Question 2 of 4 [CO3] [5 marks]

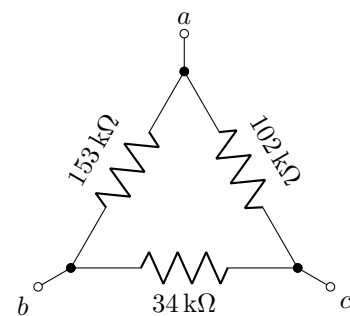

Which of the following statements is true?

- ☐ (A)  $R_{ab} = R_{bc} = R_{ca} = 21.857 \text{ k}\Omega$   
☐ (B)  $R_{ab} = 72 \Omega, R_{bc} = 30 \Omega, R_{ca} = 66 \Omega$   
☐ (C)  $R_{ab} = 153 \text{ k}\Omega, R_{bc} = 34 \text{ k}\Omega, R_{ca} = 102 \text{ k}\Omega$   
☒ (D)  **$R_{ab} = 72 \text{ k}\Omega, R_{bc} = 30 \text{ k}\Omega, R_{ca} = 66 \text{ k}\Omega$**   
☐ (E) None of the above


◇ Question 3 of 4 [CO3] [2 marks]

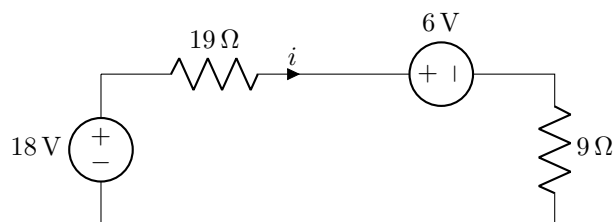

What's the relation between  $v_1$ ,  $v_2$  and  $i$ ?

- (A)  $-18 + 19i - 6 + 9i = 0$   
 (B)  $-18 - 19i - 6 + 9i = 0$   
 (C)  $-18 + 19i + 6 + 9i = 0$   
 (D)  $-18 - 19i + 6 + 9i = 0$   
 (E) None of the above

◇ Question 4 of 4 [CO1] [1 mark]

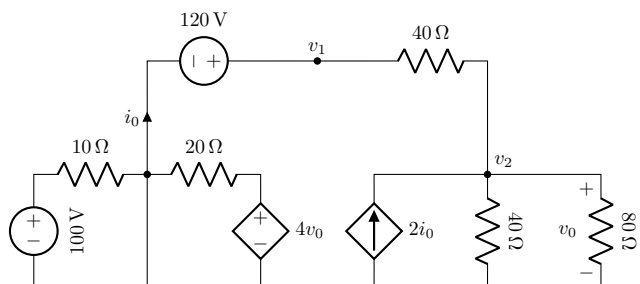

How many nodes are in this circuit?

- (A) 6 (B) 7 (C) 5 (D) 3 (E) 4



ID:

Name:



Inspiring Excellence

**Brac University**

Semester: Fall 2023

Course Code: CSE250

Circuits And Electronics

Section: 18

Set

I

Assessment: *Class Assignment 1*

Duration: 1 hour 20 minutes

Date: September 28, 2023




Full Marks: 10

- ✓ No washroom breaks. Phones must be turned off. Using/carrying any notes during the exam is not allowed.
- ✓ All **4 questions** are compulsory. Marks allotted for each question are mentioned beside each question.
- ✓ Write your answers inside the indicated boxes (where applicable). If you run out of room, continue on the back page.
- ✓ Symbols have their usual meanings.

Student ID	Answers (1-10)	Answers (11-20)	Answers (21-30)
1 <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/>	A B C D E	A B C D E	A B C D E
2 <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/>	1 <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/>	11 <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/>	21 <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/>
3 <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/>	2 <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/>	12 <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/>	22 <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/>
4 <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/>	3 <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/>	13 <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/>	23 <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/>
5 <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/>	4 <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/>	14 <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/>	24 <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/>
6 <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/>	5 <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/>	15 <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/>	25 <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/>
7 <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/>	A B C D E	A B C D E	A B C D E
8 <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/>	6 <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/>	16 <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/>	26 <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/>
9 <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/>	7 <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/>	17 <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/>	27 <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/>
0 <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/>	8 <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/>	18 <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/>	28 <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/>
Set Identifier	9 <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/>	19 <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/>	29 <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/>
§ <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/>	10 <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/>	20 <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/>	30 <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/>

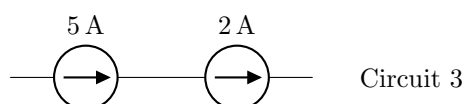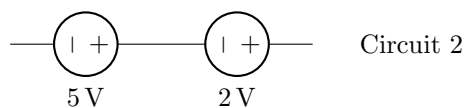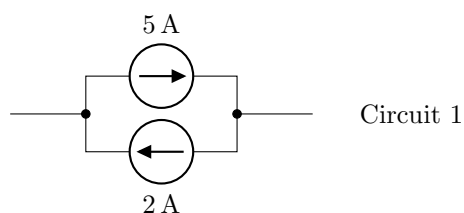
## ◇ Question 1 of 4 [CO1] [2 marks]

Which of the following circuits is/are impossible (violates Kirchhoff's laws)?



- ☐ Circuit 2   
 ☐ Circuit 3   
 ☐ Circuit 1 & 3  
☒ **Circuit 1**   
 ☐ None of the above


## ◇ Question 2 of 4 [CO3] [5 marks]

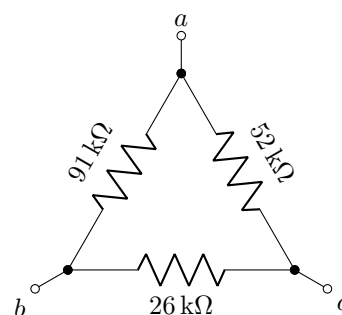

Which of the following statements is true?

- ☒ **A**  $R_{ab} = 42 \text{ k}\Omega$ ,  $R_{bc} = 22 \text{ k}\Omega$ ,  $R_{ca} = 36 \text{ k}\Omega$   
☐ B  $R_{ab} = 42 \Omega$ ,  $R_{bc} = 22 \Omega$ ,  $R_{ca} = 36 \Omega$   
☐ C  $R_{ab} = 91 \text{ k}\Omega$ ,  $R_{bc} = 26 \text{ k}\Omega$ ,  $R_{ca} = 52 \text{ k}\Omega$   
☐ D  $R_{ab} = R_{bc} = R_{ca} = 14.56 \text{ k}\Omega$   
☐ E None of the above


◇ Question 3 of 4 [CO1] [1 mark]

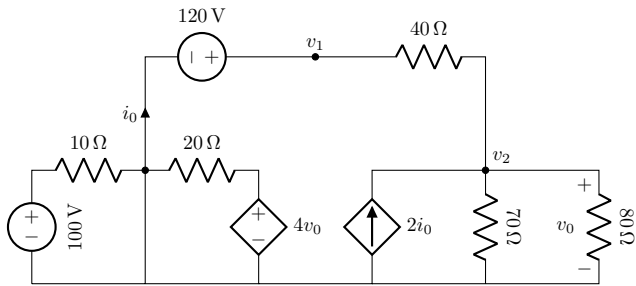

How many nodes are in this circuit?

- ☒ A 5  
 ☐ B 6  
 ☐ C 7  
 ☐ D 3  
 ☐ E 4

◇ Question 4 of 4 [CO3] [2 marks]

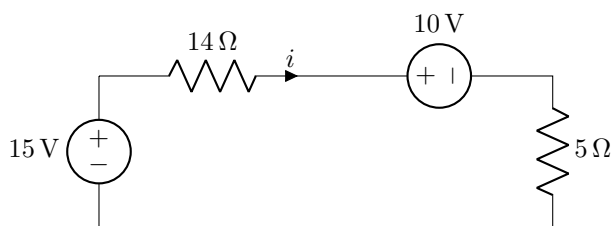

What's the relation between  $v_1$ ,  $v_2$  and  $i$ ?

- ☐ A  $-15 + 14i - 10 + 5i = 0$   
☒ B  $-15 + 14i + 10 + 5i = 0$   
☐ C  $-15 - 14i + 10 + 5i = 0$   
☐ D  $-15 - 14i - 10 + 5i = 0$   
☐ E None of the above

ID:

Name:

**Brac University**

Semester: Fall 2023

Course Code: CSE250

Circuits And Electronics

Section: 18

Set

J

Assessment: *Class Assignment 1*

Duration: 1 hour 20 minutes

Date: September 28, 2023

Full Marks: 10

- ✓ No washroom breaks. Phones must be turned off. Using/carrying any notes during the exam is not allowed.
- ✓ All **4 questions** are compulsory. Marks allotted for each question are mentioned beside each question.
- ✓ Write your answers inside the indicated boxes (where applicable). If you run out of room, continue on the back page.
- ✓ Symbols have their usual meanings.

Student ID

       
1 ☐ ☐ ☐ ☐ ☐ ☐ ☐ ☐2 ☐ ☐ ☐ ☐ ☐ ☐ ☐ ☐3 ☐ ☐ ☐ ☐ ☐ ☐ ☐ ☐4 ☐ ☐ ☐ ☐ ☐ ☐ ☐ ☐5 ☐ ☐ ☐ ☐ ☐ ☐ ☐ ☐6 ☐ ☐ ☐ ☐ ☐ ☐ ☐ ☐7 ☐ ☐ ☐ ☐ ☐ ☐ ☐ ☐8 ☐ ☐ ☐ ☐ ☐ ☐ ☐ ☐9 ☐ ☐ ☐ ☐ ☐ ☐ ☐ ☐0 ☐ ☐ ☐ ☐ ☐ ☐ ☐ ☐

Set Identifier

§ ☒ ☒ ☒ ☒ ☐ ☒ ☐ ☒

Answers (1-10)

A B C D E

1 ☐ ☐ ☐ ☐ ☐2 ☐ ☐ ☐ ☐ ☐3 ☐ ☐ ☐ ☐ ☐4 ☐ ☐ ☐ ☐ ☐5 ☐ ☐ ☐ ☐ ☐

A B C D E

6 ☐ ☐ ☐ ☐ ☐7 ☐ ☐ ☐ ☐ ☐8 ☐ ☐ ☐ ☐ ☐9 ☐ ☐ ☐ ☐ ☐10 ☐ ☐ ☐ ☐ ☐

Answers (11-20)

A B C D E

11 ☐ ☐ ☐ ☐ ☐12 ☐ ☐ ☐ ☐ ☐13 ☐ ☐ ☐ ☐ ☐14 ☐ ☐ ☐ ☐ ☐15 ☐ ☐ ☐ ☐ ☐

A B C D E

16 ☐ ☐ ☐ ☐ ☐17 ☐ ☐ ☐ ☐ ☐18 ☐ ☐ ☐ ☐ ☐19 ☐ ☐ ☐ ☐ ☐20 ☐ ☐ ☐ ☐ ☐

Answers (21-30)


A B C D E

21 ☐ ☐ ☐ ☐ ☐22 ☐ ☐ ☐ ☐ ☐23 ☐ ☐ ☐ ☐ ☐24 ☐ ☐ ☐ ☐ ☐25 ☐ ☐ ☐ ☐ ☐

A B C D E

26 ☐ ☐ ☐ ☐ ☐27 ☐ ☐ ☐ ☐ ☐28 ☐ ☐ ☐ ☐ ☐29 ☐ ☐ ☐ ☐ ☐30 ☐ ☐ ☐ ☐ ☐


## ◇ Question 1 of 4 [CO3] [2 marks]

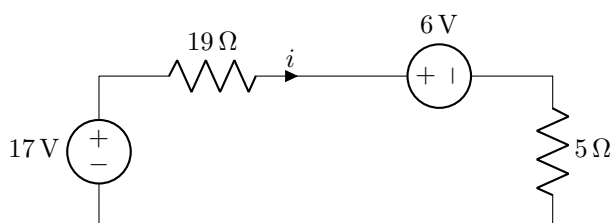What's the relation between  $v_1$ ,  $v_2$  and  $i$ ?


- (A)  $-17 - 19i - 6 + 5i = 0$
- (B)  $-17 + 19i - 6 + 5i = 0$
- (C)  $-17 + 19i + 6 + 5i = 0$
- (D)  $-17 - 19i + 6 + 5i = 0$
- (E) None of the above

## ◇ Question 2 of 4 [CO1] [2 marks]


Which of the following circuits is/are impossible (violates Kirchhoff's laws)?

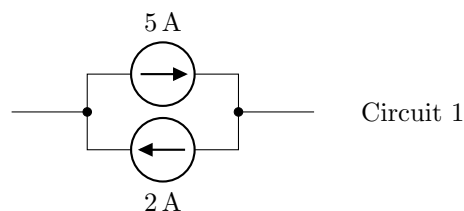

Circuit 1

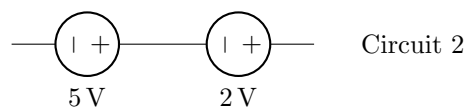


Circuit 2

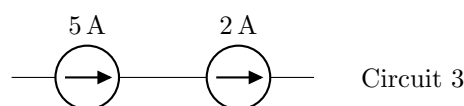

Circuit 3

- (A) Circuit 1 & 3 (B) **Circuit 1** (C) Circuit 3
- (D) Circuit 2 (E) None of the above


◇ Question 3 of 4 [CO3] [5 marks]

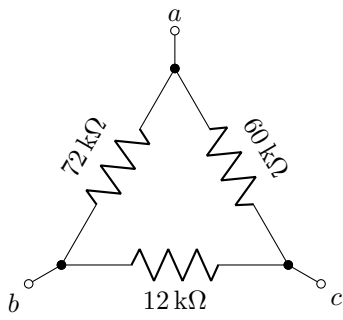

Which of the following statements is true?

- (A)  $R_{ab} = 72\text{ k}\Omega$ ,  $R_{bc} = 12\text{ k}\Omega$ ,  $R_{ca} = 60\text{ k}\Omega$
- (B)  $R_{ab} = 36\text{ k}\Omega$ ,  $R_{bc} = 11\text{ k}\Omega$ ,  $R_{ca} = 35\text{ k}\Omega$
- (C)  $R_{ab} = 36\text{ }\Omega$ ,  $R_{bc} = 11\text{ }\Omega$ ,  $R_{ca} = 35\text{ }\Omega$
- (D)  $R_{ab} = R_{bc} = R_{ca} = 8.78\text{ k}\Omega$
- (E) None of the above

◇ Question 4 of 4 [CO1] [1 mark]

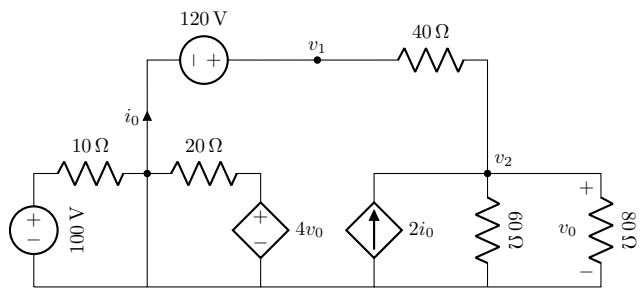

How many nodes are in this circuit?

- (A) 4
- (B) 7
- (C) 6
- (D) 3
- (E) 5