

Brac University

Semester: Fall 2023  
Course Code: CSE250  
Circuits And Electronics  
Section: 18  
Faculty: SDS

Name:

Set

A




Inspiring Excellence

Assessment: *Class Assignment 1*  
Duration: 1 hour 20 minutes  
Date: September 28, 2023  
Full Marks: 10

- ✓ No washroom breaks. Phones must be turned off. Using/carrying any notes during the exam is not allowed.
- ✓ All **4 question(s)** are compulsory. Marks allotted for each question are mentioned beside each question.
- ✓ Write your answers inside the indicated boxes (where applicable). If you run out of room, continue on the back page.
- ✓ Symbols have their usual meanings.

Student ID	Answers (1-10)	Answers (11-20)	Answers (21-30)
<div><div></div><div></div><div></div><div></div><div></div><div></div><div></div><div></div></div>			
1 <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/>	A B C D E	A B C D E	A B C D E
2 <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/>	1 <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/>	11 <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/>	21 <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/>
3 <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/>	2 <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/>	12 <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/>	22 <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/>
4 <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/>	3 <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/>	13 <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/>	23 <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/>
5 <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/>	4 <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/>	14 <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/>	24 <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/>
6 <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/>	5 <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/>	15 <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/>	25 <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/>
7 <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/>			
8 <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/>	A B C D E	A B C D E	A B C D E
9 <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/>	6 <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/>	16 <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/>	26 <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/>
0 <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/>	7 <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/>	17 <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/>	27 <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/>
	8 <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/>	18 <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/>	28 <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/>
Set Identifier	9 <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/>	19 <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/>	29 <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/>
§ <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/>	10 <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/>	20 <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/>	30 <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/>

◇ Question 1 of 4 [CO3] [5 marks]

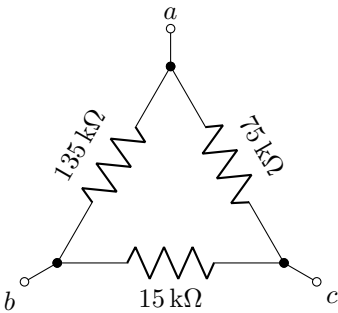


Which of the following statements is true?

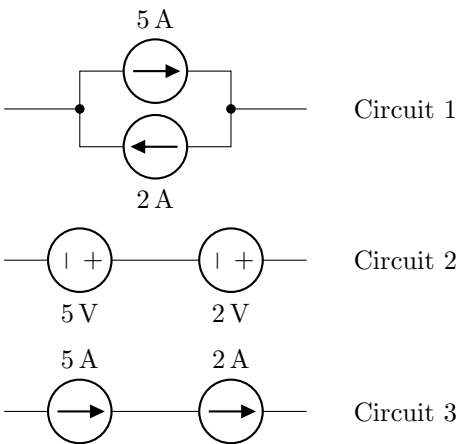- (A)  $R_{ab} = R_{bc} = R_{ca} = 11.441\text{ k}\Omega$
- (B)  $R_{ab} = 135\text{ k}\Omega, R_{bc} = 15\text{ k}\Omega, R_{ca} = 75\text{ k}\Omega$
- (C)  $R_{ab} = 54\text{ k}\Omega, R_{bc} = 14\text{ k}\Omega, R_{ca} = 50\text{ k}\Omega$
- (D)  $R_{ab} = 54\text{ }\Omega, R_{bc} = 14\text{ }\Omega, R_{ca} = 50\text{ }\Omega$
- (E) None of the above


◇ Question 2 of 4 [CO1] [2 marks]

Which of the following circuits is/are impossible (violates Kirchhoff's laws)?




- (A) Circuit 2
- (B) Circuit 3
- (C) **Circuit 1**
- (D) Circuit 1 & 3
- (E) None of the above

◇ Question 3 of 4 [CO3] [2 marks]

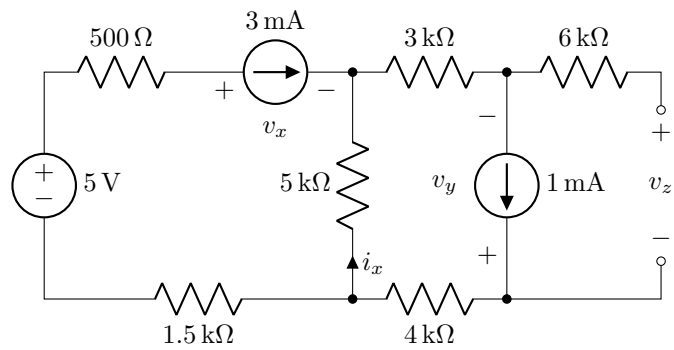

- (A) b
- (B) a
- (C) c

◇ Question 4 of 4 [CO1] [1 mark]

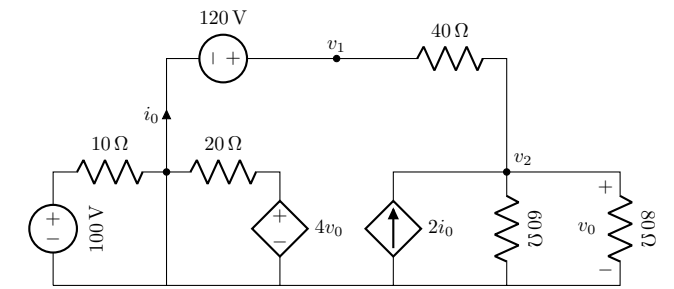

How many nodes are in this circuit?

- (A) 7
- (B) 3
- (C) 5
- (D) 4
- (E) 6

Brac University

Semester: Fall 2023  
Course Code: CSE250  
Circuits And Electronics  
Section: 18  
Faculty: SDS

Name:

ID:

Set

B



Inspiring Excellence

Assessment: *Class Assignment 1*  
Duration: 1 hour 20 minutes  
Date: September 28, 2023  
Full Marks: 10


- ✓ No washroom breaks. Phones must be turned off. Using/carrying any notes during the exam is not allowed.
- ✓ All **4 question(s)** are compulsory. Marks allotted for each question are mentioned beside each question.
- ✓ Write your answers inside the indicated boxes (where applicable). If you run out of room, continue on the back page.
- ✓ Symbols have their usual meanings.

Student ID	Answers (1-10)	Answers (11-20)	Answers (21-30)
<div><div></div><div></div><div></div><div></div><div></div><div></div><div></div><div></div></div>	<div>A B C D E</div>	<div>A B C D E</div>	<div>A B C D E</div>
1 <div><div></div><div></div><div></div><div></div><div></div><div></div><div></div><div></div></div>	1 <div><div></div><div></div><div></div><div></div><div></div></div>	11 <div><div></div><div></div><div></div><div></div><div></div></div>	21 <div><div></div><div></div><div></div><div></div><div></div></div>
2 <div><div></div><div></div><div></div><div></div><div></div><div></div><div></div><div></div></div>	2 <div><div></div><div></div><div></div><div></div><div></div></div>	12 <div><div></div><div></div><div></div><div></div><div></div></div>	22 <div><div></div><div></div><div></div><div></div><div></div></div>
3 <div><div></div><div></div><div></div><div></div><div></div><div></div><div></div><div></div></div>	3 <div><div></div><div></div><div></div><div></div><div></div></div>	13 <div><div></div><div></div><div></div><div></div><div></div></div>	23 <div><div></div><div></div><div></div><div></div><div></div></div>
4 <div><div></div><div></div><div></div><div></div><div></div><div></div><div></div><div></div></div>	4 <div><div></div><div></div><div></div><div></div><div></div></div>	14 <div><div></div><div></div><div></div><div></div><div></div></div>	24 <div><div></div><div></div><div></div><div></div><div></div></div>
5 <div><div></div><div></div><div></div><div></div><div></div><div></div><div></div><div></div></div>	5 <div><div></div><div></div><div></div><div></div><div></div></div>	15 <div><div></div><div></div><div></div><div></div><div></div></div>	25 <div><div></div><div></div><div></div><div></div><div></div></div>
6 <div><div></div><div></div><div></div><div></div><div></div><div></div><div></div><div></div></div>			
7 <div><div></div><div></div><div></div><div></div><div></div><div></div><div></div><div></div></div>			
8 <div><div></div><div></div><div></div><div></div><div></div><div></div><div></div><div></div></div>	<div>A B C D E</div>	<div>A B C D E</div>	<div>A B C D E</div>
9 <div><div></div><div></div><div></div><div></div><div></div><div></div><div></div><div></div></div>	6 <div><div></div><div></div><div></div><div></div><div></div></div>	16 <div><div></div><div></div><div></div><div></div><div></div></div>	26 <div><div></div><div></div><div></div><div></div><div></div></div>
0 <div><div></div><div></div><div></div><div></div><div></div><div></div><div></div><div></div></div>	7 <div><div></div><div></div><div></div><div></div><div></div></div>	17 <div><div></div><div></div><div></div><div></div><div></div></div>	27 <div><div></div><div></div><div></div><div></div><div></div></div>
	8 <div><div></div><div></div><div></div><div></div><div></div></div>	18 <div><div></div><div></div><div></div><div></div><div></div></div>	28 <div><div></div><div></div><div></div><div></div><div></div></div>
	9 <div><div></div><div></div><div></div><div></div><div></div></div>	19 <div><div></div><div></div><div></div><div></div><div></div></div>	29 <div><div></div><div></div><div></div><div></div><div></div></div>
	10 <div><div></div><div></div><div></div><div></div><div></div></div>	20 <div><div></div><div></div><div></div><div></div><div></div></div>	30 <div><div></div><div></div><div></div><div></div><div></div></div>

Set Identifier

§


◇ Question 1 of 4 [CO3] [2 marks]

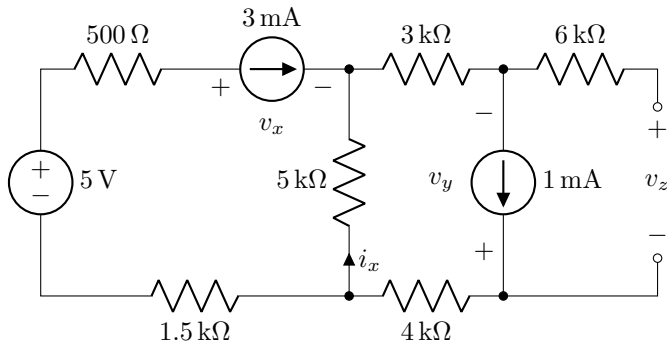

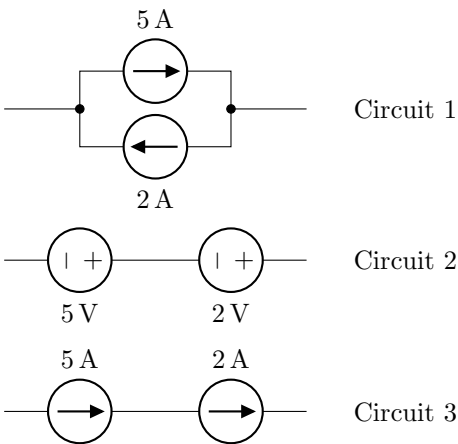- (A) c
- (B) b
- (C) a


◇ Question 2 of 4 [CO1] [2 marks]

Which of the following circuits is/are impossible (violates Kirchhoff's laws)?



- (A) Circuit 3
- (B) Circuit 1 & 3
- (C) Circuit 1
- (D) Circuit 2
- (E) None of the above


◇ Question 3 of 4 [CO1] [1 mark]

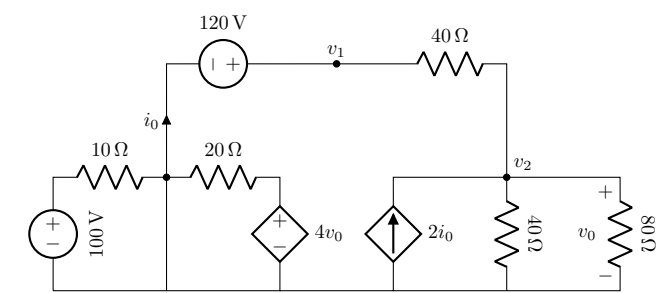

How many nodes are in this circuit?

- (A) 6   (B) 5   (C) 3   (D) 4   (E) 7

◇ Question 4 of 4 [CO3] [5 marks]

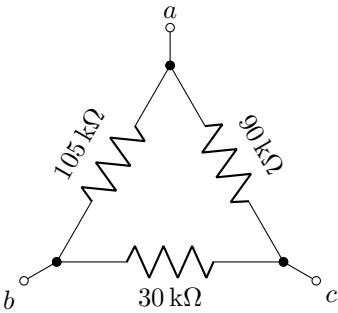

Which of the following statements is true?

- (A)  $R_{ab} = 105\text{ k}\Omega, R_{bc} = 30\text{ k}\Omega, R_{ca} = 90\text{ k}\Omega$   
(B)  $R_{ab} = 56\text{ }\Omega, R_{bc} = 26\text{ }\Omega, R_{ca} = 54\text{ }\Omega$   
(C)  $R_{ab} = 56\text{ k}\Omega, R_{bc} = 26\text{ k}\Omega, R_{ca} = 54\text{ k}\Omega$   
(D)  $R_{ab} = R_{bc} = R_{ca} = 18.529\text{ k}\Omega$   
(E) None of the above

Brac University

Semester: Fall 2023

Course Code: CSE250

Circuits And Electronics

Section: 18

Faculty: SDS

Name:

ID:

Set

C



Inspiring Excellence

Assessment: *Class Assignment 1*

Duration: 1 hour 20 minutes


Date: September 28, 2023

Full Marks: 10

- ✓ No washroom breaks. Phones must be turned off. Using/carrying any notes during the exam is not allowed.
- ✓ All **4 question(s)** are compulsory. Marks allotted for each question are mentioned beside each question.
- ✓ Write your answers inside the indicated boxes (where applicable). If you run out of room, continue on the back page.
- ✓ Symbols have their usual meanings.

Student ID	Answers (1-10)	Answers (11-20)	Answers (21-30)
<div><div></div><div></div><div></div><div></div><div></div><div></div><div></div><div></div></div>			
1 <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/>	A B C D E	A B C D E	A B C D E
2 <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/>	1 <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/>	11 <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/>	21 <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/>
3 <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/>	2 <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/>	12 <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/>	22 <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/>
4 <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/>	3 <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/>	13 <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/>	23 <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/>
5 <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/>	4 <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/>	14 <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/>	24 <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/>
6 <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/>	5 <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/>	15 <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/>	25 <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/>
7 <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/>			
8 <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/>	A B C D E	A B C D E	A B C D E
9 <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/>	6 <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/>	16 <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/>	26 <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/>
0 <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/>	7 <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/>	17 <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/>	27 <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/>
	8 <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/>	18 <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/>	28 <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/>
Set Identifier	9 <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/>	19 <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/>	29 <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/>
§ <input checked="" type="radio"/> <input checked="" type="radio"/> <input checked="" type="radio"/> <input checked="" type="radio"/> <input checked="" type="radio"/> <input checked="" type="radio"/> <input type="radio"/> <input type="radio"/>	10 <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/>	20 <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/>	30 <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/>

◇ Question 1 of 4 [CO1] [1 mark]

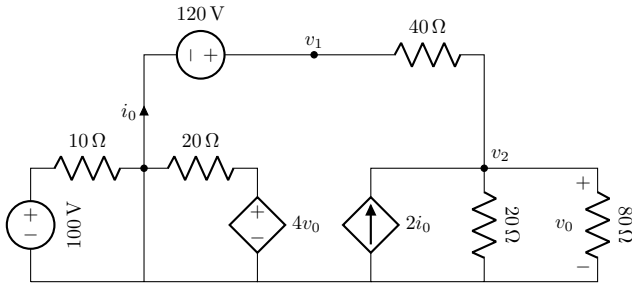


How many nodes are in this circuit?

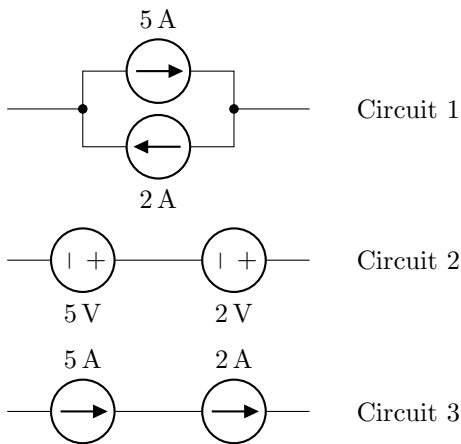- (A) 5 (B) 4 (C) 7 (D) 6 (E) 3


◇ Question 2 of 4 [CO1] [2 marks]

Which of the following circuits is/are impossible (violates Kirchhoff's laws)?



- (A) Circuit 2 (B) Circuit 1 (C) Circuit 3 (D) Circuit 1 & 3 (E) None of the above


◇ Question 3 of 4 [CO3] [2 marks]

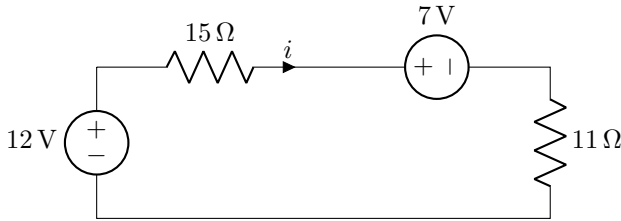

What’s the relation between  $v_1, v_2$  and  $i$ ?

- ☐ (A)  $-12 - 15i + 7 + 11i = 0$
- ☐ (B)  $-12 + 15i - 7 + 11i = 0$
- ☒ (C)  $-12 + 15i + 7 + 11i = 0$
- ☐ (D)  $-12 - 15i - 7 + 11i = 0$
- ☐ (E) None of the above

◇ Question 4 of 4 [CO3] [5 marks]

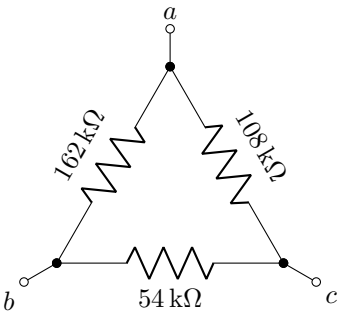

Which of the following statements is true?

- ☐ (A)  $R_{ab} = R_{bc} = R_{ca} = 29.455\text{ k}\Omega$
- ☐ (B)  $R_{ab} = 81\text{ }\Omega, R_{bc} = 45\text{ }\Omega, R_{ca} = 72\text{ }\Omega$
- ☐ (C)  $R_{ab} = 162\text{ k}\Omega, R_{bc} = 54\text{ k}\Omega, R_{ca} = 108\text{ k}\Omega$
- ☒ (D)  $R_{ab} = 81\text{ k}\Omega, R_{bc} = 45\text{ k}\Omega, R_{ca} = 72\text{ k}\Omega$
- ☐ (E) None of the above



Brac University

Semester: Fall 2023

Course Code: CSE250

Circuits And Electronics

Section: 18

Faculty: SDS

Name:

ID:

Set

D



Inspiring Excellence

Assessment: *Class Assignment 1*

Duration: 1 hour 20 minutes


Date: September 28, 2023

Full Marks: 10

- ✓ No washroom breaks. Phones must be turned off. Using/carrying any notes during the exam is not allowed.
- ✓ All **4 question(s)** are compulsory. Marks allotted for each question are mentioned beside each question.
- ✓ Write your answers inside the indicated boxes (where applicable). If you run out of room, continue on the back page.
- ✓ Symbols have their usual meanings.

Student ID	Answers (1-10)	Answers (11-20)	Answers (21-30)
<div><div></div><div></div><div></div><div></div><div></div><div></div><div></div><div></div></div>			
1 <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/>	A B C D E	A B C D E	A B C D E
2 <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/>	1 <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/>	11 <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/>	21 <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/>
3 <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/>	2 <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/>	12 <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/>	22 <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/>
4 <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/>	3 <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/>	13 <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/>	23 <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/>
5 <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/>	4 <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/>	14 <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/>	24 <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/>
6 <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/>	5 <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/>	15 <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/>	25 <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/>
7 <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/>			
8 <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/>	A B C D E	A B C D E	A B C D E
9 <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/>	6 <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/>	16 <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/>	26 <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/>
0 <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/>	7 <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/>	17 <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/>	27 <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/>
	8 <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/>	18 <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/>	28 <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/>
Set Identifier	9 <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/>	19 <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/>	29 <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/>
§ <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/>	10 <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/>	20 <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/>	30 <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/>


◇ Question 1 of 4 [CO3] [5 marks]

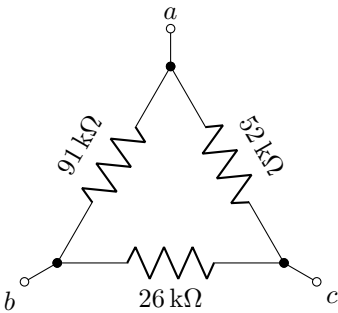

Which of the following statements is true?

- (A)  $R_{ab} = 91\text{ k}\Omega$ ,  $R_{bc} = 26\text{ k}\Omega$ ,  $R_{ca} = 52\text{ k}\Omega$
- (B)  $R_{ab} = 42\text{ k}\Omega$ ,  $R_{bc} = 22\text{ k}\Omega$ ,  $R_{ca} = 36\text{ k}\Omega$
- (C)  $R_{ab} = 42\text{ }\Omega$ ,  $R_{bc} = 22\text{ }\Omega$ ,  $R_{ca} = 36\text{ }\Omega$
- (D)  $R_{ab} = R_{bc} = R_{ca} = 14.56\text{ k}\Omega$
- (E) None of the above

◇ Question 2 of 4 [CO1] [1 mark]

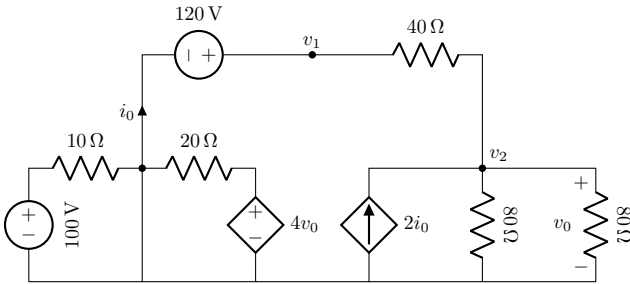


How many nodes are in this circuit?

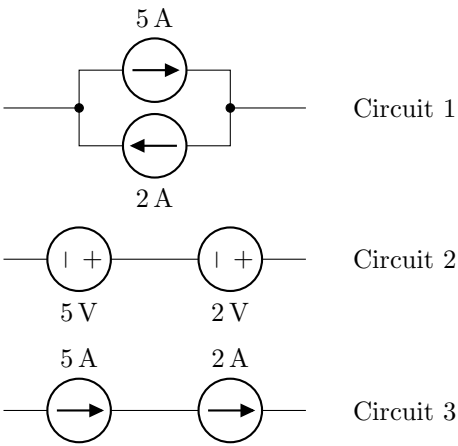- (A) 3
- (B) 7
- (C) 4
- (D) 5
- (E) 6


◇ Question 3 of 4 [CO1] [2 marks]

Which of the following circuits is/are impossible (violates Kirchhoff’s laws)?



- ☐ (A) Circuit 2
- ☐ (B) Circuit 3
- ☒ (C) **Circuit 1**
- ☐ (D) Circuit 1 & 3
- ☐ (E) None of the above

◇ Question 4 of 4 [CO3] [2 marks]

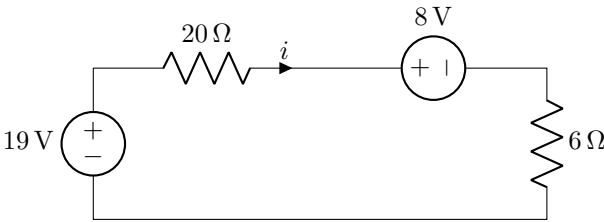

What’s the relation between  $v_1$ ,  $v_2$  and  $i$ ?

- ☒ (A)  **$-19 + 20i + 8 + 6i = 0$**
- ☐ (B)  $-19 - 20i - 8 + 6i = 0$
- ☐ (C)  $-19 - 20i + 8 + 6i = 0$
- ☐ (D)  $-19 + 20i - 8 + 6i = 0$
- ☐ (E) None of the above



Brac University

Semester: Fall 2023  
Course Code: CSE250  
Circuits And Electronics  
Section: 18  
Faculty: SDS

Name:

Set

E



Inspiring Excellence

Assessment: *Class Assignment 1*  
Duration: 1 hour 20 minutes  
Date: September 28, 2023  
Full Marks: 10


- ✓ No washroom breaks. Phones must be turned off. Using/carrying any notes during the exam is not allowed.
- ✓ All **4 question(s)** are compulsory. Marks allotted for each question are mentioned beside each question.
- ✓ Write your answers inside the indicated boxes (where applicable). If you run out of room, continue on the back page.
- ✓ Symbols have their usual meanings.

Student ID	Answers (1-10)	Answers (11-20)	Answers (21-30)
<div><div></div><div></div><div></div><div></div><div></div><div></div><div></div><div></div></div>	<div>A B C D E</div>	<div>A B C D E</div>	<div>A B C D E</div>
1 <div><div></div><div></div><div></div><div></div><div></div><div></div><div></div><div></div></div>	1 <div><div></div><div></div><div></div><div></div><div></div><div></div></div>	11 <div><div></div><div></div><div></div><div></div><div></div><div></div></div>	21 <div><div></div><div></div><div></div><div></div><div></div><div></div></div>
2 <div><div></div><div></div><div></div><div></div><div></div><div></div><div></div><div></div></div>	2 <div><div></div><div></div><div></div><div></div><div></div><div></div></div>	12 <div><div></div><div></div><div></div><div></div><div></div><div></div></div>	22 <div><div></div><div></div><div></div><div></div><div></div><div></div></div>
3 <div><div></div><div></div><div></div><div></div><div></div><div></div><div></div><div></div></div>	3 <div><div></div><div></div><div></div><div></div><div></div><div></div></div>	13 <div><div></div><div></div><div></div><div></div><div></div><div></div></div>	23 <div><div></div><div></div><div></div><div></div><div></div><div></div></div>
4 <div><div></div><div></div><div></div><div></div><div></div><div></div><div></div><div></div></div>	4 <div><div></div><div></div><div></div><div></div><div></div><div></div></div>	14 <div><div></div><div></div><div></div><div></div><div></div><div></div></div>	24 <div><div></div><div></div><div></div><div></div><div></div><div></div></div>
5 <div><div></div><div></div><div></div><div></div><div></div><div></div><div></div><div></div></div>	5 <div><div></div><div></div><div></div><div></div><div></div><div></div></div>	15 <div><div></div><div></div><div></div><div></div><div></div><div></div></div>	25 <div><div></div><div></div><div></div><div></div><div></div><div></div></div>
6 <div><div></div><div></div><div></div><div></div><div></div><div></div><div></div><div></div></div>			
7 <div><div></div><div></div><div></div><div></div><div></div><div></div><div></div><div></div></div>			
8 <div><div></div><div></div><div></div><div></div><div></div><div></div><div></div><div></div></div>	<div>A B C D E</div>	<div>A B C D E</div>	<div>A B C D E</div>
9 <div><div></div><div></div><div></div><div></div><div></div><div></div><div></div><div></div></div>	6 <div><div></div><div></div><div></div><div></div><div></div><div></div></div>	16 <div><div></div><div></div><div></div><div></div><div></div><div></div></div>	26 <div><div></div><div></div><div></div><div></div><div></div><div></div></div>
0 <div><div></div><div></div><div></div><div></div><div></div><div></div><div></div><div></div></div>	7 <div><div></div><div></div><div></div><div></div><div></div><div></div></div>	17 <div><div></div><div></div><div></div><div></div><div></div><div></div></div>	27 <div><div></div><div></div><div></div><div></div><div></div><div></div></div>
	8 <div><div></div><div></div><div></div><div></div><div></div><div></div></div>	18 <div><div></div><div></div><div></div><div></div><div></div><div></div></div>	28 <div><div></div><div></div><div></div><div></div><div></div><div></div></div>
	9 <div><div></div><div></div><div></div><div></div><div></div><div></div></div>	19 <div><div></div><div></div><div></div><div></div><div></div><div></div></div>	29 <div><div></div><div></div><div></div><div></div><div></div><div></div></div>
	10 <div><div></div><div></div><div></div><div></div><div></div><div></div></div>	20 <div><div></div><div></div><div></div><div></div><div></div><div></div></div>	30 <div><div></div><div></div><div></div><div></div><div></div><div></div></div>

Set Identifier

§

◇ Question 1 of 4 [CO1] [1 mark]

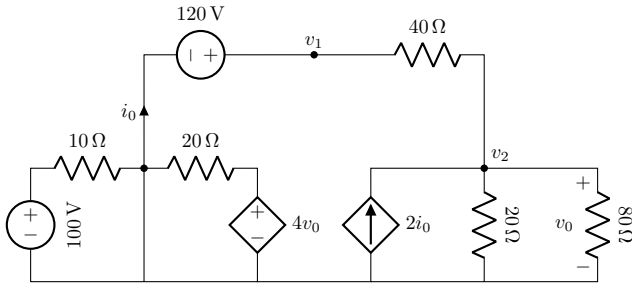


How many nodes are in this circuit?

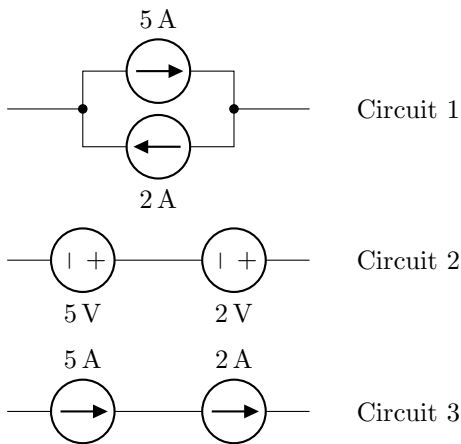- (A) 4 (B) 5 (C) 6 (D) 3 (E) 7


◇ Question 2 of 4 [CO1] [2 marks]

Which of the following circuits is/are impossible (violates Kirchhoff's laws)?



- (A) Circuit 1 (B) Circuit 3 (C) Circuit 1 & 3  
(D) Circuit 2 (E) None of the above


◇ Question 3 of 4 [CO3] [5 marks]

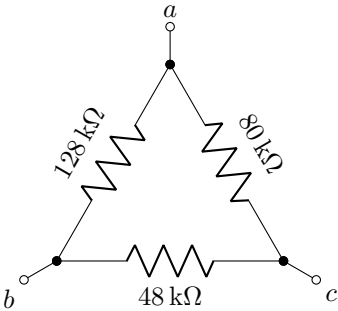

Which of the following statements is true?

- ☐ (A)  $R_{ab} = 64\text{ }\Omega, R_{bc} = 39\text{ }\Omega, R_{ca} = 55\text{ }\Omega$
- ☐ (B)  $R_{ab} = 128\text{ k}\Omega, R_{bc} = 48\text{ k}\Omega, R_{ca} = 80\text{ k}\Omega$
- ☒ (C)  $R_{ab} = 64\text{ k}\Omega, R_{bc} = 39\text{ k}\Omega, R_{ca} = 55\text{ k}\Omega$
- ☐ (D)  $R_{ab} = R_{bc} = R_{ca} = 24.304\text{ k}\Omega$
- ☐ (E) None of the above

◇ Question 4 of 4 [CO3] [2 marks]

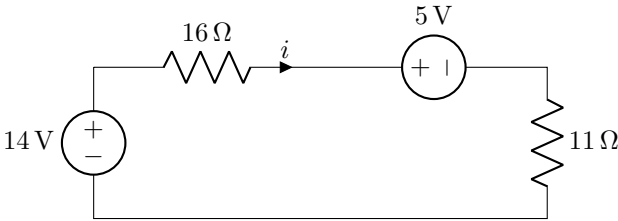

What's the relation between  $v_1, v_2$  and  $i$ ?

- ☐ (A)  $-14 + 16i - 5 + 11i = 0$
- ☐ (B)  $-14 - 16i + 5 + 11i = 0$
- ☒ (C)  $-14 + 16i + 5 + 11i = 0$
- ☐ (D)  $-14 - 16i - 5 + 11i = 0$
- ☐ (E) None of the above

Brac University

Semester: Fall 2023  
Course Code: CSE250  
Circuits And Electronics  
Section: 18  
Faculty: SDS

Name:

Set

F




Inspiring Excellence

Assessment: *Class Assignment 1*  
Duration: 1 hour 20 minutes  
Date: September 28, 2023  
Full Marks: 10

- ✓ No washroom breaks. Phones must be turned off. Using/carrying any notes during the exam is not allowed.
- ✓ All **4 question(s)** are compulsory. Marks allotted for each question are mentioned beside each question.
- ✓ Write your answers inside the indicated boxes (where applicable). If you run out of room, continue on the back page.
- ✓ Symbols have their usual meanings.

Student ID	Answers (1-10)	Answers (11-20)	Answers (21-30)
<div><div></div><div></div><div></div><div></div><div></div><div></div><div></div><div></div></div>	<div>A B C D E</div>	<div>A B C D E</div>	<div>A B C D E</div>
1 <div><div></div><div></div><div></div><div></div><div></div><div></div><div></div><div></div></div>	1 <div><div></div><div></div><div></div><div></div><div></div><div></div></div>	11 <div><div></div><div></div><div></div><div></div><div></div><div></div></div>	21 <div><div></div><div></div><div></div><div></div><div></div><div></div></div>
2 <div><div></div><div></div><div></div><div></div><div></div><div></div><div></div><div></div></div>	2 <div><div></div><div></div><div></div><div></div><div></div><div></div></div>	12 <div><div></div><div></div><div></div><div></div><div></div><div></div></div>	22 <div><div></div><div></div><div></div><div></div><div></div><div></div></div>
3 <div><div></div><div></div><div></div><div></div><div></div><div></div><div></div><div></div></div>	3 <div><div></div><div></div><div></div><div></div><div></div><div></div></div>	13 <div><div></div><div></div><div></div><div></div><div></div><div></div></div>	23 <div><div></div><div></div><div></div><div></div><div></div><div></div></div>
4 <div><div></div><div></div><div></div><div></div><div></div><div></div><div></div><div></div></div>	4 <div><div></div><div></div><div></div><div></div><div></div><div></div></div>	14 <div><div></div><div></div><div></div><div></div><div></div><div></div></div>	24 <div><div></div><div></div><div></div><div></div><div></div><div></div></div>
5 <div><div></div><div></div><div></div><div></div><div></div><div></div><div></div><div></div></div>	5 <div><div></div><div></div><div></div><div></div><div></div><div></div></div>	15 <div><div></div><div></div><div></div><div></div><div></div><div></div></div>	25 <div><div></div><div></div><div></div><div></div><div></div><div></div></div>
6 <div><div></div><div></div><div></div><div></div><div></div><div></div><div></div><div></div></div>			
7 <div><div></div><div></div><div></div><div></div><div></div><div></div><div></div><div></div></div>	<div>A B C D E</div>	<div>A B C D E</div>	<div>A B C D E</div>
8 <div><div></div><div></div><div></div><div></div><div></div><div></div><div></div><div></div></div>	6 <div><div></div><div></div><div></div><div></div><div></div><div></div></div>	16 <div><div></div><div></div><div></div><div></div><div></div><div></div></div>	26 <div><div></div><div></div><div></div><div></div><div></div><div></div></div>
9 <div><div></div><div></div><div></div><div></div><div></div><div></div><div></div><div></div></div>	7 <div><div></div><div></div><div></div><div></div><div></div><div></div></div>	17 <div><div></div><div></div><div></div><div></div><div></div><div></div></div>	27 <div><div></div><div></div><div></div><div></div><div></div><div></div></div>
0 <div><div></div><div></div><div></div><div></div><div></div><div></div><div></div><div></div></div>	8 <div><div></div><div></div><div></div><div></div><div></div><div></div></div>	18 <div><div></div><div></div><div></div><div></div><div></div><div></div></div>	28 <div><div></div><div></div><div></div><div></div><div></div><div></div></div>
Set Identifier	9 <div><div></div><div></div><div></div><div></div><div></div><div></div></div>	19 <div><div></div><div></div><div></div><div></div><div></div><div></div></div>	29 <div><div></div><div></div><div></div><div></div><div></div><div></div></div>
§ <div><div></div><div></div><div></div><div></div><div></div><div></div><div></div><div></div></div>	10 <div><div></div><div></div><div></div><div></div><div></div><div></div></div>	20 <div><div></div><div></div><div></div><div></div><div></div><div></div></div>	30 <div><div></div><div></div><div></div><div></div><div></div><div></div></div>

◇ Question 1 of 4 [CO1] [1 mark]

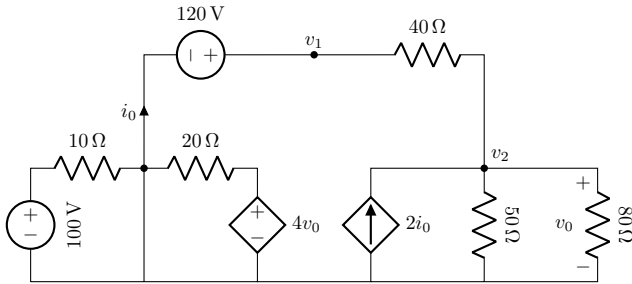


How many nodes are in this circuit?

- A 5** (B 6) (C 7) (D 4) (E 3)


◇ Question 2 of 4 [CO1] [2 marks]

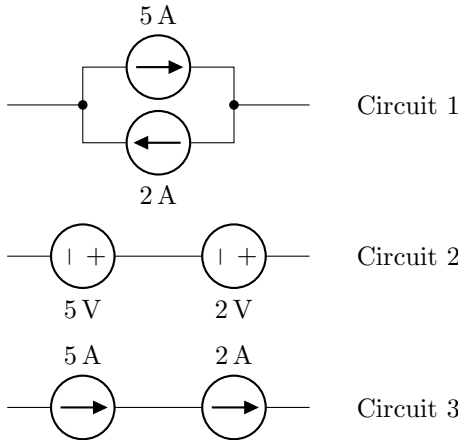Which of the following circuits is/are impossible (violates Kirchhoff's laws)?



- A Circuit 1** (B Circuit 1 & 3) (C Circuit 3)  
(D Circuit 2) (E None of the above)


◇ Question 3 of 4 [CO3] [2 marks]

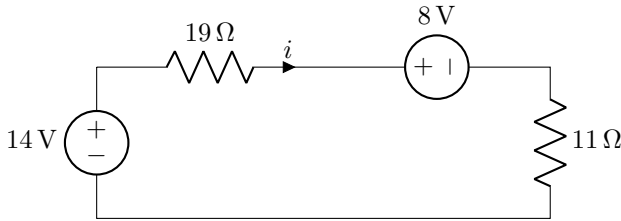

What’s the relation between  $v_1, v_2$  and  $i$ ?

- ☐ (A)  $-14 - 19i + 8 + 11i = 0$
- ☐ (B)  $-14 + 19i - 8 + 11i = 0$
- ☐ (C)  $-14 - 19i - 8 + 11i = 0$
- ☒ (D)  $-14 + 19i + 8 + 11i = 0$
- ☐ (E) None of the above

◇ Question 4 of 4 [CO3] [5 marks]

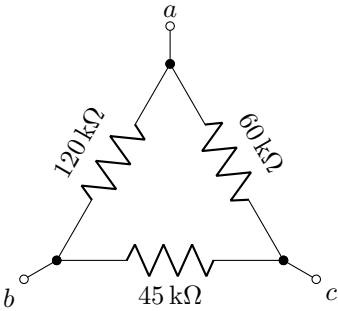

Which of the following statements is true?

- ☒ (A)  $R_{ab} = 56\text{ k}\Omega, R_{bc} = 36\text{ k}\Omega, R_{ca} = 44\text{ k}\Omega$
- ☐ (B)  $R_{ab} = R_{bc} = R_{ca} = 21.176\text{ k}\Omega$
- ☐ (C)  $R_{ab} = 120\text{ k}\Omega, R_{bc} = 45\text{ k}\Omega, R_{ca} = 60\text{ k}\Omega$
- ☐ (D)  $R_{ab} = 56\text{ }\Omega, R_{bc} = 36\text{ }\Omega, R_{ca} = 44\text{ }\Omega$
- ☐ (E) None of the above

Brac University

Semester: Fall 2023

Course Code: CSE250

Circuits And Electronics

Section: 18

Faculty: SDS

Name:

ID:

Set

G



Inspiring Excellence

Assessment: *Class Assignment 1*

Duration: 1 hour 20 minutes


Date: September 28, 2023

Full Marks: 10

- ✓ No washroom breaks. Phones must be turned off. Using/carrying any notes during the exam is not allowed.
- ✓ All **4 question(s)** are compulsory. Marks allotted for each question are mentioned beside each question.
- ✓ Write your answers inside the indicated boxes (where applicable). If you run out of room, continue on the back page.
- ✓ Symbols have their usual meanings.

Student ID	Answers (1-10)	Answers (11-20)	Answers (21-30)
<div><div></div><div></div><div></div><div></div><div></div><div></div><div></div><div></div></div>	<div>A B C D E</div>	<div>A B C D E</div>	<div>A B C D E</div>
1 <div><div></div><div></div><div></div><div></div><div></div><div></div><div></div><div></div></div>	1 <div><div></div><div></div><div></div><div></div><div></div><div></div></div>	11 <div><div></div><div></div><div></div><div></div><div></div><div></div></div>	21 <div><div></div><div></div><div></div><div></div><div></div><div></div></div>
2 <div><div></div><div></div><div></div><div></div><div></div><div></div><div></div><div></div></div>	2 <div><div></div><div></div><div></div><div></div><div></div><div></div></div>	12 <div><div></div><div></div><div></div><div></div><div></div><div></div></div>	22 <div><div></div><div></div><div></div><div></div><div></div><div></div></div>
3 <div><div></div><div></div><div></div><div></div><div></div><div></div><div></div><div></div></div>	3 <div><div></div><div></div><div></div><div></div><div></div><div></div></div>	13 <div><div></div><div></div><div></div><div></div><div></div><div></div></div>	23 <div><div></div><div></div><div></div><div></div><div></div><div></div></div>
4 <div><div></div><div></div><div></div><div></div><div></div><div></div><div></div><div></div></div>	4 <div><div></div><div></div><div></div><div></div><div></div><div></div></div>	14 <div><div></div><div></div><div></div><div></div><div></div><div></div></div>	24 <div><div></div><div></div><div></div><div></div><div></div><div></div></div>
5 <div><div></div><div></div><div></div><div></div><div></div><div></div><div></div><div></div></div>	5 <div><div></div><div></div><div></div><div></div><div></div><div></div></div>	15 <div><div></div><div></div><div></div><div></div><div></div><div></div></div>	25 <div><div></div><div></div><div></div><div></div><div></div><div></div></div>
6 <div><div></div><div></div><div></div><div></div><div></div><div></div><div></div><div></div></div>			
7 <div><div></div><div></div><div></div><div></div><div></div><div></div><div></div><div></div></div>	<div>A B C D E</div>	<div>A B C D E</div>	<div>A B C D E</div>
8 <div><div></div><div></div><div></div><div></div><div></div><div></div><div></div><div></div></div>	6 <div><div></div><div></div><div></div><div></div><div></div><div></div></div>	16 <div><div></div><div></div><div></div><div></div><div></div><div></div></div>	26 <div><div></div><div></div><div></div><div></div><div></div><div></div></div>
9 <div><div></div><div></div><div></div><div></div><div></div><div></div><div></div><div></div></div>	7 <div><div></div><div></div><div></div><div></div><div></div><div></div></div>	17 <div><div></div><div></div><div></div><div></div><div></div><div></div></div>	27 <div><div></div><div></div><div></div><div></div><div></div><div></div></div>
0 <div><div></div><div></div><div></div><div></div><div></div><div></div><div></div><div></div></div>	8 <div><div></div><div></div><div></div><div></div><div></div><div></div></div>	18 <div><div></div><div></div><div></div><div></div><div></div><div></div></div>	28 <div><div></div><div></div><div></div><div></div><div></div><div></div></div>
Set Identifier	9 <div><div></div><div></div><div></div><div></div><div></div><div></div></div>	19 <div><div></div><div></div><div></div><div></div><div></div><div></div></div>	29 <div><div></div><div></div><div></div><div></div><div></div><div></div></div>
§ <div><div></div><div></div><div></div><div></div><div></div><div></div><div></div><div></div></div>	10 <div><div></div><div></div><div></div><div></div><div></div><div></div></div>	20 <div><div></div><div></div><div></div><div></div><div></div><div></div></div>	30 <div><div></div><div></div><div></div><div></div><div></div><div></div></div>


◇ Question 1 of 4 [CO1] [1 mark]

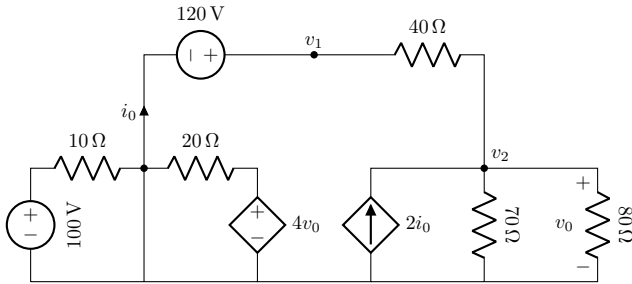

How many nodes are in this circuit?

- (A) 7 (B) 4 (C) 3 (D) 5 (E) 6

◇ Question 2 of 4 [CO3] [2 marks]



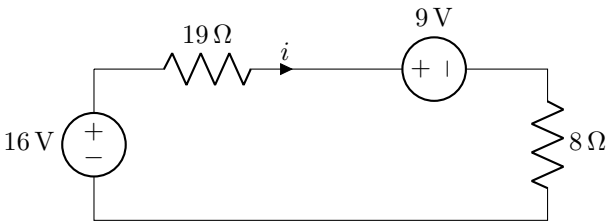


What's the relation between  $v_1$ ,  $v_2$  and  $i$ ?

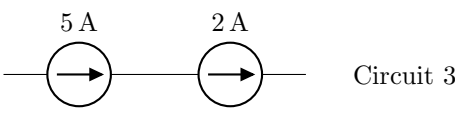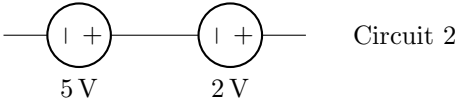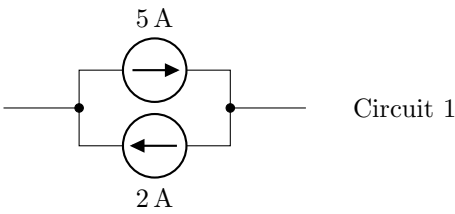- (A)  $-16 - 19i - 9 + 8i = 0$   
(B)  $-16 + 19i - 9 + 8i = 0$   
(C)  $-16 - 19i + 9 + 8i = 0$   
(D)  $-16 + 19i + 9 + 8i = 0$   
(E) None of the above


◇ Question 3 of 4 [CO1] [2 marks]

Which of the following circuits is/are impossible (violates Kirchhoff’s laws)?



- ☐ (A) Circuit 1 & 3
- ☒ (B) **Circuit 1**
- ☐ (C) Circuit 3
- ☐ (D) Circuit 2
- ☐ (E) None of the above

◇ Question 4 of 4 [CO3] [5 marks]

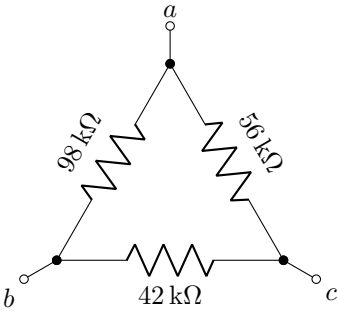

Which of the following statements is true?

- ☐ (A)  $R_{ab} = R_{bc} = R_{ca} = 19.279\text{ k}\Omega$
- ☐ (B)  $R_{ab} = 49\text{ }\Omega, R_{bc} = 33\text{ }\Omega, R_{ca} = 40\text{ }\Omega$
- ☒ (C)  **$R_{ab} = 49\text{ k}\Omega, R_{bc} = 33\text{ k}\Omega, R_{ca} = 40\text{ k}\Omega$**
- ☐ (D)  $R_{ab} = 98\text{ k}\Omega, R_{bc} = 42\text{ k}\Omega, R_{ca} = 56\text{ k}\Omega$
- ☐ (E) None of the above



Brac University

Semester: Fall 2023  
Course Code: CSE250  
Circuits And Electronics  
Section: 18  
Faculty: SDS

Name:

ID:

Set

H




Inspiring Excellence

Assessment: *Class Assignment 1*  
Duration: 1 hour 20 minutes  
Date: September 28, 2023  
Full Marks: 10

- ✓ No washroom breaks. Phones must be turned off. Using/carrying any notes during the exam is not allowed.
- ✓ All **4 question(s)** are compulsory. Marks allotted for each question are mentioned beside each question.
- ✓ Write your answers inside the indicated boxes (where applicable). If you run out of room, continue on the back page.
- ✓ Symbols have their usual meanings.

Student ID	Answers (1-10)	Answers (11-20)	Answers (21-30)
<div><div></div><div></div><div></div><div></div><div></div><div></div><div></div><div></div></div>			
1 <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/>	A B C D E	11 <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/>	21 <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/>
2 <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/>	1 <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/>	12 <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/>	22 <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/>
3 <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/>	2 <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/>	13 <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/>	23 <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/>
4 <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/>	3 <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/>	14 <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/>	24 <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/>
5 <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/>	4 <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/>	15 <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/>	25 <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/>
6 <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/>	5 <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/>		
7 <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/>	A B C D E	16 <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/>	26 <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/>
8 <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/>	6 <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/>	17 <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/>	27 <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/>
9 <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/>	7 <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/>	18 <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/>	28 <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/>
0 <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/>	8 <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/>	19 <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/>	29 <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/>
Set Identifier	9 <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/>	20 <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/>	30 <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/>
§ <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/>	10 <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/>		


◇ Question 1 of 4 [CO3] [5 marks]

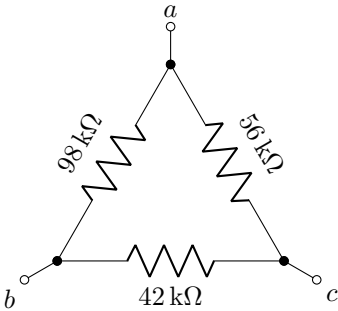

Which of the following statements is true?

- (A)  $R_{ab} = R_{bc} = R_{ca} = 19.279\text{ k}\Omega$
- (B)  $R_{ab} = 49\text{ k}\Omega, R_{bc} = 33\text{ k}\Omega, R_{ca} = 40\text{ k}\Omega$
- (C)  $R_{ab} = 49\text{ }\Omega, R_{bc} = 33\text{ }\Omega, R_{ca} = 40\text{ }\Omega$
- (D)  $R_{ab} = 98\text{ k}\Omega, R_{bc} = 42\text{ k}\Omega, R_{ca} = 56\text{ k}\Omega$
- (E) None of the above

◇ Question 2 of 4 [CO3] [2 marks]

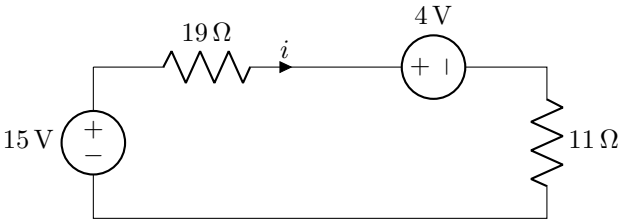


What's the relation between  $v_1$ ,  $v_2$  and  $i$ ?

- (A)  $-15 - 19i + 4 + 11i = 0$
- (B)  $-15 - 19i - 4 + 11i = 0$
- (C)  $-15 + 19i + 4 + 11i = 0$
- (D)  $-15 + 19i - 4 + 11i = 0$
- (E) None of the above



◇ Question 3 of 4 [CO1] [1 mark]



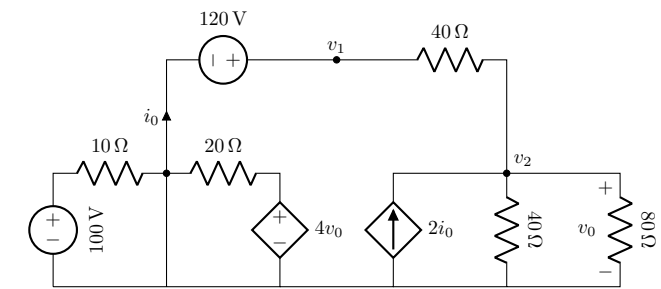


How many nodes are in this circuit?

- ☒ A 5    ☐ B 4    ☐ C 3    ☐ D 6    ☐ E 7

◇ Question 4 of 4 [CO1] [2 marks]

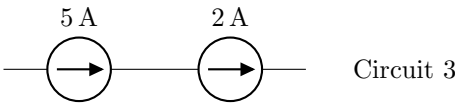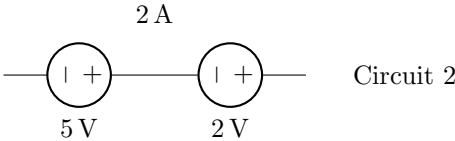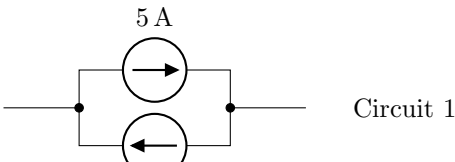Which of the following circuits is/are impossible (violates Kirchhoff’s laws)?



- ☒ A Circuit 1    ☐ B Circuit 1 & 3    ☐ C Circuit 2  
☐ D Circuit 3    ☐ E None of the above

Brac University

Semester: Fall 2023  
Course Code: CSE250  
Circuits And Electronics  
Section: 18  
Faculty: SDS

Name:

Set

I




Inspiring Excellence

Assessment: *Class Assignment 1*  
Duration: 1 hour 20 minutes  
Date: September 28, 2023  
Full Marks: 10

- ✓ No washroom breaks. Phones must be turned off. Using/carrying any notes during the exam is not allowed.
- ✓ All **4 question(s)** are compulsory. Marks allotted for each question are mentioned beside each question.
- ✓ Write your answers inside the indicated boxes (where applicable). If you run out of room, continue on the back page.
- ✓ Symbols have their usual meanings.

Student ID	Answers (1-10)	Answers (11-20)	Answers (21-30)
<div><div></div><div></div><div></div><div></div><div></div><div></div><div></div><div></div></div>			
1 <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/>	A B C D E	A B C D E	A B C D E
2 <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/>	1 <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/>	11 <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/>	21 <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/>
3 <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/>	2 <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/>	12 <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/>	22 <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/>
4 <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/>	3 <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/>	13 <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/>	23 <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/>
5 <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/>	4 <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/>	14 <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/>	24 <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/>
6 <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/>	5 <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/>	15 <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/>	25 <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/>
7 <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/>			
8 <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/>	A B C D E	A B C D E	A B C D E
9 <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/>	6 <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/>	16 <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/>	26 <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/>
0 <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/>	7 <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/>	17 <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/>	27 <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/>
	8 <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/>	18 <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/>	28 <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/>
Set Identifier	9 <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/>	19 <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/>	29 <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/>
§ <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/>	10 <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/>	20 <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/>	30 <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/>


◇ Question 1 of 4 [CO1] [1 mark]

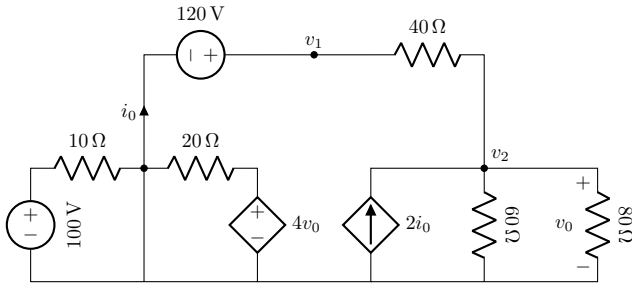

How many nodes are in this circuit?

- (A) 6 (B) 4 (C) 3 (D) 5 (E) 7


◇ Question 2 of 4 [CO3] [5 marks]

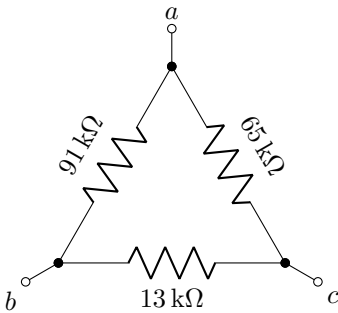

Which of the following statements is true?

- (A)  $R_{ab} = 42\,\Omega, R_{bc} = 12\,\Omega, R_{ca} = 40\,\Omega$   
(B)  $R_{ab} = R_{bc} = R_{ca} = 9.681\,\text{k}\Omega$   
(C)  $R_{ab} = 42\,\text{k}\Omega, R_{bc} = 12\,\text{k}\Omega, R_{ca} = 40\,\text{k}\Omega$   
(D)  $R_{ab} = 91\,\text{k}\Omega, R_{bc} = 13\,\text{k}\Omega, R_{ca} = 65\,\text{k}\Omega$   
(E) None of the above

◇ Question 3 of 4 [CO3] [2 marks]

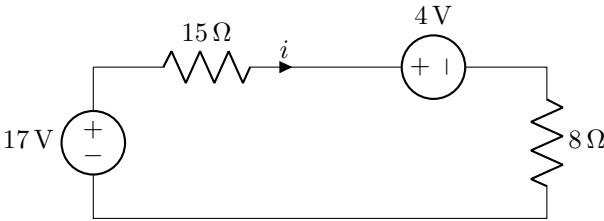


What’s the relation between  $v_1, v_2$  and  $i$ ?

- ☐ (A)  $-17 - 15i - 4 + 8i = 0$
- ☐ (B)  $-17 - 15i + 4 + 8i = 0$
- ☐ (C)  $-17 + 15i - 4 + 8i = 0$
- ☒ (D)  $-17 + 15i + 4 + 8i = 0$
- ☐ (E) None of the above

◇ Question 4 of 4 [CO1] [2 marks]

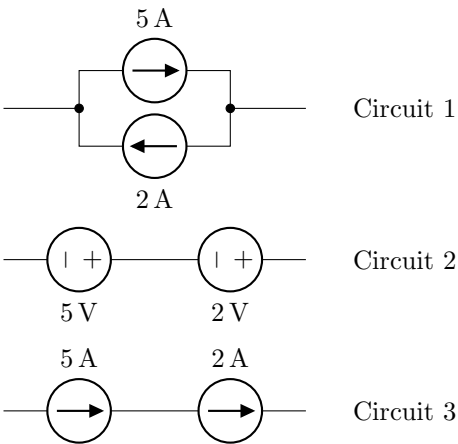Which of the following circuits is/are impossible (violates Kirchhoff’s laws)?



- ☐ (A) Circuit 1 & 3
- ☐ (B) Circuit 2
- ☒ (C) Circuit 1
- ☐ (D) Circuit 3
- ☐ (E) None of the above

Brac University

Semester: Fall 2023  
Course Code: CSE250  
Circuits And Electronics  
Section: 18  
Faculty: SDS

Name:

Set

J



Inspiring Excellence

Assessment: *Class Assignment 1*  
Duration: 1 hour 20 minutes  
Date: September 28, 2023  
Full Marks: 10


- ✓ No washroom breaks. Phones must be turned off. Using/carrying any notes during the exam is not allowed.
- ✓ All **4 question(s)** are compulsory. Marks allotted for each question are mentioned beside each question.
- ✓ Write your answers inside the indicated boxes (where applicable). If you run out of room, continue on the back page.
- ✓ Symbols have their usual meanings.

Student ID	Answers (1-10)	Answers (11-20)	Answers (21-30)
<div><div></div><div></div><div></div><div></div><div></div><div></div><div></div><div></div></div>	<div>A B C D E</div>	<div>A B C D E</div>	<div>A B C D E</div>
1 <div><div></div><div></div><div></div><div></div><div></div><div></div><div></div><div></div></div>	1 <div><div></div><div></div><div></div><div></div><div></div><div></div><div></div><div></div></div>	11 <div><div></div><div></div><div></div><div></div><div></div><div></div><div></div><div></div></div>	21 <div><div></div><div></div><div></div><div></div><div></div><div></div><div></div><div></div></div>
2 <div><div></div><div></div><div></div><div></div><div></div><div></div><div></div><div></div></div>	2 <div><div></div><div></div><div></div><div></div><div></div><div></div><div></div><div></div></div>	12 <div><div></div><div></div><div></div><div></div><div></div><div></div><div></div><div></div></div>	22 <div><div></div><div></div><div></div><div></div><div></div><div></div><div></div><div></div></div>
3 <div><div></div><div></div><div></div><div></div><div></div><div></div><div></div><div></div></div>	3 <div><div></div><div></div><div></div><div></div><div></div><div></div><div></div><div></div></div>	13 <div><div></div><div></div><div></div><div></div><div></div><div></div><div></div><div></div></div>	23 <div><div></div><div></div><div></div><div></div><div></div><div></div><div></div><div></div></div>
4 <div><div></div><div></div><div></div><div></div><div></div><div></div><div></div><div></div></div>	4 <div><div></div><div></div><div></div><div></div><div></div><div></div><div></div><div></div></div>	14 <div><div></div><div></div><div></div><div></div><div></div><div></div><div></div><div></div></div>	24 <div><div></div><div></div><div></div><div></div><div></div><div></div><div></div><div></div></div>
5 <div><div></div><div></div><div></div><div></div><div></div><div></div><div></div><div></div></div>	5 <div><div></div><div></div><div></div><div></div><div></div><div></div><div></div><div></div></div>	15 <div><div></div><div></div><div></div><div></div><div></div><div></div><div></div><div></div></div>	25 <div><div></div><div></div><div></div><div></div><div></div><div></div><div></div><div></div></div>
6 <div><div></div><div></div><div></div><div></div><div></div><div></div><div></div><div></div></div>			
7 <div><div></div><div></div><div></div><div></div><div></div><div></div><div></div><div></div></div>	<div>A B C D E</div>	<div>A B C D E</div>	<div>A B C D E</div>
8 <div><div></div><div></div><div></div><div></div><div></div><div></div><div></div><div></div></div>	6 <div><div></div><div></div><div></div><div></div><div></div><div></div><div></div><div></div></div>	16 <div><div></div><div></div><div></div><div></div><div></div><div></div><div></div><div></div></div>	26 <div><div></div><div></div><div></div><div></div><div></div><div></div><div></div><div></div></div>
9 <div><div></div><div></div><div></div><div></div><div></div><div></div><div></div><div></div></div>	7 <div><div></div><div></div><div></div><div></div><div></div><div></div><div></div><div></div></div>	17 <div><div></div><div></div><div></div><div></div><div></div><div></div><div></div><div></div></div>	27 <div><div></div><div></div><div></div><div></div><div></div><div></div><div></div><div></div></div>
0 <div><div></div><div></div><div></div><div></div><div></div><div></div><div></div><div></div></div>	8 <div><div></div><div></div><div></div><div></div><div></div><div></div><div></div><div></div></div>	18 <div><div></div><div></div><div></div><div></div><div></div><div></div><div></div><div></div></div>	28 <div><div></div><div></div><div></div><div></div><div></div><div></div><div></div><div></div></div>
	9 <div><div></div><div></div><div></div><div></div><div></div><div></div><div></div><div></div></div>	19 <div><div></div><div></div><div></div><div></div><div></div><div></div><div></div><div></div></div>	29 <div><div></div><div></div><div></div><div></div><div></div><div></div><div></div><div></div></div>
	10 <div><div></div><div></div><div></div><div></div><div></div><div></div><div></div><div></div></div>	20 <div><div></div><div></div><div></div><div></div><div></div><div></div><div></div><div></div></div>	30 <div><div></div><div></div><div></div><div></div><div></div><div></div><div></div><div></div></div>

Set Identifier

§


◇ Question 1 of 4 [CO1] [1 mark]

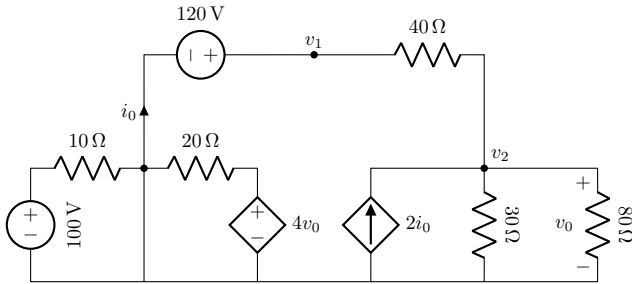

How many nodes are in this circuit?

- (A) 3 (B) 4 (C) 6 (D) 7 (E) 5

◇ Question 2 of 4 [CO3] [5 marks]

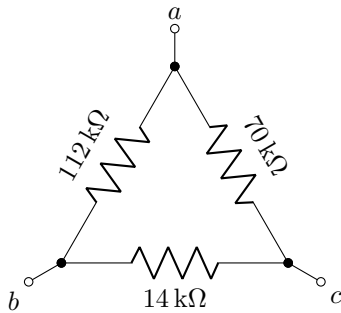


Which of the following statements is true?

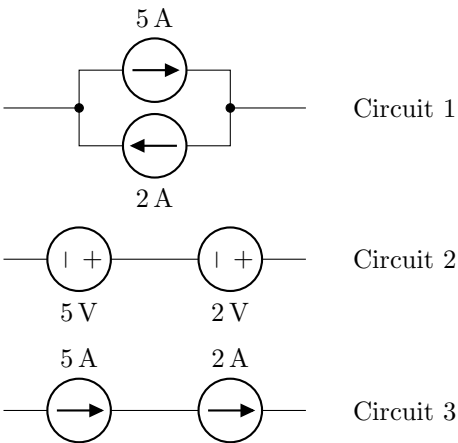- (A)  $R_{ab} = 48\Omega, R_{bc} = 13\Omega, R_{ca} = 45\Omega$   
(B)  $R_{ab} = 48\text{ k}\Omega, R_{bc} = 13\text{ k}\Omega, R_{ca} = 45\text{ k}\Omega$   
(C)  $R_{ab} = R_{bc} = R_{ca} = 10.566\text{ k}\Omega$   
(D)  $R_{ab} = 112\text{ k}\Omega, R_{bc} = 14\text{ k}\Omega, R_{ca} = 70\text{ k}\Omega$   
(E) None of the above


◇ Question 3 of 4 [CO1] [2 marks]

Which of the following circuits is/are impossible (violates Kirchhoff's laws)?



- ☐ (A) Circuit 2
- ☐ (B) Circuit 3
- ☐ (C) Circuit 1 & 3
- ☒ (D) Circuit 1
- ☐ (E) None of the above

◇ Question 4 of 4 [CO3] [2 marks]

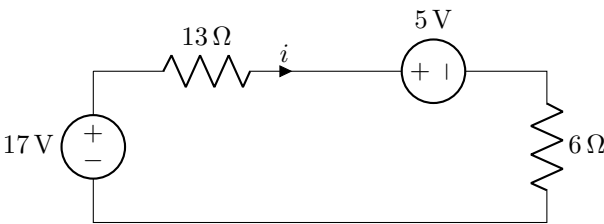

What's the relation between  $v_1$ ,  $v_2$  and  $i$ ?

- ☐ (A)  $-17 + 13i - 5 + 6i = 0$
- ☐ (B)  $-17 - 13i + 5 + 6i = 0$
- ☐ (C)  $-17 - 13i - 5 + 6i = 0$
- ☒ (D)  $-17 + 13i + 5 + 6i = 0$
- ☐ (E) None of the above



