

Brac University

Semester: Fall 2023
Course Code: CSE250
Circuits And Electronics
Section: 18
Faculty: SDS

Name:

Set

A




Inspiring Excellence

Assessment: *Class Assignment 1*
Duration: 1 hour 20 minutes
Date: September 28, 2023
Full Marks: 10

- ✓ No washroom breaks. Phones must be turned off. Using/carrying any notes during the exam is not allowed.
- ✓ All **4 questions** are compulsory. Marks allotted for each question are mentioned beside each question.
- ✓ Write your answers inside the indicated boxes (where applicable). If you run out of room, continue on the back page.
- ✓ Symbols have their usual meanings.

Student ID	Answers (1-10)	Answers (11-20)	Answers (21-30)
<div><div></div><div></div><div></div><div></div><div></div><div></div><div></div><div></div></div>			
1 <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/>	A B C D E	11 <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/>	21 <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/>
2 <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/>	1 <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/>	12 <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/>	22 <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/>
3 <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/>	2 <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/>	13 <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/>	23 <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/>
4 <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/>	3 <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/>	14 <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/>	24 <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/>
5 <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/>	4 <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/>	15 <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/>	25 <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/>
6 <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/>	5 <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/>		
7 <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/>	A B C D E	16 <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/>	26 <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/>
8 <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/>	6 <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/>	17 <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/>	27 <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/>
9 <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/>	7 <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/>	18 <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/>	28 <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/>
0 <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/>	8 <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/>	19 <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/>	29 <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/>
Set Identifier	9 <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/>	20 <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/>	30 <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/>
§ <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/>	10 <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/>		

◇ Question 1 of 4 [CO3] [5 marks]

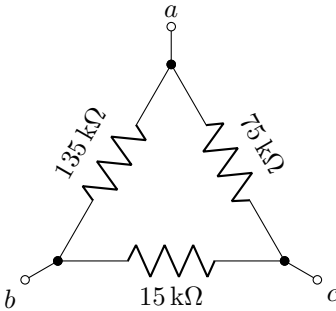


Which of the following statements is true?

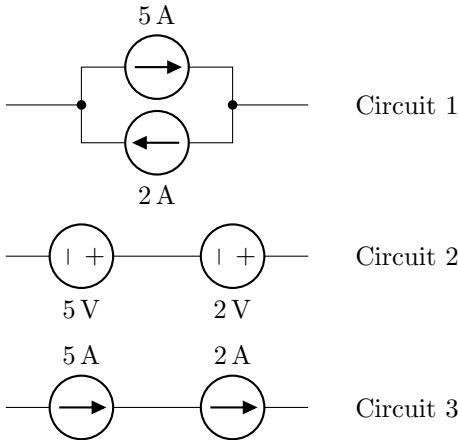- (A) $R_{ab} = R_{bc} = R_{ca} = 11.441\text{ k}\Omega$
- (B) $R_{ab} = 135\text{ k}\Omega$, $R_{bc} = 15\text{ k}\Omega$, $R_{ca} = 75\text{ k}\Omega$
- (C) $R_{ab} = 54\text{ k}\Omega$, $R_{bc} = 14\text{ k}\Omega$, $R_{ca} = 50\text{ k}\Omega$
- (D) $R_{ab} = 54\text{ }\Omega$, $R_{bc} = 14\text{ }\Omega$, $R_{ca} = 50\text{ }\Omega$
- (E) None of the above


◇ Question 2 of 4 [CO1] [2 marks]

Which of the following circuits is/are impossible (violates Kirchhoff's laws)?




- (A) Circuit 2
- (B) Circuit 3
- (C) Circuit 1
- (D) Circuit 1 & 3
- (E) None of the above

◇ Question 3 of 4 [CO3] [2 marks]

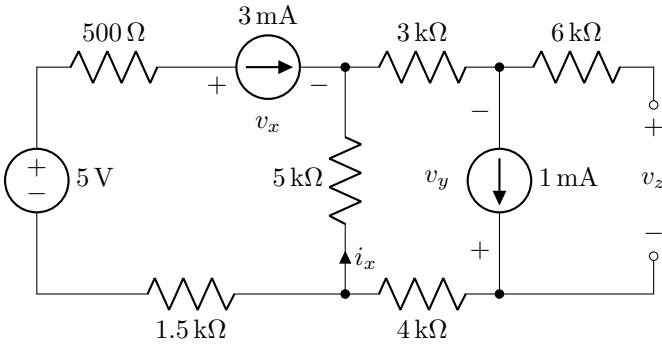

- (A) b
- (B) a
- (C) c

◇ Question 4 of 4 [CO1] [1 mark]

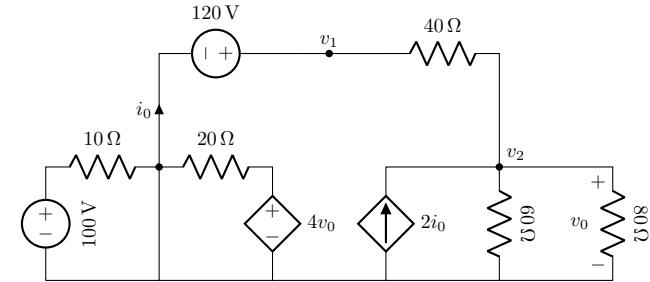

How many nodes are in this circuit?

- (A) 7
- (B) 3
- (C) 5
- (D) 4
- (E) 6

Brac University

Semester: Fall 2023
Course Code: CSE250
Circuits And Electronics
Section: 18
Faculty: SDS

Name:

ID:

Set

B




Inspiring Excellence

Assessment: *Class Assignment 1*
Duration: 1 hour 20 minutes
Date: September 28, 2023
Full Marks: 10

- ✓ No washroom breaks. Phones must be turned off. Using/carrying any notes during the exam is not allowed.
- ✓ All **4 questions** are compulsory. Marks allotted for each question are mentioned beside each question.
- ✓ Write your answers inside the indicated boxes (where applicable). If you run out of room, continue on the back page.
- ✓ Symbols have their usual meanings.

Student ID	Answers (1-10)	Answers (11-20)	Answers (21-30)
<div><div></div><div></div><div></div><div></div><div></div><div></div><div></div><div></div></div>			
1 <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/>	A B C D E		
2 <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/>	1 <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/>	11 <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/>	21 <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/>
3 <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/>	2 <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/>	12 <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/>	22 <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/>
4 <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/>	3 <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/>	13 <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/>	23 <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/>
5 <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/>	4 <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/>	14 <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/>	24 <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/>
6 <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/>	5 <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/>	15 <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/>	25 <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/>
7 <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/>			
8 <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/>	A B C D E	A B C D E	A B C D E
9 <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/>	6 <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/>	16 <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/>	26 <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/>
0 <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/>	7 <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/>	17 <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/>	27 <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/>
	8 <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/>	18 <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/>	28 <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/>
Set Identifier	9 <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/>	19 <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/>	29 <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/>
§ <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/>	10 <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/>	20 <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/>	30 <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/>


◇ Question 1 of 4 [CO3] [2 marks]

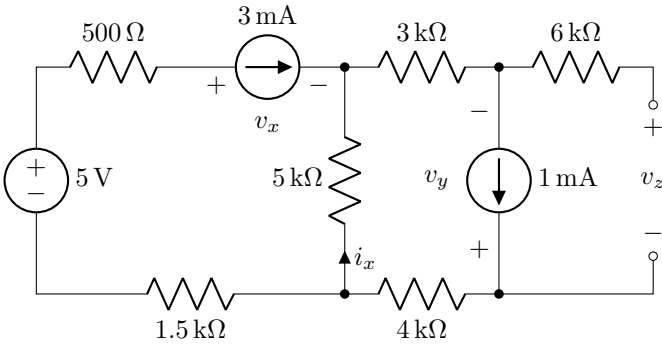

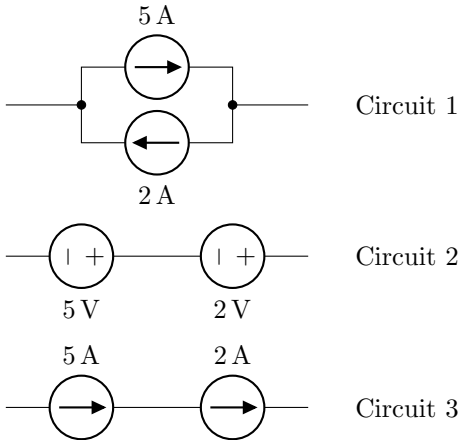- (A) c
(B) b
(C) a


◇ Question 2 of 4 [CO1] [2 marks]

Which of the following circuits is/are impossible (violates Kirchhoff's laws)?



- (A) Circuit 3
(B) Circuit 1 & 3
(C) Circuit 1
(D) Circuit 2
(E) None of the above


◇ Question 3 of 4 [CO1] [1 mark]

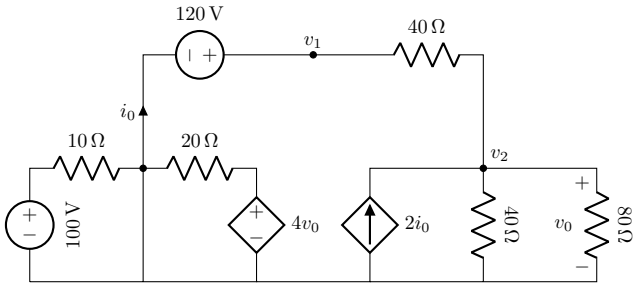

How many nodes are in this circuit?

- (A) 6 (B) 5 (C) 3 (D) 4 (E) 7

◇ Question 4 of 4 [CO3] [5 marks]

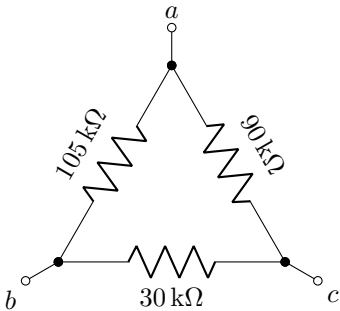

Which of the following statements is true?

- (A) $R_{ab} = 105\text{ k}\Omega, R_{bc} = 30\text{ k}\Omega, R_{ca} = 90\text{ k}\Omega$
(B) $R_{ab} = 56\text{ }\Omega, R_{bc} = 26\text{ }\Omega, R_{ca} = 54\text{ }\Omega$
(C) $R_{ab} = 56\text{ k}\Omega, R_{bc} = 26\text{ k}\Omega, R_{ca} = 54\text{ k}\Omega$
(D) $R_{ab} = R_{bc} = R_{ca} = 18.529\text{ k}\Omega$
(E) None of the above

Brac University

Semester: Fall 2023

Course Code: CSE250

Circuits And Electronics

Section: 18

Faculty: SDS

Name:

ID:

Set

C



Inspiring Excellence

Assessment: *Class Assignment 1*

Duration: 1 hour 20 minutes


Date: September 28, 2023

Full Marks: 10

- ✓ No washroom breaks. Phones must be turned off. Using/carrying any notes during the exam is not allowed.
- ✓ All **4 questions** are compulsory. Marks allotted for each question are mentioned beside each question.
- ✓ Write your answers inside the indicated boxes (where applicable). If you run out of room, continue on the back page.
- ✓ Symbols have their usual meanings.

Student ID	Answers (1-10)	Answers (11-20)	Answers (21-30)
<div><div></div><div></div><div></div><div></div><div></div><div></div><div></div><div></div></div>			
1 <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/>	A B C D E	11 <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/>	21 <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/>
2 <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/>	1 <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/>	12 <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/>	22 <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/>
3 <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/>	2 <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/>	13 <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/>	23 <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/>
4 <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/>	3 <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/>	14 <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/>	24 <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/>
5 <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/>	4 <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/>	15 <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/>	25 <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/>
6 <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/>	5 <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/>		
7 <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/>	A B C D E	16 <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/>	26 <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/>
8 <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/>	6 <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/>	17 <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/>	27 <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/>
9 <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/>	7 <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/>	18 <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/>	28 <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/>
0 <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/>	8 <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/>	19 <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/>	29 <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/>
Set Identifier	9 <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/>	20 <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/>	30 <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/>
§ <input checked="" type="radio"/> <input checked="" type="radio"/> <input checked="" type="radio"/> <input checked="" type="radio"/> <input checked="" type="radio"/> <input checked="" type="radio"/> <input type="radio"/> <input type="radio"/>	10 <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/>		

◇ Question 1 of 4 [CO1] [1 mark]

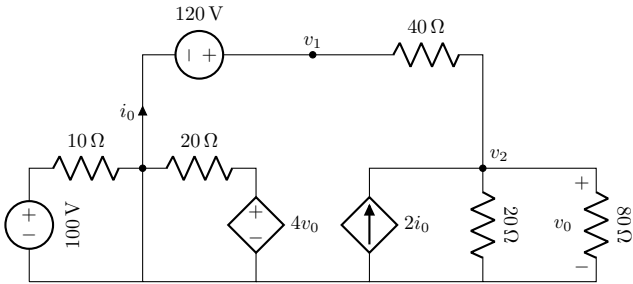


How many nodes are in this circuit?

- ☒ A 5 ☐ B 4 ☐ C 7 ☐ D 6 ☐ E 3


◇ Question 2 of 4 [CO1] [2 marks]

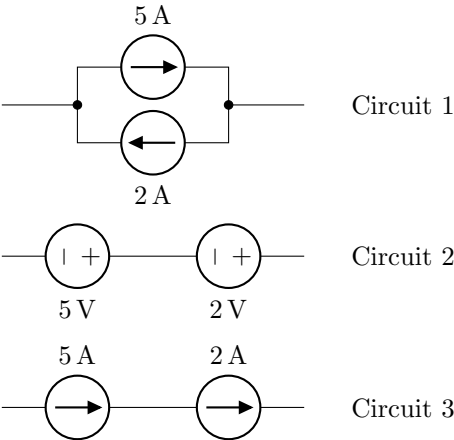Which of the following circuits is/are impossible (violates Kirchhoff's laws)?



- ☐ A Circuit 2 ☒ B Circuit 1 ☐ C Circuit 3
☐ D Circuit 1 & 3 ☐ E None of the above


◇ Question 3 of 4 [CO3] [2 marks]

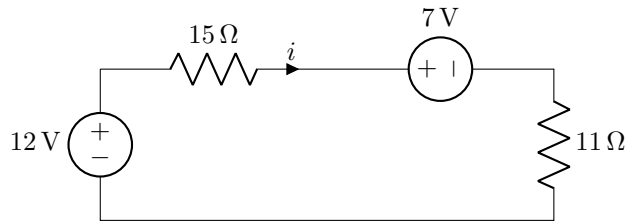

What's the relation between v_1, v_2 and i ?

- (A) $-12 - 15i + 7 + 11i = 0$
- (B) $-12 + 15i - 7 + 11i = 0$
- (C) $-12 + 15i + 7 + 11i = 0$
- (D) $-12 - 15i - 7 + 11i = 0$
- (E) None of the above

◇ Question 4 of 4 [CO3] [5 marks]

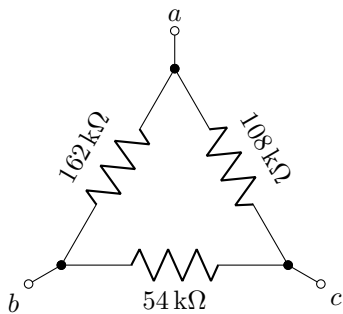

Which of the following statements is true?

- (A) $R_{ab} = R_{bc} = R_{ca} = 29.455\text{ k}\Omega$
- (B) $R_{ab} = 81\text{ }\Omega, R_{bc} = 45\text{ }\Omega, R_{ca} = 72\text{ }\Omega$
- (C) $R_{ab} = 162\text{ k}\Omega, R_{bc} = 54\text{ k}\Omega, R_{ca} = 108\text{ k}\Omega$
- (D) $R_{ab} = 81\text{ k}\Omega, R_{bc} = 45\text{ k}\Omega, R_{ca} = 72\text{ k}\Omega$
- (E) None of the above

Brac University

Semester: Fall 2023

Course Code: CSE250

Circuits And Electronics

Section: 18

Faculty: SDS

Name:

ID:

Set

D



Inspiring Excellence

Assessment: *Class Assignment 1*

Duration: 1 hour 20 minutes


Date: September 28, 2023

Full Marks: 10

- ✓ No washroom breaks. Phones must be turned off. Using/carrying any notes during the exam is not allowed.
- ✓ All **4 questions** are compulsory. Marks allotted for each question are mentioned beside each question.
- ✓ Write your answers inside the indicated boxes (where applicable). If you run out of room, continue on the back page.
- ✓ Symbols have their usual meanings.


Student ID	Answers (1-10)	Answers (11-20)	Answers (21-30)
<div><div></div><div></div><div></div><div></div><div></div><div></div><div></div><div></div></div>			
1 <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/>	A B C D E	A B C D E	A B C D E
2 <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/>	1 <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/>	11 <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/>	21 <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/>
3 <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/>	2 <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/>	12 <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/>	22 <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/>
4 <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/>	3 <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/>	13 <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/>	23 <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/>
5 <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/>	4 <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/>	14 <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/>	24 <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/>
6 <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/>	5 <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/>	15 <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/>	25 <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/>
7 <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/>			
8 <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/>	A B C D E	A B C D E	A B C D E
9 <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/>	6 <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/>	16 <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/>	26 <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/>
0 <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/>	7 <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/>	17 <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/>	27 <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/>
	8 <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/>	18 <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/>	28 <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/>
Set Identifier	9 <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/>	19 <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/>	29 <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/>
§ <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/>	10 <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/>	20 <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/>	30 <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/>

◇ Question 1 of 4 [CO3] [5 marks]

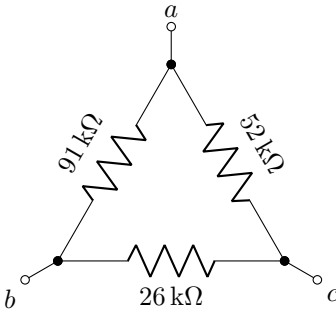

- Which of the following statements is true?
- (A) $R_{ab} = 91\text{ k}\Omega$, $R_{bc} = 26\text{ k}\Omega$, $R_{ca} = 52\text{ k}\Omega$
 - (B) $R_{ab} = 42\text{ k}\Omega$, $R_{bc} = 22\text{ k}\Omega$, $R_{ca} = 36\text{ k}\Omega$
 - (C) $R_{ab} = 42\text{ }\Omega$, $R_{bc} = 22\text{ }\Omega$, $R_{ca} = 36\text{ }\Omega$
 - (D) $R_{ab} = R_{bc} = R_{ca} = 14.56\text{ k}\Omega$
 - (E) None of the above

◇ Question 2 of 4 [CO1] [1 mark]



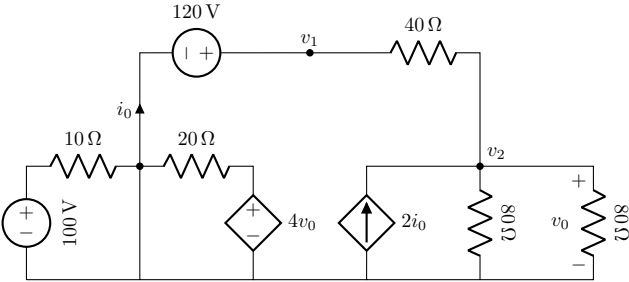


How many nodes are in this circuit?

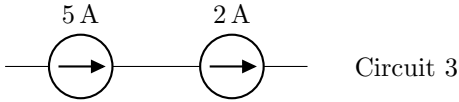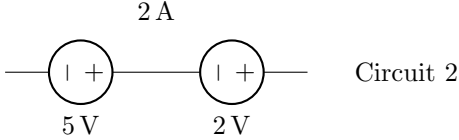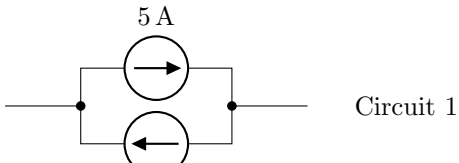- (A) 3
- (B) 7
- (C) 4
- (D) 5
- (E) 6


◇ Question 3 of 4 [CO1] [2 marks]

Which of the following circuits is/are impossible (violates Kirchhoff’s laws)?



- ☐ A
- Circuit 2
- ☐ B
- Circuit 3
- ☒ C
- Circuit 1**
- ☐ D
- Circuit 1 & 3
- ☐ E
- None of the above

◇ Question 4 of 4 [CO3] [2 marks]

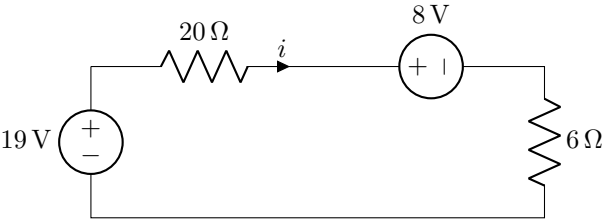

What’s the relation between v_1, v_2 and i ?

- ☒ A
- $-19 + 20i + 8 + 6i = 0$**
- ☐ B
- $-19 - 20i - 8 + 6i = 0$
- ☐ C
- $-19 - 20i + 8 + 6i = 0$
- ☐ D
- $-19 + 20i - 8 + 6i = 0$
- ☐ E
- None of the above

Brac University

Semester: Fall 2023

Course Code: CSE250

Circuits And Electronics

Section: 18

Faculty: SDS

Name:

ID:

Set

E



Inspiring Excellence

Assessment: *Class Assignment 1*

Duration: 1 hour 20 minutes


Date: September 28, 2023

Full Marks: 10

- ✓ No washroom breaks. Phones must be turned off. Using/carrying any notes during the exam is not allowed.
- ✓ All **4 questions** are compulsory. Marks allotted for each question are mentioned beside each question.
- ✓ Write your answers inside the indicated boxes (where applicable). If you run out of room, continue on the back page.
- ✓ Symbols have their usual meanings.

Student ID	Answers (1-10)	Answers (11-20)	Answers (21-30)
<div><div></div><div></div><div></div><div></div><div></div><div></div><div></div><div></div></div>			
1 <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/>	A B C D E	A B C D E	A B C D E
2 <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/>	1 <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/>	11 <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/>	21 <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/>
3 <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/>	2 <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/>	12 <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/>	22 <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/>
4 <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/>	3 <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/>	13 <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/>	23 <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/>
5 <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/>	4 <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/>	14 <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/>	24 <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/>
6 <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/>	5 <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/>	15 <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/>	25 <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/>
7 <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/>			
8 <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/>	A B C D E	A B C D E	A B C D E
9 <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/>	6 <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/>	16 <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/>	26 <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/>
0 <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/>	7 <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/>	17 <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/>	27 <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/>
	8 <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/>	18 <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/>	28 <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/>
Set Identifier	9 <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/>	19 <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/>	29 <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/>
§ <input checked="" type="radio"/> <input checked="" type="radio"/> <input checked="" type="radio"/> <input checked="" type="radio"/> <input checked="" type="radio"/> <input type="radio"/> <input checked="" type="radio"/> <input type="radio"/>	10 <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/>	20 <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/>	30 <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/>

◇ Question 1 of 4 [CO1] [1 mark]

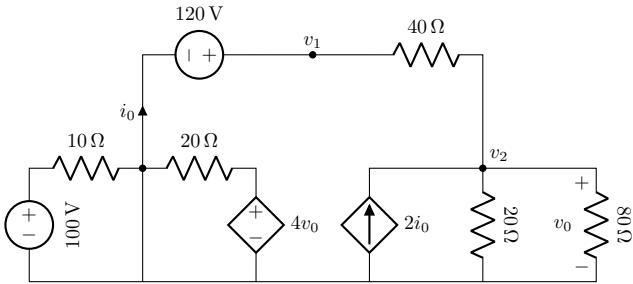


How many nodes are in this circuit?

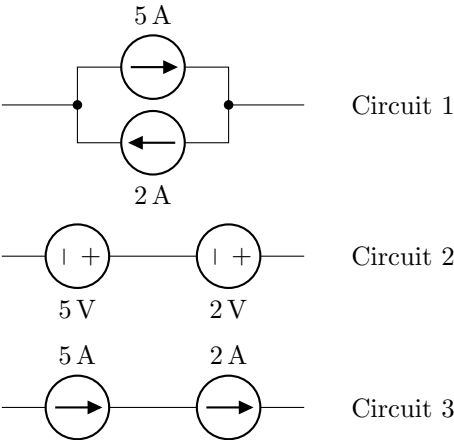- (A) 4 (B) 5 (C) 6 (D) 3 (E) 7


◇ Question 2 of 4 [CO1] [2 marks]

Which of the following circuits is/are impossible (violates Kirchhoff's laws)?



- (A) Circuit 1 (B) Circuit 3 (C) Circuit 1 & 3
(D) Circuit 2 (E) None of the above


◇ Question 3 of 4 [CO3] [5 marks]

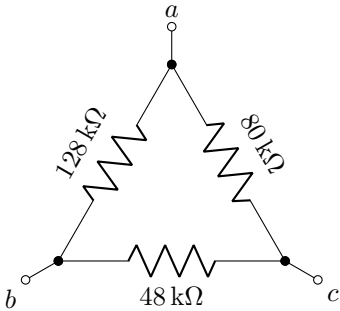

Which of the following statements is true?

- (A) $R_{ab} = 64\ \Omega, R_{bc} = 39\ \Omega, R_{ca} = 55\ \Omega$
- (B) $R_{ab} = 128\ \text{k}\Omega, R_{bc} = 48\ \text{k}\Omega, R_{ca} = 80\ \text{k}\Omega$
- (C) **$R_{ab} = 64\ \text{k}\Omega, R_{bc} = 39\ \text{k}\Omega, R_{ca} = 55\ \text{k}\Omega$**
- (D) $R_{ab} = R_{bc} = R_{ca} = 24.304\ \text{k}\Omega$
- (E) None of the above

◇ Question 4 of 4 [CO3] [2 marks]

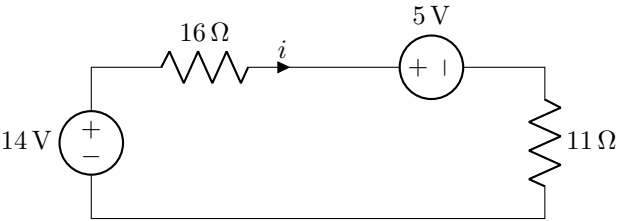

What's the relation between v_1, v_2 and i ?

- (A) $-14 + 16i - 5 + 11i = 0$
- (B) $-14 - 16i + 5 + 11i = 0$
- (C) **$-14 + 16i + 5 + 11i = 0$**
- (D) $-14 - 16i - 5 + 11i = 0$
- (E) None of the above

Brac University

Semester: Fall 2023

Course Code: CSE250

Circuits And Electronics

Section: 18

Faculty: SDS

Name:

ID:

Set

F



Inspiring Excellence

Assessment: *Class Assignment 1*

Duration: 1 hour 20 minutes

Date: September 28, 2023

Full Marks: 10


- ✓ No washroom breaks. Phones must be turned off. Using/carrying any notes during the exam is not allowed.
- ✓ All **4 questions** are compulsory. Marks allotted for each question are mentioned beside each question.
- ✓ Write your answers inside the indicated boxes (where applicable). If you run out of room, continue on the back page.
- ✓ Symbols have their usual meanings.

Student ID	Answers (1-10)	Answers (11-20)	Answers (21-30)
<div><div></div><div></div><div></div><div></div><div></div><div></div><div></div><div></div></div>	<div>A B C D E</div>	<div>A B C D E</div>	<div>A B C D E</div>
1 <div><div></div><div></div><div></div><div></div><div></div><div></div><div></div><div></div></div>	1 <div><div></div><div></div><div></div><div></div><div></div><div></div></div>	11 <div><div></div><div></div><div></div><div></div><div></div><div></div></div>	21 <div><div></div><div></div><div></div><div></div><div></div><div></div></div>
2 <div><div></div><div></div><div></div><div></div><div></div><div></div><div></div><div></div></div>	2 <div><div></div><div></div><div></div><div></div><div></div><div></div></div>	12 <div><div></div><div></div><div></div><div></div><div></div><div></div></div>	22 <div><div></div><div></div><div></div><div></div><div></div><div></div></div>
3 <div><div></div><div></div><div></div><div></div><div></div><div></div><div></div><div></div></div>	3 <div><div></div><div></div><div></div><div></div><div></div><div></div></div>	13 <div><div></div><div></div><div></div><div></div><div></div><div></div></div>	23 <div><div></div><div></div><div></div><div></div><div></div><div></div></div>
4 <div><div></div><div></div><div></div><div></div><div></div><div></div><div></div><div></div></div>	4 <div><div></div><div></div><div></div><div></div><div></div><div></div></div>	14 <div><div></div><div></div><div></div><div></div><div></div><div></div></div>	24 <div><div></div><div></div><div></div><div></div><div></div><div></div></div>
5 <div><div></div><div></div><div></div><div></div><div></div><div></div><div></div><div></div></div>	5 <div><div></div><div></div><div></div><div></div><div></div><div></div></div>	15 <div><div></div><div></div><div></div><div></div><div></div><div></div></div>	25 <div><div></div><div></div><div></div><div></div><div></div><div></div></div>
6 <div><div></div><div></div><div></div><div></div><div></div><div></div><div></div><div></div></div>			
7 <div><div></div><div></div><div></div><div></div><div></div><div></div><div></div><div></div></div>	<div>A B C D E</div>	<div>A B C D E</div>	<div>A B C D E</div>
8 <div><div></div><div></div><div></div><div></div><div></div><div></div><div></div><div></div></div>	6 <div><div></div><div></div><div></div><div></div><div></div><div></div></div>	16 <div><div></div><div></div><div></div><div></div><div></div><div></div></div>	26 <div><div></div><div></div><div></div><div></div><div></div><div></div></div>
9 <div><div></div><div></div><div></div><div></div><div></div><div></div><div></div><div></div></div>	7 <div><div></div><div></div><div></div><div></div><div></div><div></div></div>	17 <div><div></div><div></div><div></div><div></div><div></div><div></div></div>	27 <div><div></div><div></div><div></div><div></div><div></div><div></div></div>
0 <div><div></div><div></div><div></div><div></div><div></div><div></div><div></div><div></div></div>	8 <div><div></div><div></div><div></div><div></div><div></div><div></div></div>	18 <div><div></div><div></div><div></div><div></div><div></div><div></div></div>	28 <div><div></div><div></div><div></div><div></div><div></div><div></div></div>
	9 <div><div></div><div></div><div></div><div></div><div></div><div></div></div>	19 <div><div></div><div></div><div></div><div></div><div></div><div></div></div>	29 <div><div></div><div></div><div></div><div></div><div></div><div></div></div>
	10 <div><div></div><div></div><div></div><div></div><div></div><div></div></div>	20 <div><div></div><div></div><div></div><div></div><div></div><div></div></div>	30 <div><div></div><div></div><div></div><div></div><div></div><div></div></div>

Set Identifier

§

◇ Question 1 of 4 [CO1] [1 mark]

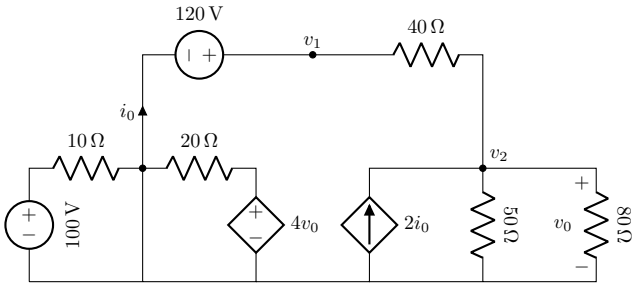

How many nodes are in this circuit?

- A

 5

B

 6

C

 7

D


 4

E

 3

◇ Question 2 of 4 [CO1] [2 marks]

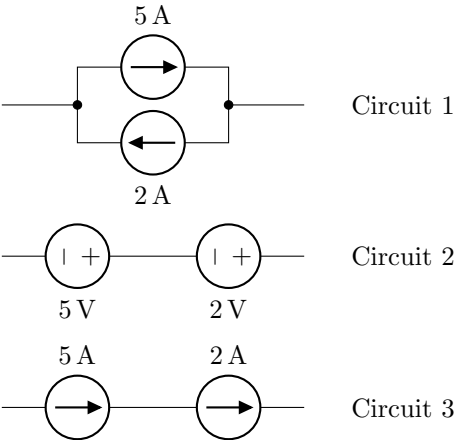Which of the following circuits is/are impossible (violates Kirchhoff's laws)?



- A

 Circuit 1

B

 Circuit 1 & 3

C

 Circuit 3


D

 Circuit 2

E

 None of the above


◇ Question 3 of 4 [CO3] [2 marks]

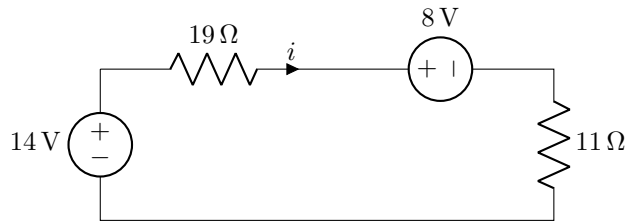

What's the relation between v_1, v_2 and i ?

- (A) $-14 - 19i + 8 + 11i = 0$
- (B) $-14 + 19i - 8 + 11i = 0$
- (C) $-14 - 19i - 8 + 11i = 0$
- (D) $-14 + 19i + 8 + 11i = 0$
- (E) None of the above

◇ Question 4 of 4 [CO3] [5 marks]

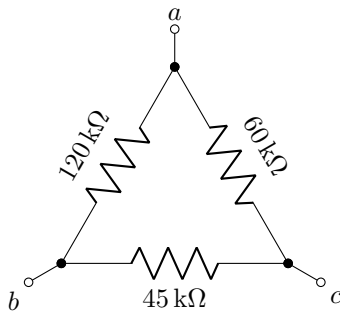

Which of the following statements is true?

- (A) $R_{ab} = 56\text{ k}\Omega, R_{bc} = 36\text{ k}\Omega, R_{ca} = 44\text{ k}\Omega$
- (B) $R_{ab} = R_{bc} = R_{ca} = 21.176\text{ k}\Omega$
- (C) $R_{ab} = 120\text{ k}\Omega, R_{bc} = 45\text{ k}\Omega, R_{ca} = 60\text{ k}\Omega$
- (D) $R_{ab} = 56\text{ }\Omega, R_{bc} = 36\text{ }\Omega, R_{ca} = 44\text{ }\Omega$
- (E) None of the above

Brac University

Semester: Fall 2023
Course Code: CSE250
Circuits And Electronics
Section: 18
Faculty: SDS

Name:

ID:

Set

G




Inspiring Excellence

Assessment: *Class Assignment 1*
Duration: 1 hour 20 minutes
Date: September 28, 2023
Full Marks: 10

- ✓ No washroom breaks. Phones must be turned off. Using/carrying any notes during the exam is not allowed.
- ✓ All **4 questions** are compulsory. Marks allotted for each question are mentioned beside each question.
- ✓ Write your answers inside the indicated boxes (where applicable). If you run out of room, continue on the back page.
- ✓ Symbols have their usual meanings.

Student ID	Answers (1-10)	Answers (11-20)	Answers (21-30)
<div><div></div><div></div><div></div><div></div><div></div><div></div><div></div><div></div></div>			
1 <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/>	A B C D E	A B C D E	A B C D E
2 <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/>	1 <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/>	11 <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/>	21 <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/>
3 <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/>	2 <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/>	12 <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/>	22 <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/>
4 <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/>	3 <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/>	13 <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/>	23 <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/>
5 <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/>	4 <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/>	14 <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/>	24 <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/>
6 <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/>	5 <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/>	15 <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/>	25 <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/>
7 <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/>			
8 <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/>	A B C D E	A B C D E	A B C D E
9 <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/>	6 <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/>	16 <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/>	26 <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/>
0 <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/>	7 <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/>	17 <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/>	27 <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/>
	8 <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/>	18 <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/>	28 <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/>
Set Identifier	9 <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/>	19 <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/>	29 <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/>
§ <input checked="" type="radio"/> <input checked="" type="radio"/> <input checked="" type="radio"/> <input checked="" type="radio"/> <input checked="" type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/>	10 <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/>	20 <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/>	30 <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/>


◇ Question 1 of 4 [CO1] [1 mark]

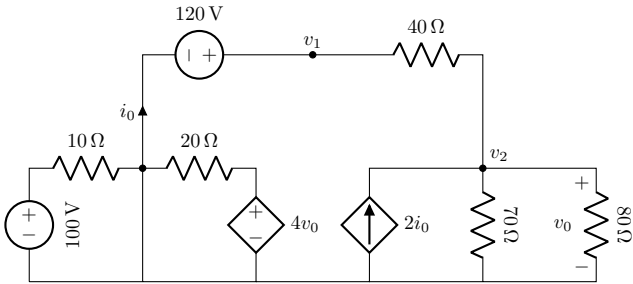

How many nodes are in this circuit?

- (A) 7 (B) 4 (C) 3 (D) 5 (E) 6

◇ Question 2 of 4 [CO3] [2 marks]

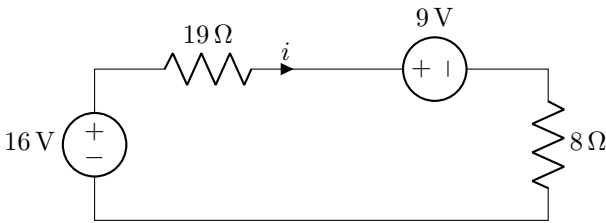


What's the relation between v_1 , v_2 and i ?

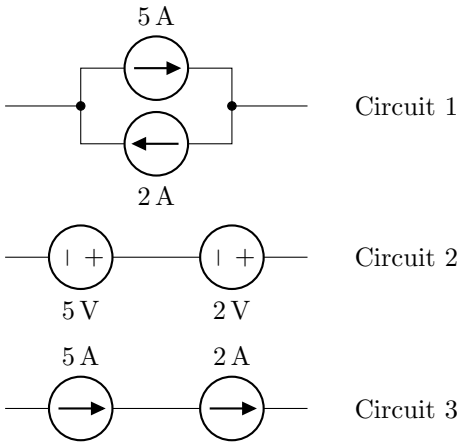- (A) $-16 - 19i - 9 + 8i = 0$
(B) $-16 + 19i - 9 + 8i = 0$
(C) $-16 - 19i + 9 + 8i = 0$
(D) $-16 + 19i + 9 + 8i = 0$
(E) None of the above


◇ Question 3 of 4 [CO1] [2 marks]

Which of the following circuits is/are impossible (violates Kirchhoff’s laws)?



- ☐ A
- Circuit 1 & 3
- ☒ B
- Circuit 1**
- ☐ C
- Circuit 3
- ☐ D
- Circuit 2
- ☐ E
- None of the above

◇ Question 4 of 4 [CO3] [5 marks]

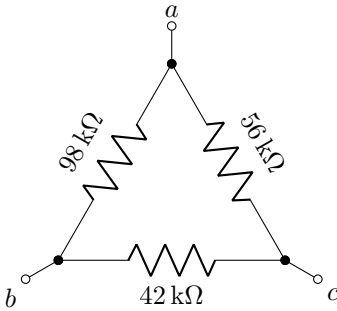

Which of the following statements is true?

- ☐ A
- $R_{ab} = R_{bc} = R_{ca} = 19.279\text{ k}\Omega$
- ☐ B
- $R_{ab} = 49\text{ }\Omega, R_{bc} = 33\text{ }\Omega, R_{ca} = 40\text{ }\Omega$
- ☒ C
- $R_{ab} = 49\text{ k}\Omega, R_{bc} = 33\text{ k}\Omega, R_{ca} = 40\text{ k}\Omega$**
- ☐ D
- $R_{ab} = 98\text{ k}\Omega, R_{bc} = 42\text{ k}\Omega, R_{ca} = 56\text{ k}\Omega$
- ☐ E
- None of the above

Brac University

Semester: Fall 2023

Course Code: CSE250

Circuits And Electronics

Section: 18

Faculty: SDS

Name:

ID:

Set

H



Inspiring Excellence

Assessment: *Class Assignment 1*

Duration: 1 hour 20 minutes


Date: September 28, 2023

Full Marks: 10

- ✓ No washroom breaks. Phones must be turned off. Using/carrying any notes during the exam is not allowed.
- ✓ All **4 questions** are compulsory. Marks allotted for each question are mentioned beside each question.
- ✓ Write your answers inside the indicated boxes (where applicable). If you run out of room, continue on the back page.
- ✓ Symbols have their usual meanings.

Student ID	Answers (1-10)	Answers (11-20)	Answers (21-30)
<div><div></div><div></div><div></div><div></div><div></div><div></div><div></div><div></div></div>			
1 <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/>	A B C D E	11 <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/>	21 <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/>
2 <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/>	1 <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/>	12 <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/>	22 <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/>
3 <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/>	2 <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/>	13 <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/>	23 <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/>
4 <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/>	3 <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/>	14 <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/>	24 <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/>
5 <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/>	4 <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/>	15 <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/>	25 <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/>
6 <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/>	5 <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/>		
7 <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/>	A B C D E	16 <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/>	26 <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/>
8 <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/>	6 <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/>	17 <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/>	27 <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/>
9 <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/>	7 <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/>	18 <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/>	28 <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/>
0 <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/>	8 <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/>	19 <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/>	29 <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/>
Set Identifier	9 <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/>	20 <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/>	30 <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/>
§ <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/>	10 <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/>		


◇ Question 1 of 4 [CO3] [5 marks]

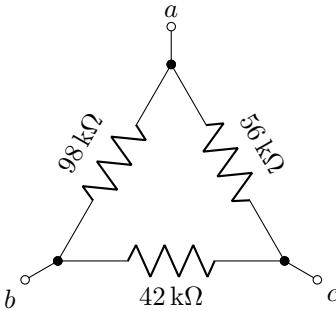

Which of the following statements is true?

- (A) $R_{ab} = R_{bc} = R_{ca} = 19.279\text{ k}\Omega$
- (B) $R_{ab} = 49\text{ k}\Omega, R_{bc} = 33\text{ k}\Omega, R_{ca} = 40\text{ k}\Omega$
- (C) $R_{ab} = 49\text{ }\Omega, R_{bc} = 33\text{ }\Omega, R_{ca} = 40\text{ }\Omega$
- (D) $R_{ab} = 98\text{ k}\Omega, R_{bc} = 42\text{ k}\Omega, R_{ca} = 56\text{ k}\Omega$
- (E) None of the above


◇ Question 2 of 4 [CO3] [2 marks]

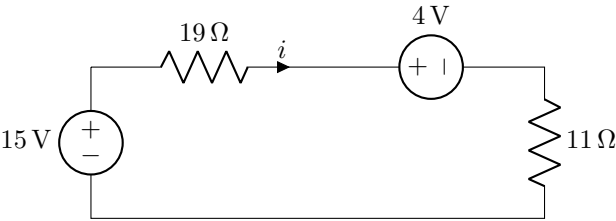

What's the relation between v_1, v_2 and i ?

- (A) $-15 - 19i + 4 + 11i = 0$
- (B) $-15 - 19i - 4 + 11i = 0$
- (C) $-15 + 19i + 4 + 11i = 0$
- (D) $-15 + 19i - 4 + 11i = 0$
- (E) None of the above

◇ Question 3 of 4 [CO1] [1 mark]

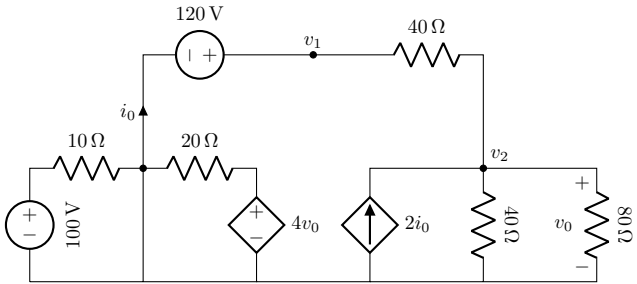


How many nodes are in this circuit?

- ☒ A 5 ☐ B 4 ☐ C 3 ☐ D 6 ☐ E 7

◇ Question 4 of 4 [CO1] [2 marks]

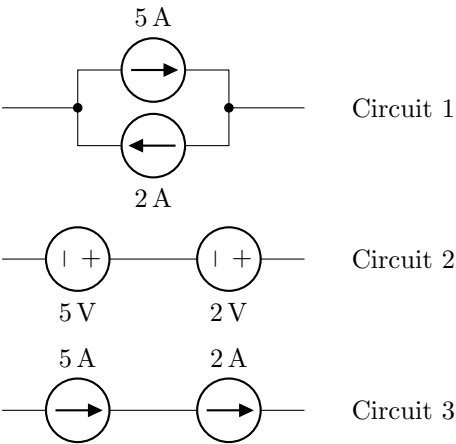Which of the following circuits is/are impossible (violates Kirchhoff’s laws)?



- ☒ A Circuit 1 ☐ B Circuit 1 & 3 ☐ C Circuit 2
☐ D Circuit 3 ☐ E None of the above

Brac University

Semester: Fall 2023
Course Code: CSE250
Circuits And Electronics
Section: 18
Faculty: SDS

Name:

Set

I




Inspiring Excellence

Assessment: *Class Assignment 1*
Duration: 1 hour 20 minutes
Date: September 28, 2023
Full Marks: 10

- ✓ No washroom breaks. Phones must be turned off. Using/carrying any notes during the exam is not allowed.
- ✓ All **4 questions** are compulsory. Marks allotted for each question are mentioned beside each question.
- ✓ Write your answers inside the indicated boxes (where applicable). If you run out of room, continue on the back page.
- ✓ Symbols have their usual meanings.

Student ID	Answers (1-10)	Answers (11-20)	Answers (21-30)
<div><div></div><div></div><div></div><div></div><div></div><div></div><div></div><div></div></div>			
1 <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/>	A B C D E	A B C D E	A B C D E
2 <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/>	1 <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/>	11 <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/>	21 <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/>
3 <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/>	2 <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/>	12 <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/>	22 <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/>
4 <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/>	3 <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/>	13 <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/>	23 <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/>
5 <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/>	4 <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/>	14 <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/>	24 <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/>
6 <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/>	5 <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/>	15 <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/>	25 <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/>
7 <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/>			
8 <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/>	A B C D E	A B C D E	A B C D E
9 <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/>	6 <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/>	16 <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/>	26 <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/>
0 <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/>	7 <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/>	17 <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/>	27 <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/>
	8 <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/>	18 <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/>	28 <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/>
Set Identifier	9 <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/>	19 <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/>	29 <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/>
§ <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/>	10 <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/>	20 <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/>	30 <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/>


◇ Question 1 of 4 [CO1] [1 mark]

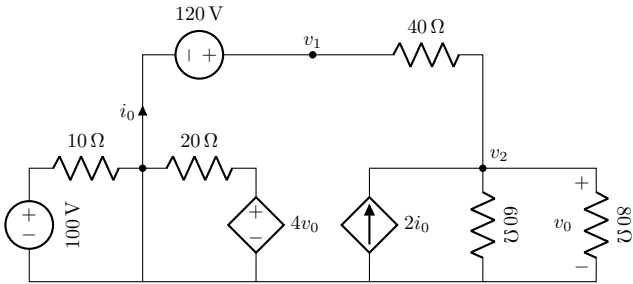

How many nodes are in this circuit?

- (A) 6 (B) 4 (C) 3 (D) 5 (E) 7


◇ Question 2 of 4 [CO3] [5 marks]

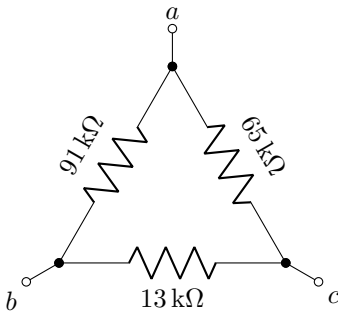

Which of the following statements is true?

- (A) $R_{ab} = 42\Omega, R_{bc} = 12\Omega, R_{ca} = 40\Omega$
(B) $R_{ab} = R_{bc} = R_{ca} = 9.681\text{ k}\Omega$
(C) $R_{ab} = 42\text{ k}\Omega, R_{bc} = 12\text{ k}\Omega, R_{ca} = 40\text{ k}\Omega$
(D) $R_{ab} = 91\text{ k}\Omega, R_{bc} = 13\text{ k}\Omega, R_{ca} = 65\text{ k}\Omega$
(E) None of the above

◇ Question 3 of 4 [CO3] [2 marks]

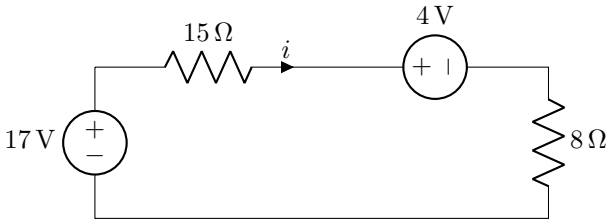


What’s the relation between v_1, v_2 and i ?

- ☐ (A) $-17 - 15i - 4 + 8i = 0$
- ☐ (B) $-17 - 15i + 4 + 8i = 0$
- ☐ (C) $-17 + 15i - 4 + 8i = 0$
- ☒ (D) $-17 + 15i + 4 + 8i = 0$
- ☐ (E) None of the above

◇ Question 4 of 4 [CO1] [2 marks]

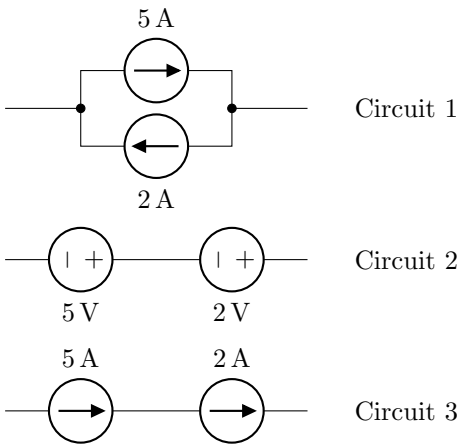Which of the following circuits is/are impossible (violates Kirchhoff’s laws)?



- ☐ (A) Circuit 1 & 3
- ☐ (B) Circuit 2
- ☒ (C) Circuit 1
- ☐ (D) Circuit 3
- ☐ (E) None of the above

Brac University

Semester: Fall 2023
Course Code: CSE250
Circuits And Electronics
Section: 18
Faculty: SDS

Name:

Set

J


Assessment: *Class Assignment 1*
Duration: 1 hour 20 minutes
Date: September 28, 2023
Full Marks: 10



- ✓ No washroom breaks. Phones must be turned off. Using/carrying any notes during the exam is not allowed.
- ✓ All **4 questions** are compulsory. Marks allotted for each question are mentioned beside each question.
- ✓ Write your answers inside the indicated boxes (where applicable). If you run out of room, continue on the back page.
- ✓ Symbols have their usual meanings.

Student ID	Answers (1-10)	Answers (11-20)	Answers (21-30)
<div><div></div><div></div><div></div><div></div><div></div><div></div><div></div><div></div></div>			
1 <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/>	A B C D E	A B C D E	A B C D E
2 <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/>	1 <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/>	11 <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/>	21 <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/>
3 <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/>	2 <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/>	12 <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/>	22 <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/>
4 <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/>	3 <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/>	13 <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/>	23 <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/>
5 <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/>	4 <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/>	14 <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/>	24 <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/>
6 <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/>	5 <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/>	15 <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/>	25 <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/>
7 <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/>			
8 <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/>	A B C D E	A B C D E	A B C D E
9 <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/>	6 <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/>	16 <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/>	26 <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/>
0 <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/>	7 <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/>	17 <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/>	27 <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/>
	8 <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/>	18 <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/>	28 <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/>
Set Identifier	9 <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/>	19 <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/>	29 <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/>
§ <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/>	10 <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/>	20 <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/>	30 <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/> <input type="radio"/>


◇ Question 1 of 4 [CO1] [1 mark]

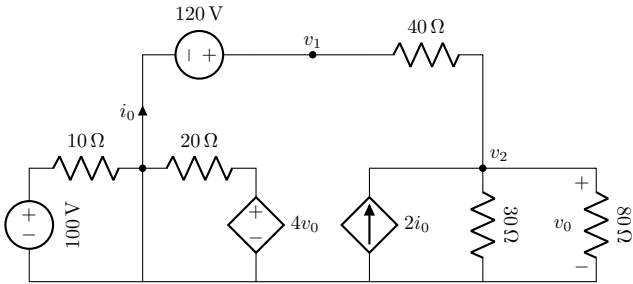

How many nodes are in this circuit?

- (A) 3 (B) 4 (C) 6 (D) 7 (E) 5

◇ Question 2 of 4 [CO3] [5 marks]



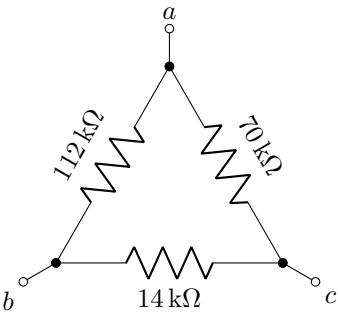


Which of the following statements is true?

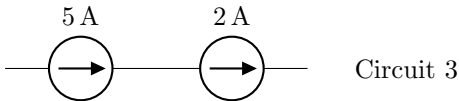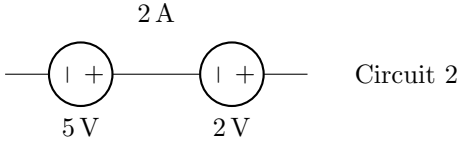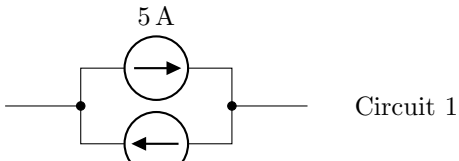- (A) $R_{ab} = 48\,\Omega, R_{bc} = 13\,\Omega, R_{ca} = 45\,\Omega$
(B) $R_{ab} = 48\,\text{k}\Omega, R_{bc} = 13\,\text{k}\Omega, R_{ca} = 45\,\text{k}\Omega$
(C) $R_{ab} = R_{bc} = R_{ca} = 10.566\,\text{k}\Omega$
(D) $R_{ab} = 112\,\text{k}\Omega, R_{bc} = 14\,\text{k}\Omega, R_{ca} = 70\,\text{k}\Omega$
(E) None of the above


◇ Question 3 of 4 [CO1] [2 marks]

Which of the following circuits is/are impossible (violates Kirchhoff’s laws)?



- ☐ (A) Circuit 2 ☐ (B) Circuit 3 ☐ (C) Circuit 1 & 3
☒ (D) **Circuit 1** ☐ (E) None of the above

◇ Question 4 of 4 [CO3] [2 marks]

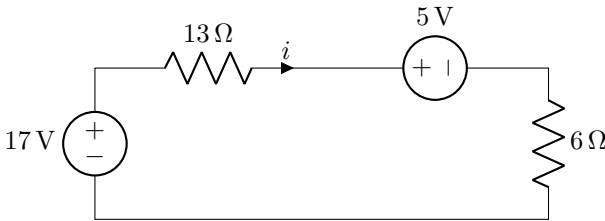

What’s the relation between v_1, v_2 and i ?

- ☐ (A) $-17 + 13i - 5 + 6i = 0$
☐ (B) $-17 - 13i + 5 + 6i = 0$
☐ (C) $-17 - 13i - 5 + 6i = 0$
☒ (D) **$-17 + 13i + 5 + 6i = 0$**
☐ (E) None of the above

